

7.4 Demultiplexer

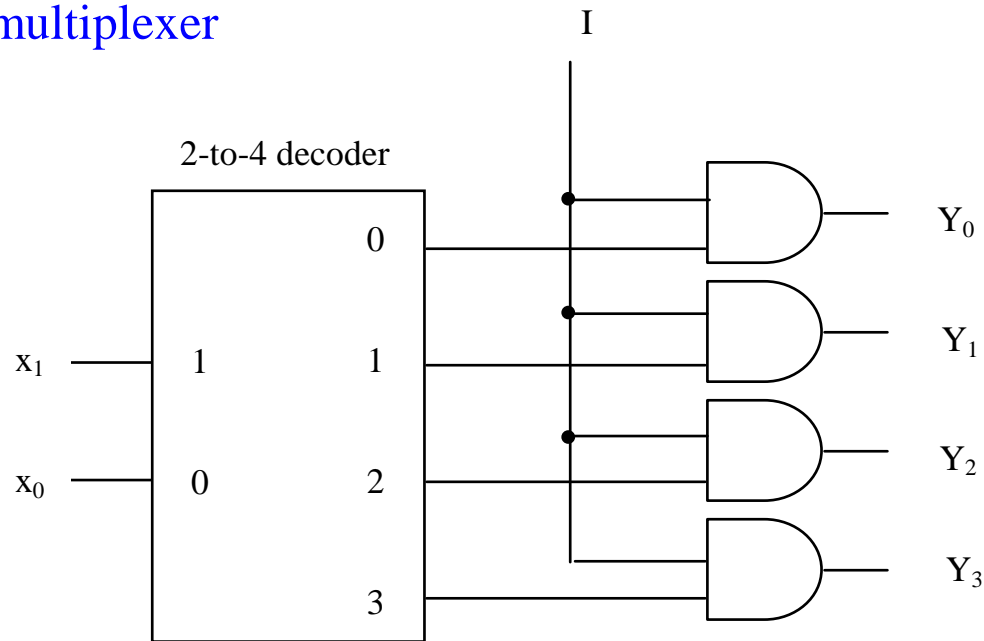


Figure 7.24 Example of a de-multiplexer.

2-to-4 decoder with enable EN
(Section 7.1.4)

$$D_0 = EN (x_1' x_0')$$

$$D_1 = EN (x_1' x_0)$$

$$D_2 = EN (x_1 x_0')$$

$$D_3 = EN (x_1 x_0)$$

Demultiplexer

$$Y_0 = I (x_1' x_0')$$

$$Y_1 = I (x_1' x_0)$$

$$Y_2 = I (x_1 x_0')$$

$$Y_3 = I (x_1 x_0)$$

EN input of decoder as data input for demultiplexer

Demultiplexer with Enable

$$Y_0 = I \bullet EN \bullet (x_1' x_0')$$

$$Y_1 = I \bullet EN \bullet (x_1' x_0)$$

$$Y_2 = I \bullet EN \bullet (x_1 x_0')$$

$$Y_3 = I \bullet EN \bullet (x_1 x_0)$$

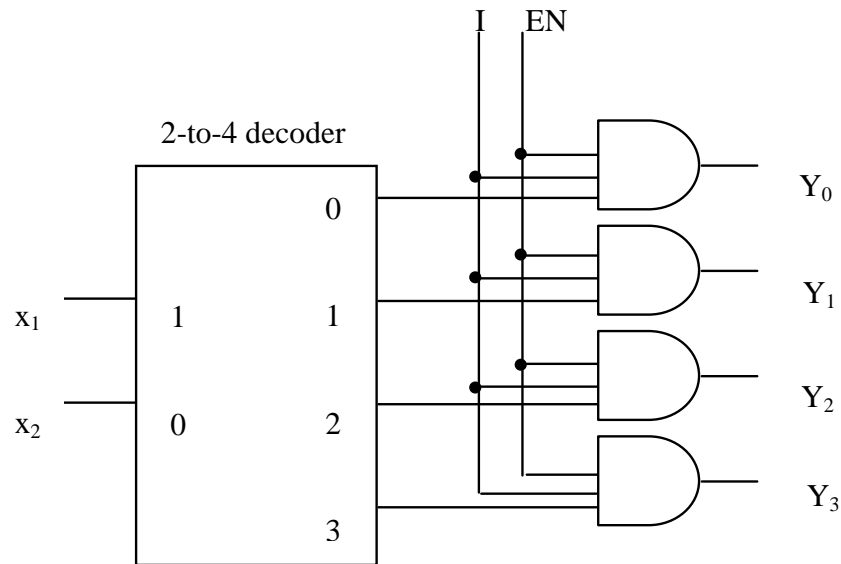


Figure 7.25 A de-multiplexer with enable input.

Demultiplexer with Enable

Data input: I

Control signals: x_1, x_2

Enable (Strobe): EN



Outputs: Y_0, Y_1, Y_2, Y_3

Decoder with Enable

Inputs: x_1, x_2

Enable (strobe): EN, I

Outputs: Y_0, Y_1, Y_2, Y_3

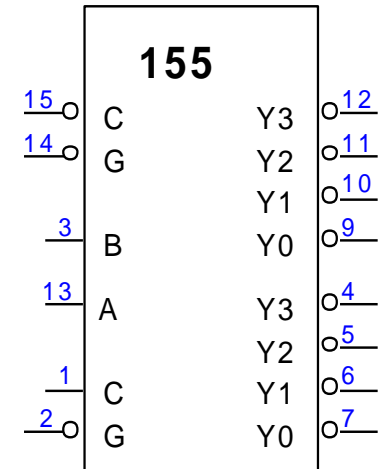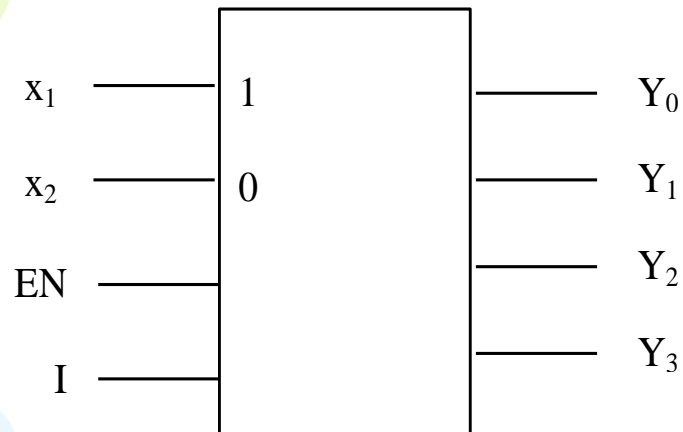



74155 Dual 2-to-4 Decoders/Demultiplexers

EN (active-high) → G (active-low)
 I (active-high) → C (active-low in 1), C (active-high in 2)
 x_1, x_2 → B, A respectively
 Active-high outputs → Active-low outputs

Conversion of 74155 to 3-to-8 Decoder


See Figure 7.4 for conversion.

3-to-8 decoder

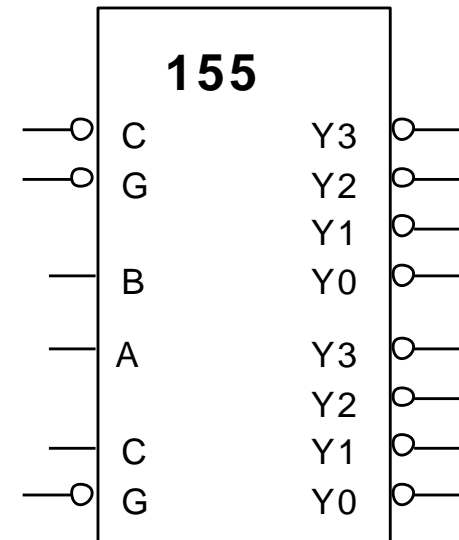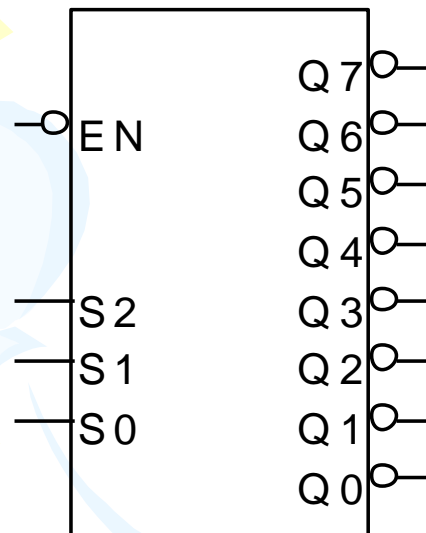

74153 Dual 4-to-1 Multiplexer

Active-low strobe G. Active-high output.

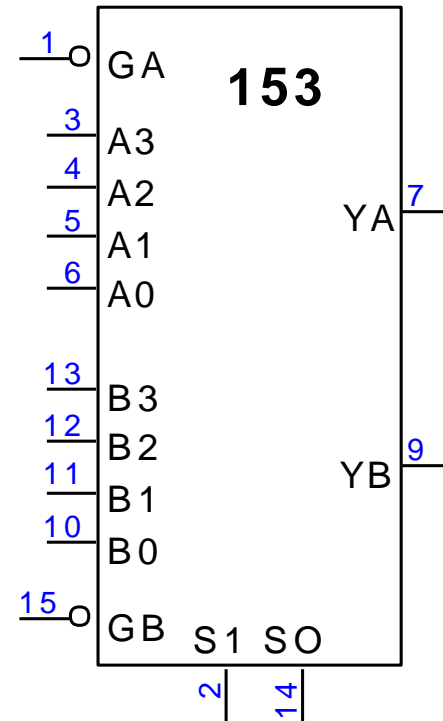

Conversion of 74153 to 8-to-1 Multiplexer

See Figure 7.19 for conversion.

