

16.265 Logic Design
 Experiment 4:: Counter - JK flip-flops
 Name: Dangnhi Ngo
 Student Logic Number: 140
 Counter sequence: 134760

