

## CHAPTER 9

# **LATCHES AND FLIP-FLOPS**

## 9.1 Introduction

 


Figure 9.1 Structure of a sequential circuit.

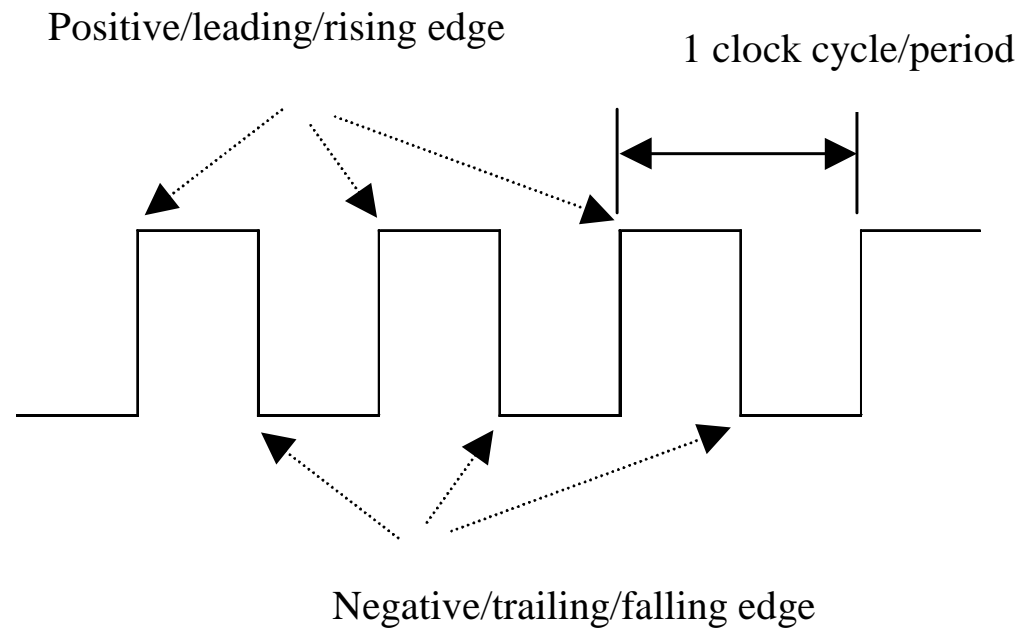


Figure 9.2 Clock for a synchronous sequential circuit.

## 9.2 SR Latch

Figure 9.3 A cross-coupled NOR SR latch.

 
 


Figure 9.4 Timing diagrams for the cross-coupled NOR SR latch.

 
 


Table 9.1 Characteristic table for SR latch.

Present inputs S R		Present state Q	Next state Q <sup>+</sup>	Function
0	0	0	0	Hold (No change)
0	0	1	1	
0	1	0	0	Reset
0	1	1	0	
1	0	0	1	Set
1	0	1	1	
1	1	0	d	Prohibited
1	1	1	d	

t<sub>3</sub>  
t<sub>1</sub>  
t<sub>4</sub>  
t<sub>2</sub>,  
t<sub>0</sub>  
t<sub>0</sub>  
t<sub>5</sub>

 


Table 9.1 Characteristic table for SR latch.

Present inputs S R		Present state Q	Next state Q <sup>+</sup>	Function
0	0	0	0	Hold (No change)
0	0	1	1	
0	1	0	0	Reset
0	1	1	0	
1	0	0	1	Set
1	0	1	1	
1	1	0	d	Prohibited
1	1	1	d	

t<sub>3</sub>  
t<sub>1</sub>  
t<sub>4</sub>  
t<sub>2</sub>  
t<sub>0</sub>  
t<sub>0</sub>  
t<sub>5</sub>

Characteristic equation:

$$Q^+ = S + R'Q$$

$$SR = 0$$

 


Figure 9.5 Next-state map for SR latch.



 


Figure 9.6 Logic symbol for SR

## Gated SR Latch

 

(a)

 

(b)

Figure 9.7 Gated SR latch. (a) Circuit structure. (b) Logic symbol.



 


Figure 9.1 Structure of a sequential circuit.

## 9.3 Flip-flops

### 9.3.1 Gated latch as Flip-flop

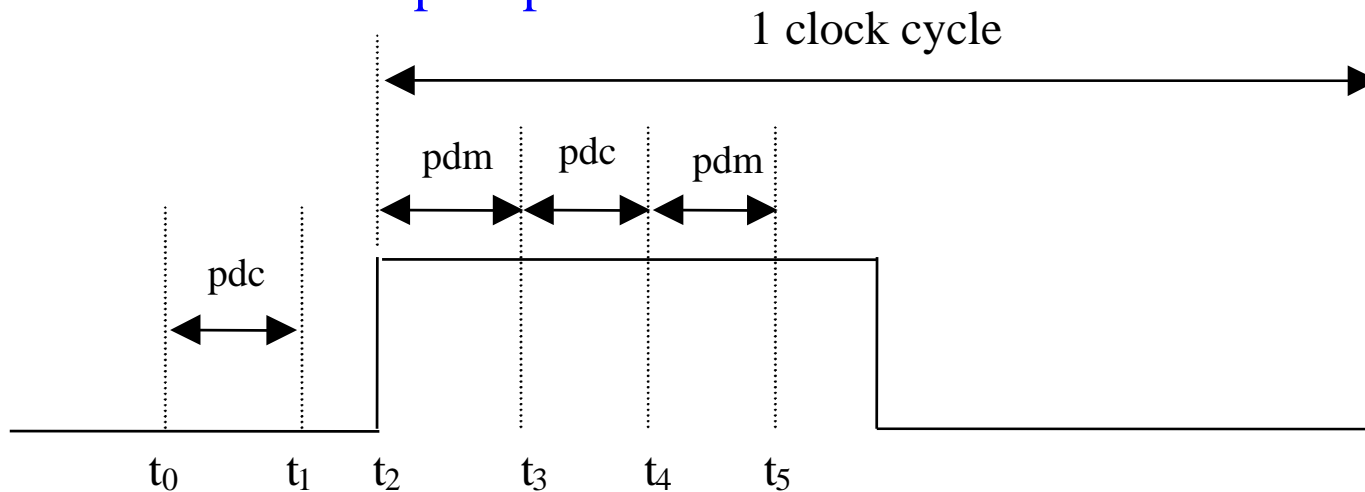


Figure 9.8 Timing diagram for a gated SR latch as a flip-flop.

 


Figure 9.1 Structure of a sequential circuit.

## 9.3.2 Flip-flops

### Master-slave SR flip-flop

 


Figure 9.9 Master-slave SR flip-flop.

### 9.3.2 Flip-flops

#### Master-slave SR flip-flop

 


Figure 9.9 Master-slave SR flip-flop.

 


Figure 9.10 Logic symbol for SR flip-flop.

 


Figure 9.11 State diagram for SR flip-flop.

## JK Flip-flop

 


Figure 9.12 JK flip-flop. (a) Circuit structure. (b) Logic symbol.

Table 9.2 Characteristic table for JK flip-flop.

Present inputs J K		Present state Q	S = JQ'	R = KQ	Next state Q <sup>+</sup>	Function
0	0	0	0	0	0	Hold (No change)
0	0	1	0	0	1	
0	1	0	0	0	0	Reset
0	1	1	0	1	0	
1	0	0	1	0	1	Set
1	0	1	0	0	1	
1	1	0	1	0	1	Toggle
1	1	1	0	1	0	

Characteristic equation:  $Q^+ = JQ' + K'Q$

Figure 9.13 Next-state map  
for JK flip-flop.

JK		00	01	11	10
Q	0	0	0	1	1
	1	1	0	0	1

$Q^+$

## D flip-flop

 


Figure 9.14 D flip-flop. (a) Circuit structure. (b) Logic symbol.

Table 9.3 Characteristic table for D flip-flop.

Present input D	Present state Q	J = D	K = D'	Next state Q <sup>+</sup>
0	0	0	1	0
0	1	0	1	0
1	0	1	0	1
1	1	1	0	1

Characteristic equation

$$Q^+ = D$$

## T flip-flop

 


Figure 9.15 T flip-flop. (a) Circuit structure. (b) Logic symbol.

Table 9.4 Characteristic table for T flip-flop.

Present input T	Present state Q	J = T	K = T	Next state Q <sup>+</sup>
0	0	0	0	0
0	1	0	0	1
1	0	1	1	1
1	1	1	1	0

Characteristic equation  $Q^+ = T \oplus Q$

### 9.3.3 Edge-triggered Flip-flops

 


Figure 9.16 Timing constraint of positive-edge triggered flip-flop.

 


Figure 9.17 Logic symbols for edge-triggered flip-flop.  
(a) positive edge. (b) Negative edge.



### 9.3.4 Asynchronous Preset and Clear

 


Figure 9.18 Logic symbols for flip-flops with asynchronous preset and clear.

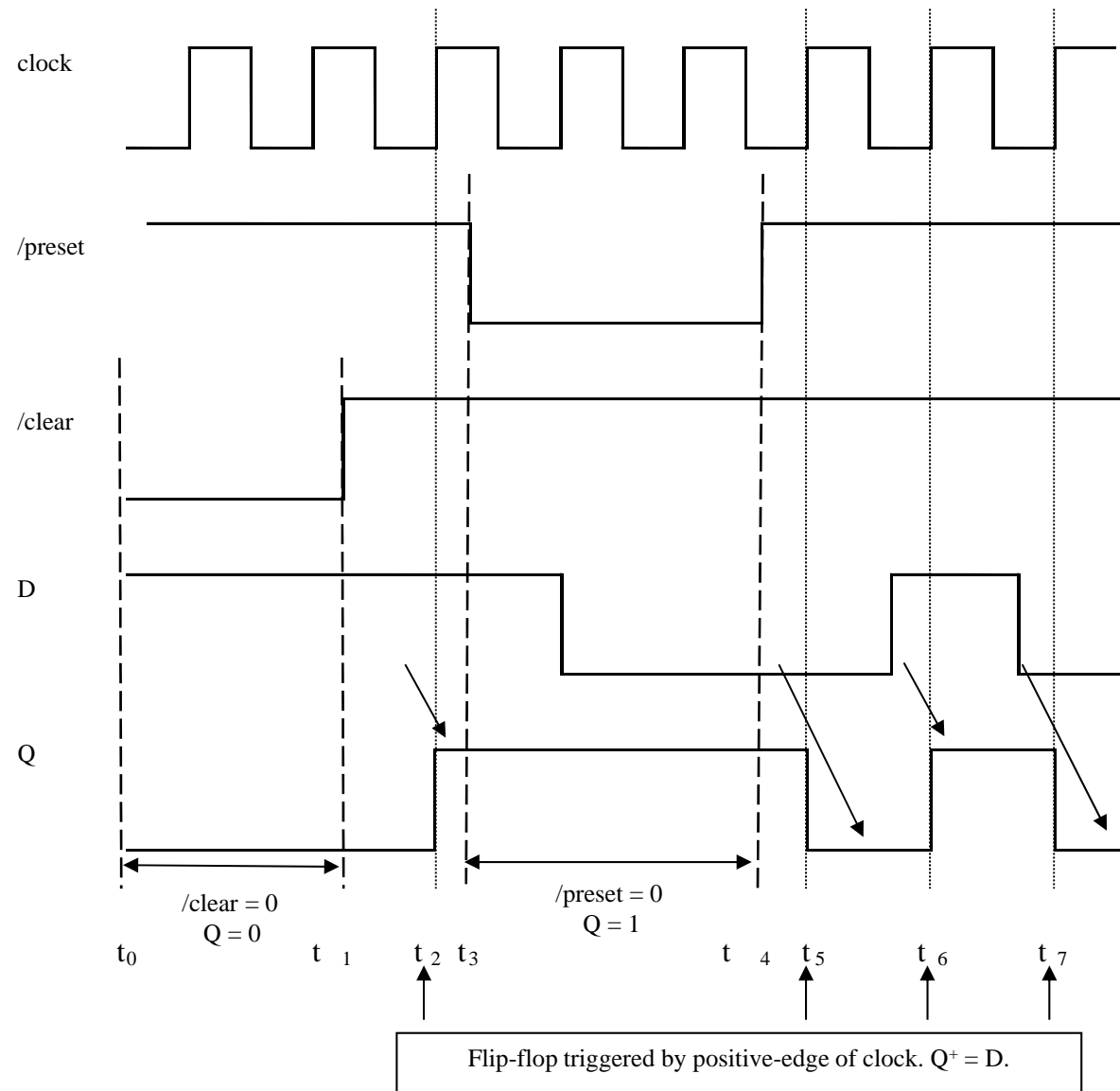


Figure 9.19 Timing diagrams for a positive edge-triggered D flip-flop with asynchronous preset and clear.