



CHAPTER 10

SYNCHRONOUS SEQUENTIAL CIRCUITS

10.1 Registers



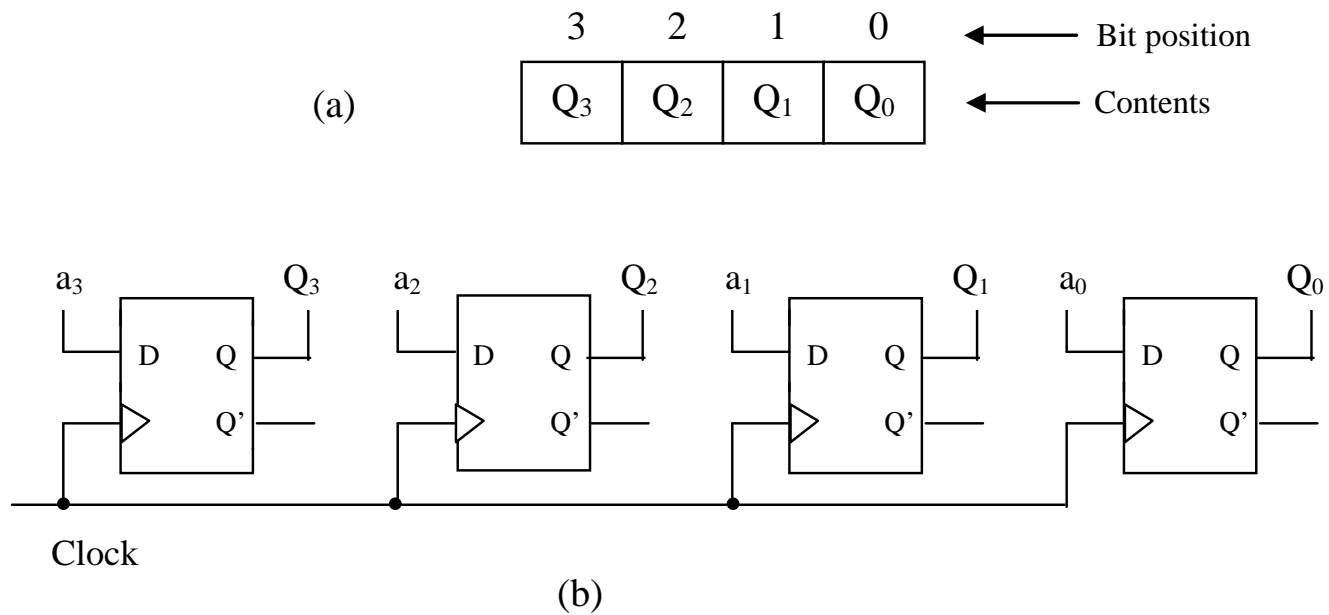
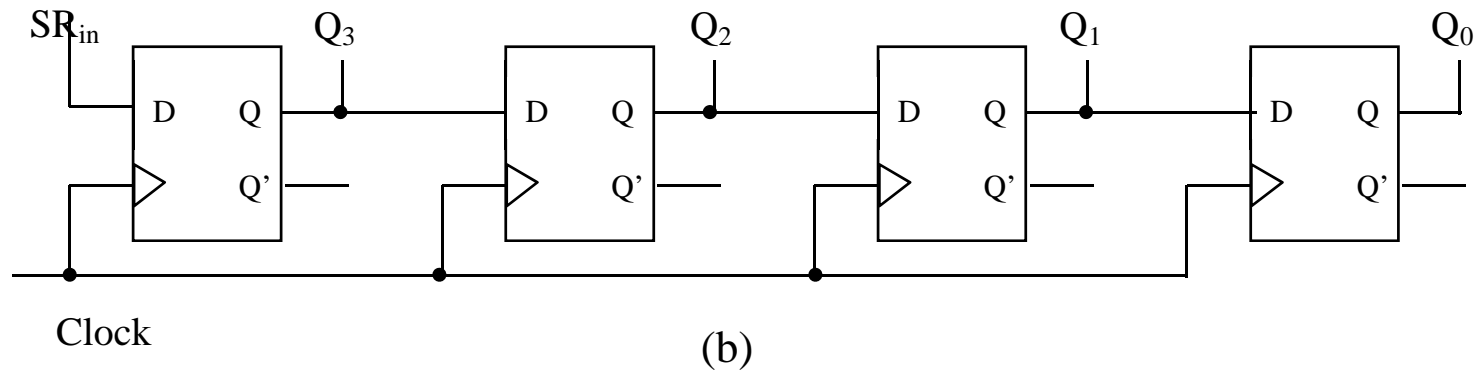
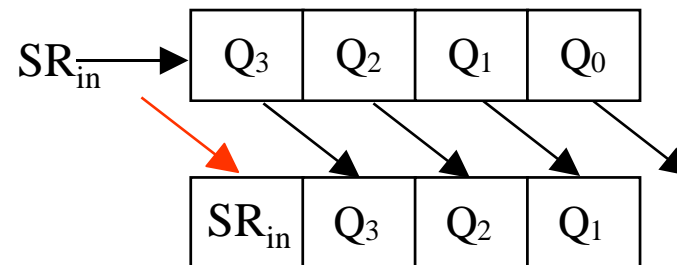
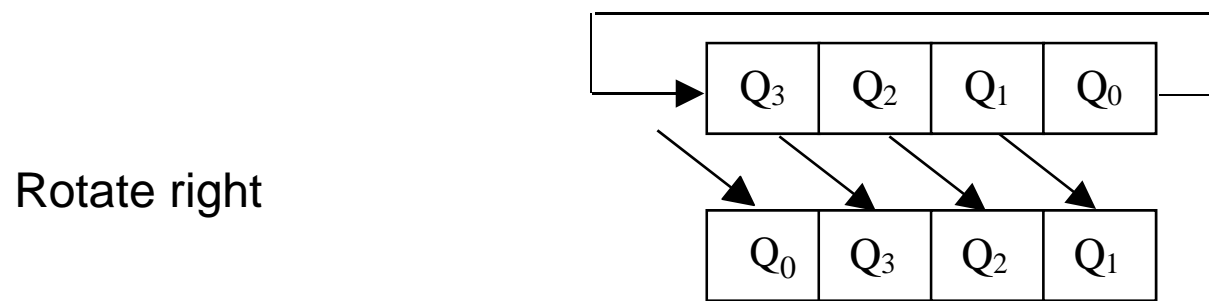




Figure 10.1 (a) Notation for a 4-bit register. (b) Circuit for a 4-bit register.

Parallel load

Figure 10.2 (a) Operation of a 4-bit shift-right register.
(b) Circuit of register.

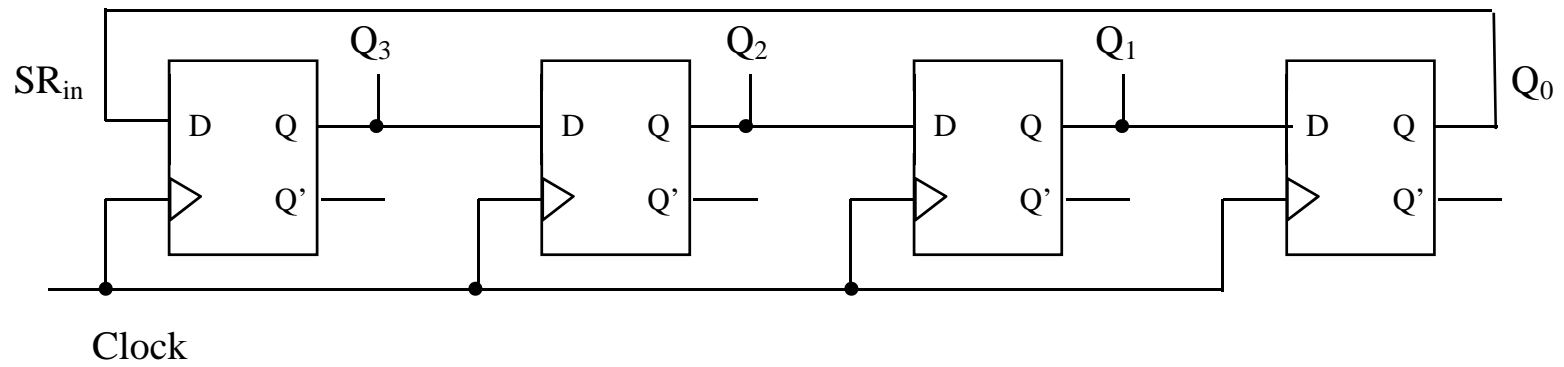

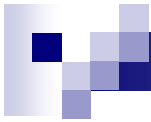

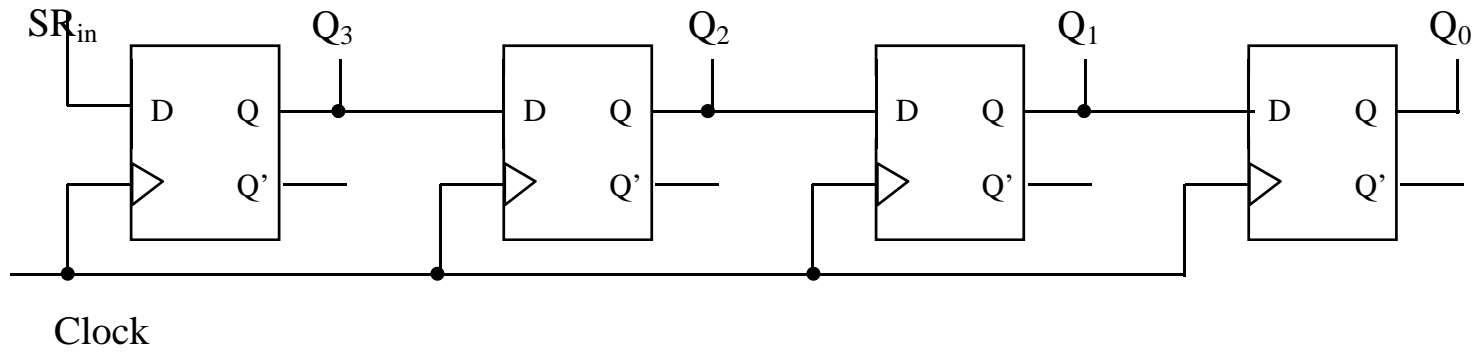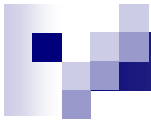

Serial load

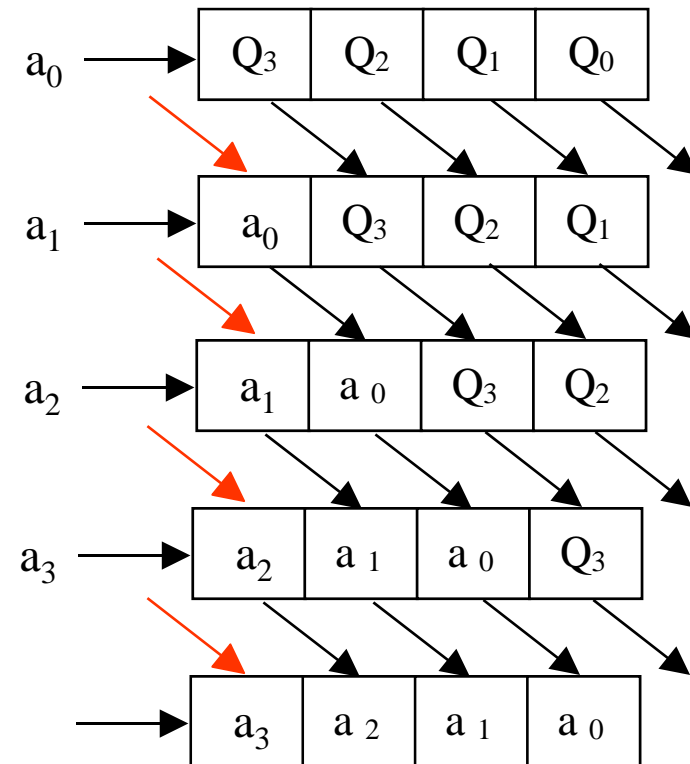


Table 10.1 Function table for a 4-bit universal shift register.

Function	$s_1 s_0$	Contents			
		Bit position			
		3	2	1	0
Hold	0 0	Q_3	Q_2	Q_1	Q_0
Shift right	0 1	SR_{in}	Q_3	Q_2	Q_1
Shift left	1 0	Q_2	Q_1	Q_0	SL_{in}
Parallel load	1 1	a_3	a_2	a_1	a_0

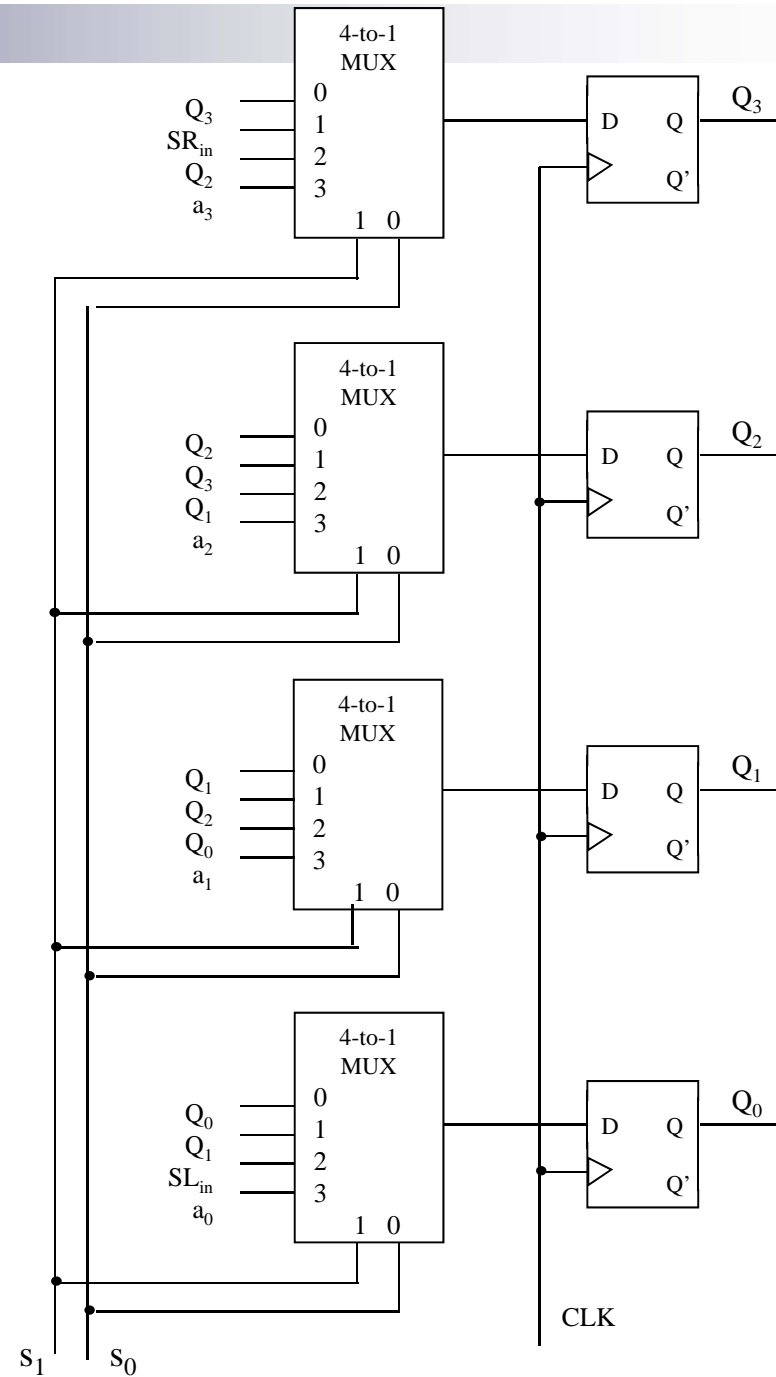


Figure 10.3 Design of a 4-bit universal shift register.

10.2 Counter

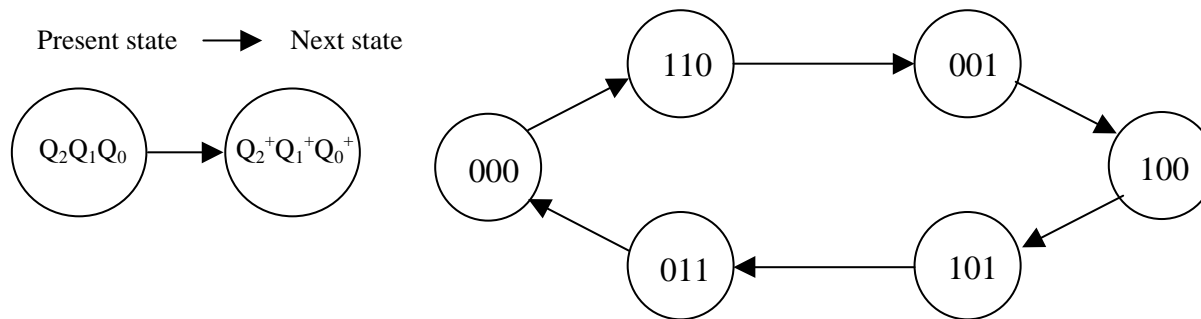


Figure 10.4 State diagram of a 6-state counter.

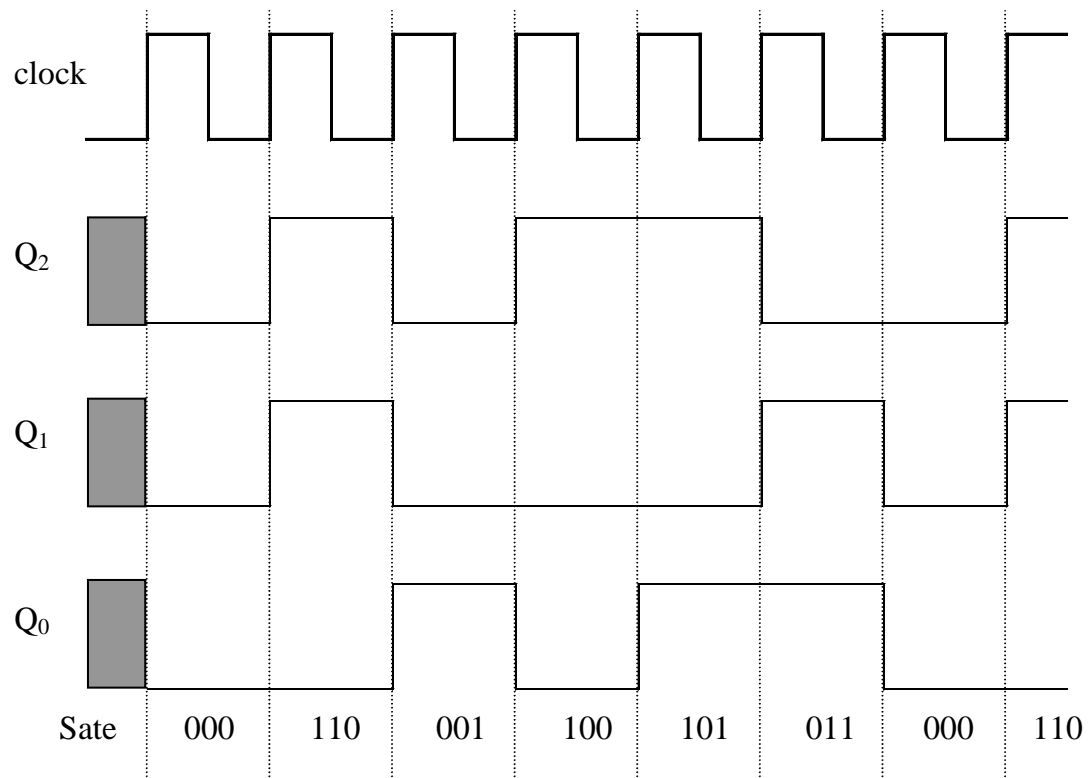


Figure 10.5 Timing diagram of the 6-state counter in Figure 10.4.

Ring Counter

Table 10.2 State assignment table for a 4-state ring counter

State	Q ₀	Q ₁	Q ₂	Q ₃
T ₀	1	0	0	0
T ₁	0	1	0	0
T ₂	0	0	1	0
T ₃	0	0	0	1

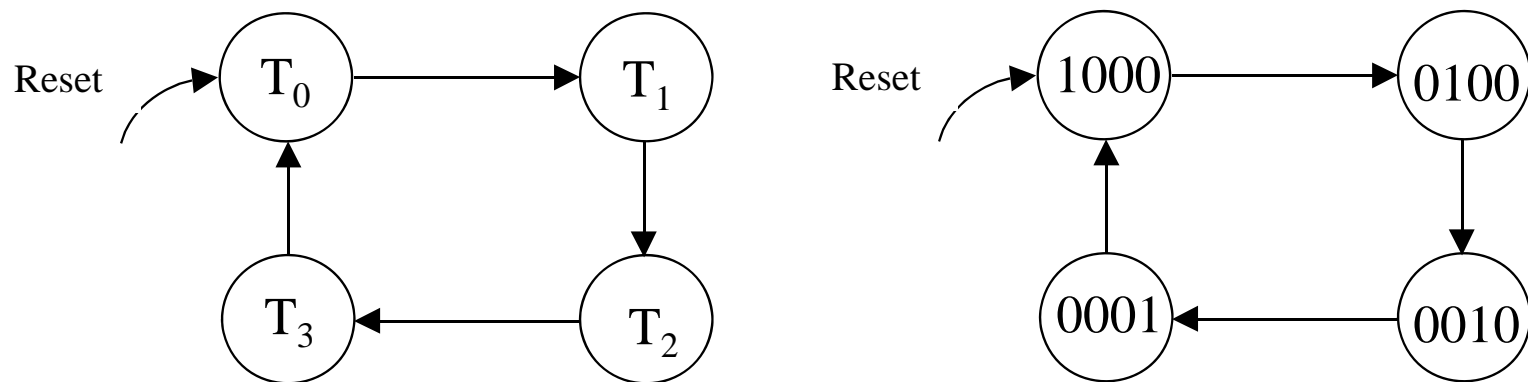


Figure 10.6 State diagram for a 4-state ring counter.

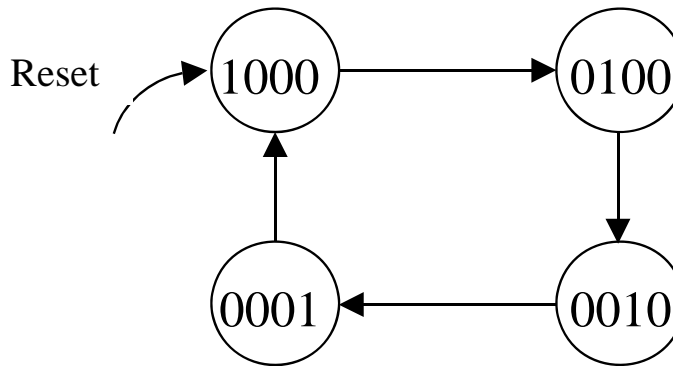


Figure 10.6 State diagram for a 4-state ring counter.

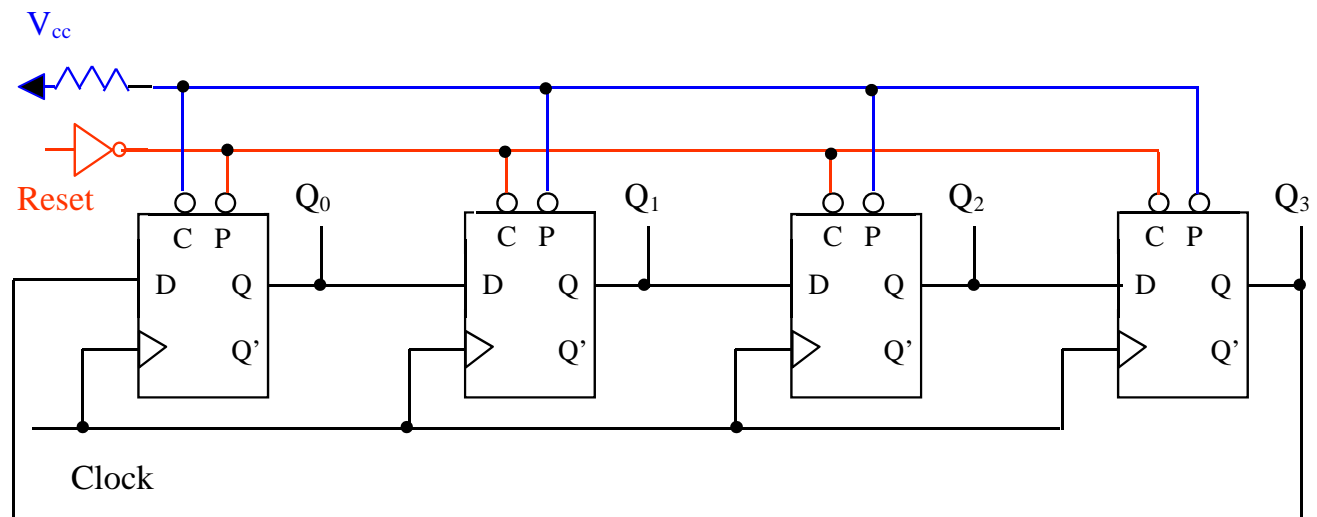
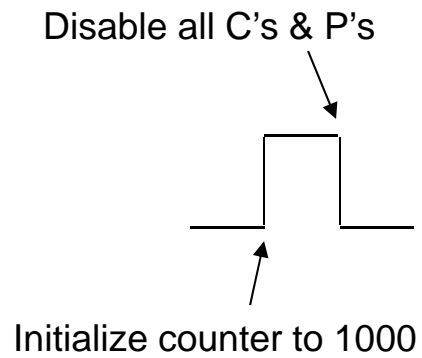


Figure 10.7 Circuit diagram for a 4-bit ring counter.

10.3 Analysis of Synchronous Sequential Circuits

Moore model

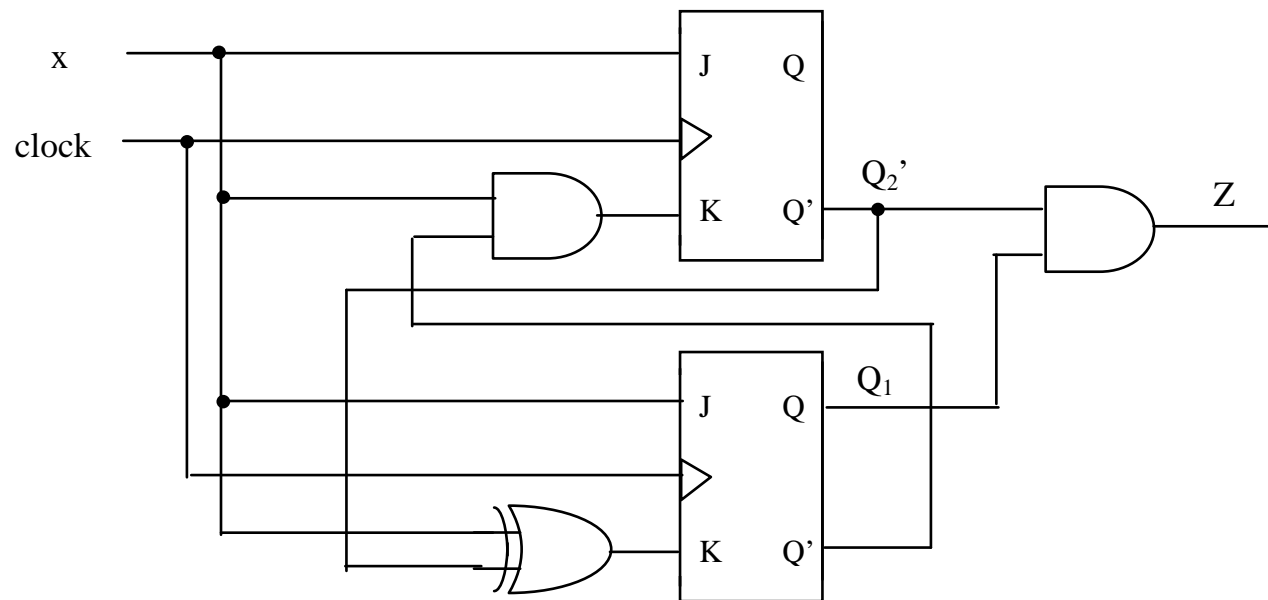


Figure 10.8 Synchronous sequential circuit of Moore model for analysis.

Step 1: Write the excitation and output functions.

$$\begin{array}{ll} J_2 = x & K_2 = x Q_1' \\ J_1 = x & K_1 = x \oplus Q_2' \\ Z = Q_2' Q_1 \end{array}$$



Step 1: Write the excitation and output functions.

$$\begin{aligned}J_2 &= x & K_2 &= x Q_1' \\J_1 &= x & K_1 &= x \oplus Q_2' \\Z &= Q_1\end{aligned}$$

Step 2: Substitute the excitation functions into the characteristic equations for the two flip-flops to get the next-state equations.

$$Q_2^+ = J_2 Q_2' + K_2' Q_2 = x Q_2' + (x Q_1')' Q_2 = x Q_2' + x' Q_2 + Q_2 Q_1$$

$$Q_1^+ = J_1 Q_1' + K_1' Q_1 = x Q_1' + (x \oplus Q_2')' Q_1 = x Q_1' + x' Q_2 Q_1 + x Q_2' Q_1$$

Step 3: Convert the next-state equations to next-state maps.

$Q_2 Q_1$					
		00	01	11	10
x	0	0	0	1	1
	1	1	1	1	0

Q_2^+

$Q_2 Q_1$					
		00	01	11	10
x	0	0	0	1	0
	1	1	1	0	1

Q_1^+

Figure 10.9 Next-state equations.

Step 3: Convert the next-state equations to next-state maps.

		Q_2Q_1			
		00	01	11	10
x	0	0	0	1	1
	1	1	1	1	0

Q_2^+

		Q_2Q_1			
		00	01	11	10
x	0	0	0	1	0
	1	1	1	0	1

Q_1^+

Figure 10.9 Next-state equations.

Step 4: Convert the next-state maps to a table. The table is called a transition table because it shows the transition from present states to next states. If the output is also included in the table, it is called a transition/output table.

Table 10.3 Transition/output table.

Q_2Q_1	$Q_2^+ Q_1^+$		Z
	$x = 0$	$x = 1$	
00	00	11	0
01	00	11	1
11	11	10	0
10	10	01	0

Step 4: Convert the next-state maps to a table. The table is called a transition table because it shows the transition from present states to next states. If the output is also included in the table, it is called a transition/output table.

Table 10.3 Transition/output table.

Q_2Q_1	$Q_2^+ Q_1^+$		Z
	x = 0	x = 1	
0 0	0 0	1 1	0
0 1	0 0	1 1	1
1 1	1 1	1 0	0
1 0	1 0	0 1	0

Step 5: Replace the states in the transition/output table using the state assignment in Table 10.4. The transition/output table is transformed into a state/output table.

Table 10.4 State assignment.

Q_2Q_1	State
0 0	A
0 1	B
1 1	C
1 0	D

Table 10.5 State/output table.

Present state	Next state		Z
	x = 0	x = 1	
A	A	C	0
B	A	C	1
C	C	D	0
D	D	B	0

Step 5: Replace the states in the transition/output table using the state assignment in Table 10.4. The transition/output table is transformed into a state/output table.

Table 10.4 State assignment.

Q_2Q_1	State
0 0	A
0 1	B
1 1	C
1 0	D

Table 10.5 State/output table.

Present state	Next state		Z
	x = 0	x = 1	
A	A	C	0
B	A	C	1
C	C	D	0
D	D	B	0

Step 6: Convert the state/output table to a state diagram.


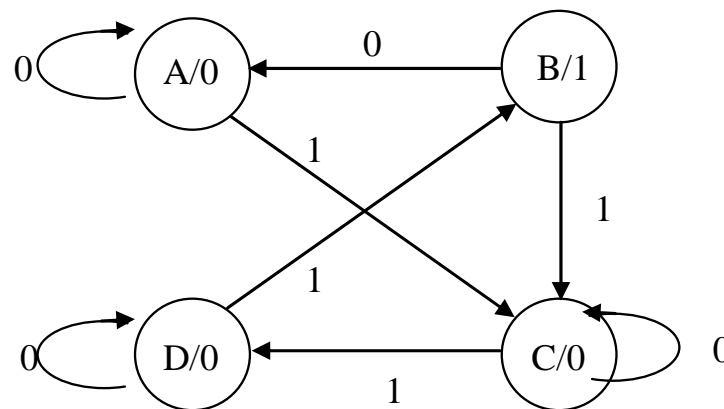


Figure 10.10 State diagram.

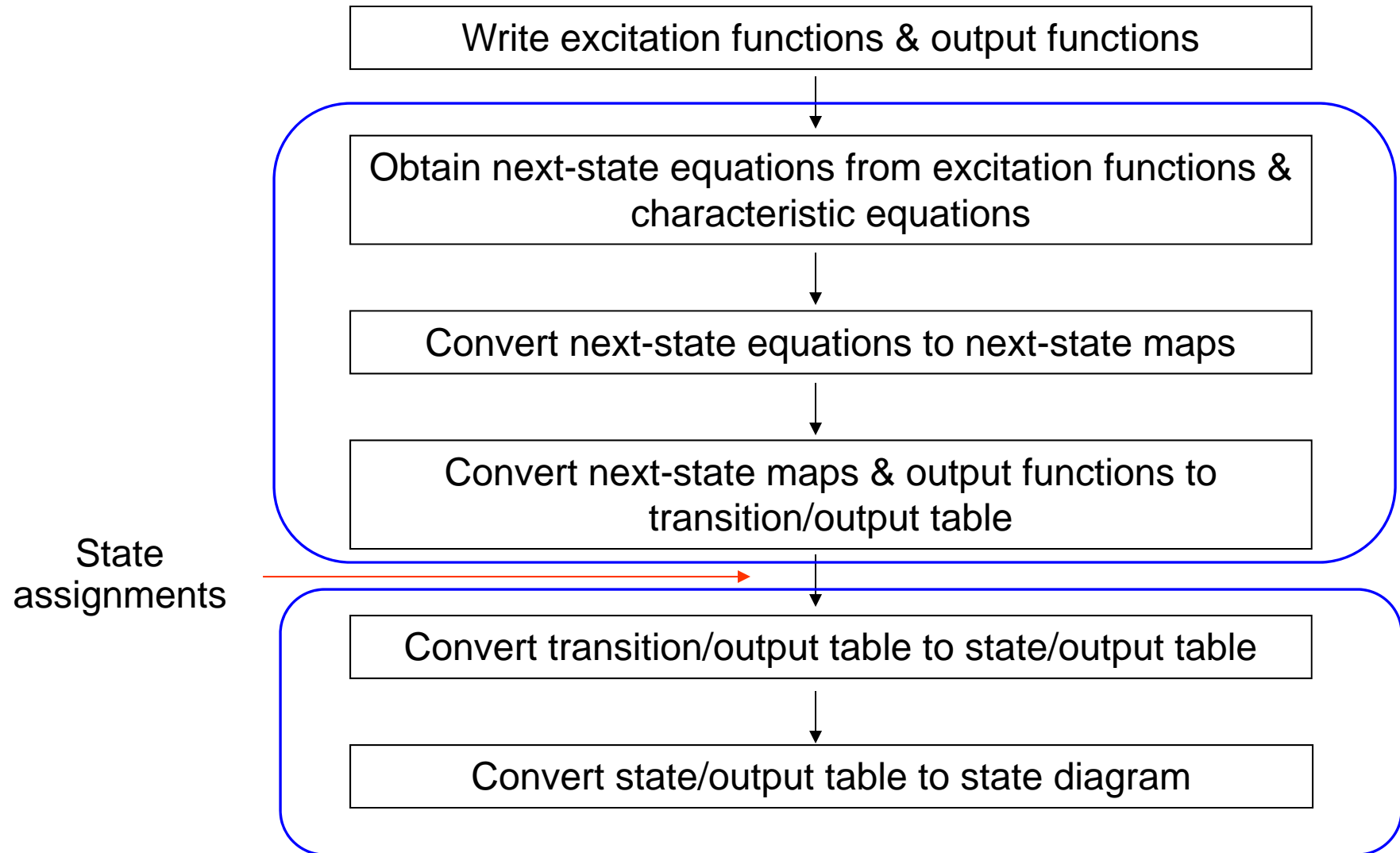

Mealy model

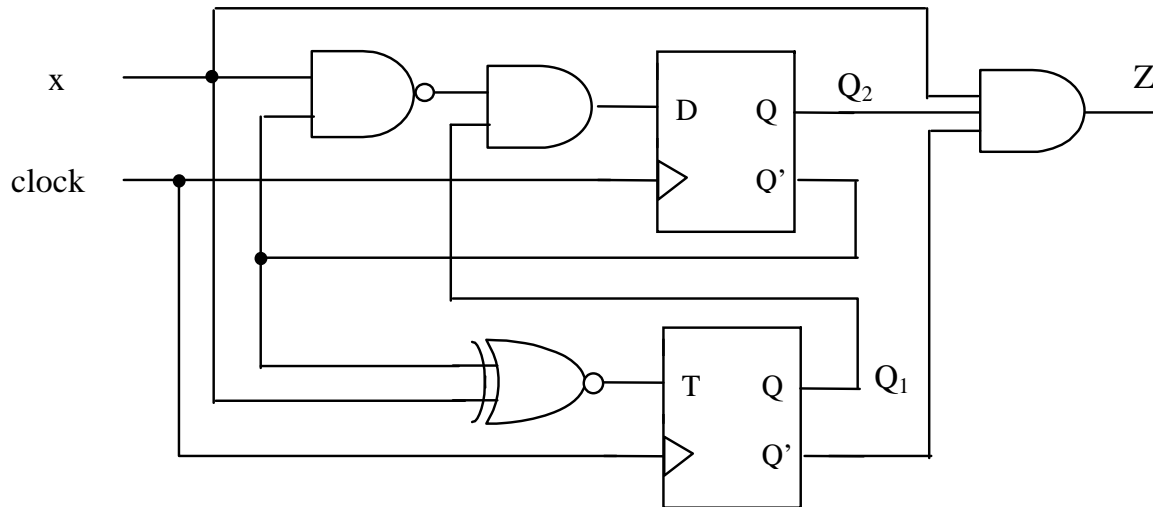


Figure 10.11 Synchronous sequential circuit of Moore model for analysis.

Step 1: Write the excitation and output functions.

$$D_2 = (xQ_2')'Q_1$$

$$T_1 = x \odot Q_2'$$

$$Z = xQ_2Q_1'$$

Step 2: Substitute the excitation functions into the characteristic equations to get the next-state equations.

$$Q_2^+ = D_2 = (xQ_2')'Q_1 = x'Q_1 + Q_2Q_1$$

$$Q_1^+ = T_1 \oplus Q_1 = (x \odot Q_2') \oplus Q_1 = (x \odot Q_2)' \oplus Q_1 = x \oplus Q_2 \oplus Q_1$$

Step 2: Substitute the excitation functions into the characteristic equations to get the next-state equations.

$$Q_2^+ = D_2 = (xQ_2')'Q_1 = x'Q_1 + Q_2Q_1$$

$$Q_1^+ = T_1 \oplus Q_1 = (x \odot Q_2') \oplus Q_1 = (x \odot Q_2)' \oplus Q_1 = x \oplus Q_2 \oplus Q_1$$

Step 3: Convert the next-state equations to next-state maps. Q_1^+ is the same as the function in Example 5.6.

		Q_2Q_1			
		00	01	11	10
x	0	0	1	1	0
	1	0	0	1	0

Q_2^+

		Q_2Q_1			
		00	01	11	10
x	0	0	1	0	1
	1	1	0	1	0

Q_1^+

Figure 10.12 Next-state equations.

Step 4: Convert the next-state maps to a transition/output table. Note that the values of Z do not have to be listed separately. They are placed next to the values of $Q_2^+Q_1^+$ because Z is also a function of Q_2 , Q_1 , and x .

Table 10.6 Transition/output table.

Q_2Q_1	$Q_2^+ Q_1^+, Z$	
	$x = 0$	$x = 1$
00	00, 0	01, 0
01	11, 0	00, 0
11	10, 0	11, 0
10	01, 0	00, 1

Table 10.6 Transition/output table.

Q_2Q_1	$Q_2^+ Q_1^+, Z$	
	$x = 0$	$x = 1$
0 0	0 0, 0	0 1, 0
0 1	1 1, 0	0 0, 0
1 1	1 0, 0	1 1, 0
1 0	0 1, 0	0 0, 1

Step 5: Convert the transition/output table to a state/output table using the state assignment in Table 10.7.

Table 10.7 State assignment.

Q_2Q_1	State
0 0	A
0 1	B
1 1	C
1 0	D

Table 10.8 State/output table.

Present state	Next state	
	$x = 0$	$x = 1$
A	A, 0	B, 0
B	C, 0	A, 0
C	D, 0	C, 0
D	B, 0	A, 1

Step 5: Convert the transition/output table to a state/output table using the state assignment in Table 10.7.

Table 10.7 State assignment.

Q_2Q_1	State
0 0	A
0 1	B
1 1	C
1 0	D

Table 10.8 State/output table.

Present state	Next state	
	x = 0	x = 1
A	A, 0	B, 0
B	C, 0	A, 0
C	D, 0	C, 0
D	B, 0	A, 1

Step 6: Convert the state/output table to a state diagram. Because Z is a function of the present state and the input x, its values are placed after x and separated by a slash.

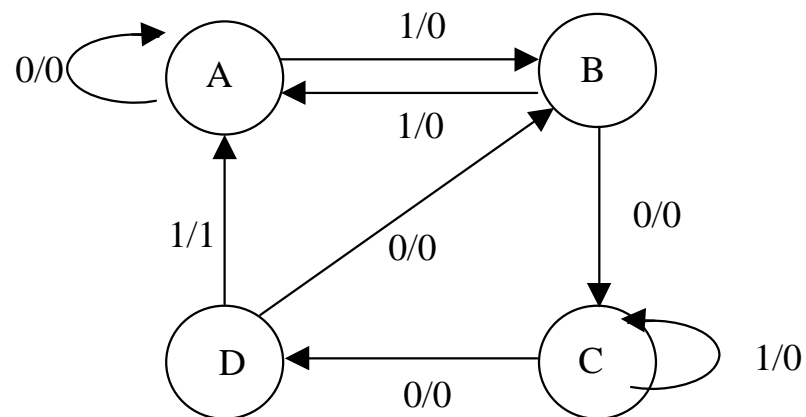


Figure 10.13 State diagram.

10.4 Synthesis of Synchronous Sequential Circuits

10.4.1 Counter Design

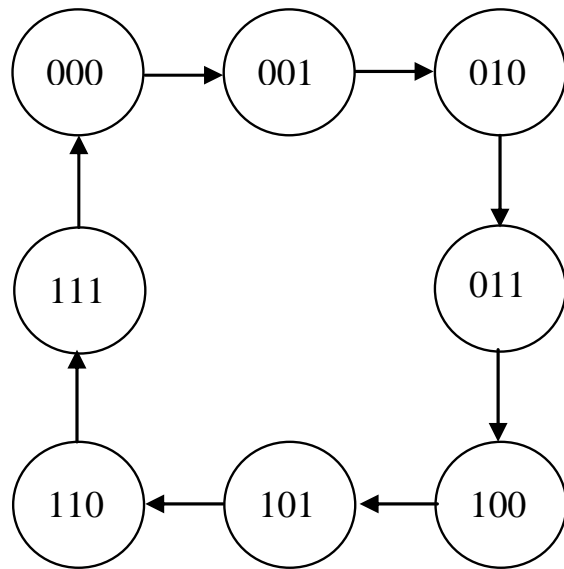


Table 10.9 Transition table for a modulo-8 counter.

Present state $Q_2Q_1Q_0$	Next state $Q_2^+Q_1^+Q_0^+$
0 0 0	0 0 1
0 0 1	0 1 0
0 1 0	0 1 1
0 1 1	1 0 0
1 0 0	1 0 1
1 0 1	1 1 0
1 1 0	1 1 1
1 1 1	0 0 0

Figure 10.14 State diagram for a modulo-8 counter.

Q_2Q_1					Q_2Q_1					Q_2Q_1							
Q_0		00	01	11	10	Q_0		00	01	11	10	Q_0		00	01	11	10
		0	0	1	1			0	1	1	0			1	1	0	0
		1	0	1	0	1		1	0	0	1		1	0	0	0	0
Q_2^+					Q_1^+					Q_0^+							

Figure 10.15 Next-state maps for a modulo-8 counter.

		Q_2Q_1			
		00	01	11	10
Q_0	0	0	0	1	1
	1	0	1	0	1

Q_2^+

		Q_2Q_1			
		00	01	11	10
Q_0	0	0	1	1	0
	1	1	0	0	1

Q_1^+

		Q_2Q_1			
		00	01	11	10
Q_0	0	1	1	1	1
	1	0	0	0	0

Q_0^+

Figure 10.15 Next-state maps for a modulo-8 counter.

$$\begin{aligned}
 Q_2^+ &= Q_2'Q_1Q_0 + Q_2Q_0' + Q_2Q_1' = Q_2'Q_1Q_0 + (Q_0' + Q_1')Q_2 \\
 &= (Q_1Q_0)Q_2' + (Q_1Q_0)'Q_2 = (Q_1Q_0) \oplus Q_2
 \end{aligned}$$

$$Q_1^+ = Q_1Q_0' + Q_1'Q_0 = Q_1 \oplus Q_0$$

$$Q_0^+ = Q_0'$$

Design with D flip-flops

$$D_2 = Q_2^+ = (Q_1 Q_0) \oplus Q_2$$

$$D_1 = Q_1^+ = Q_1 \oplus Q_0$$

$$D_0 = Q_0^+ = Q_0'$$

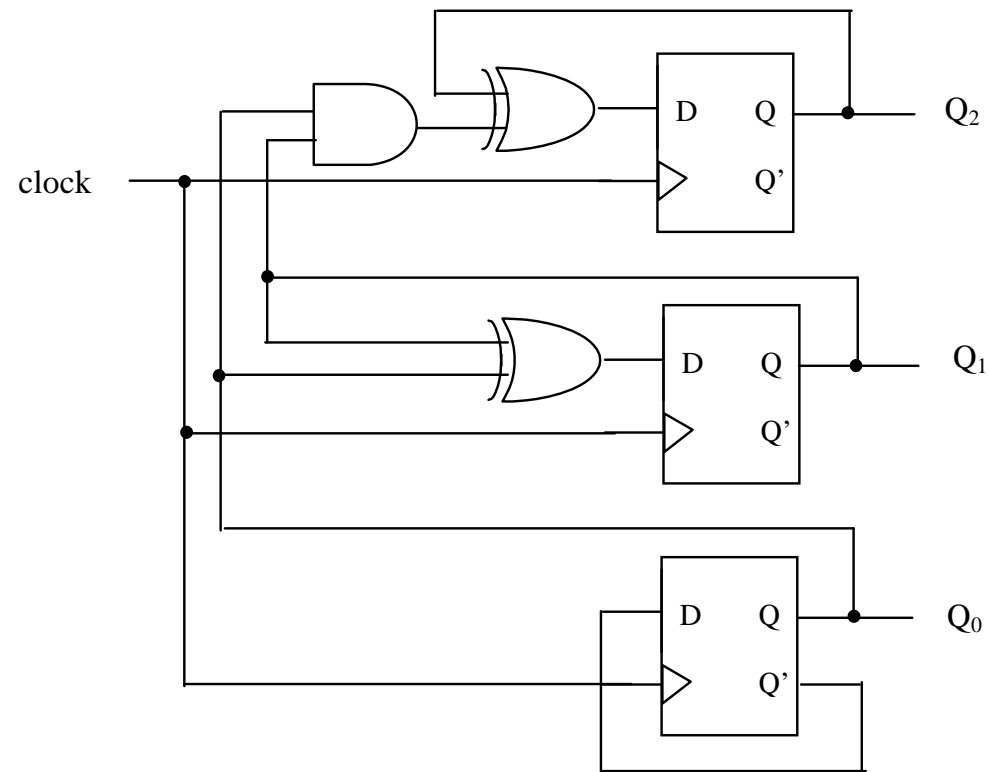


Figure 10.16 Circuit diagram for modulo-8 counter.

Design with JK flip-flops

Table 10.10 Excitation table for JK flip-flops.

Q	Q ⁺	J	K	Function
0	0	0	d	No change (JK = 00) or reset (JK = 01)
0	1	1	d	Set (JK = 10) or toggled (JK = 11)
1	0	d	1	Reset (JK = 01) or toggle (JK = 11)
1	1	d	0	No change (JK = 00) or set (JK = 10)

Table 10.11 J and K excitations for a modulo-8 counter.

Present state Q ₂ Q ₁ Q ₀	Next state Q ₂ ⁺ Q ₁ ⁺ Q ₀ ⁺	Excitations					
		J ₂	K ₂	J ₁	K ₁	J ₀	K ₀
0 0 0	0 0 1	0	d	0	d	1	d
0 0 1	0 1 0	0	d	1	d	d	1
0 1 0	0 1 1	0	d	d	0	1	d
0 1 1	1 0 0	1	d	d	1	d	1
1 0 0	1 0 1	d	0	0	d	1	d
1 0 1	1 1 0	d	0	1	d	d	1
1 1 0	1 1 1	d	0	d	0	1	d
1 1 1	0 0 0	d	1	d	1	d	1

Table 10.11 J and K excitations for a modulo-8 counter.

Present state $Q_2Q_1Q_0$	Next state $Q_2^+Q_1^+Q_0^+$	Excitations			
		J_2 K_2	J_1 K_1	J_0 K_0	
0 0 0	0 0 1	0 d	0 d	1 d	
0 0 1	0 1 0	0 d	1 d	d 1	
0 1 0	0 1 1	0 d	d 0	1 d	
0 1 1	1 0 0	1 d	d 1	d 1	
1 0 0	1 0 1	d 0	0 d	1 d	
1 0 1	1 1 0	d 0	1 d	d 1	
1 1 0	1 1 1	d 0	d 0	1 d	
1 1 1	0 0 0	d 1	d 1	d 1	

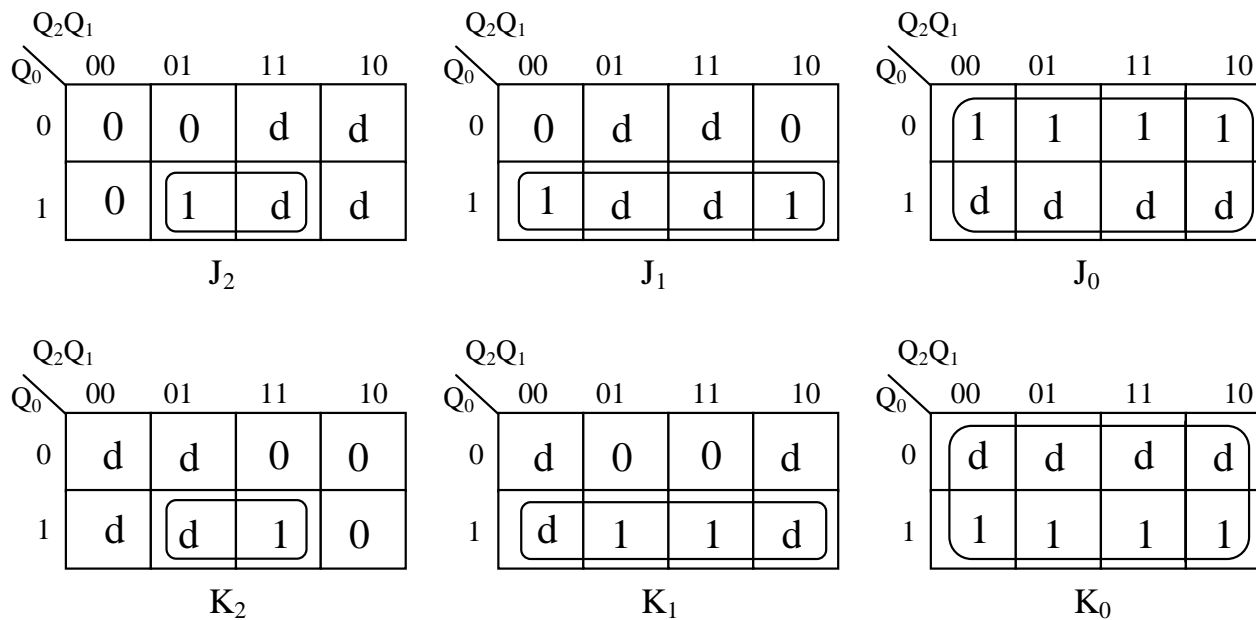


Figure 10.17 K-maps for excitation functions.

$$J_2 = Q_1Q_0$$

$$K_2 = Q_1Q_0$$

$$J_1 = Q_0$$

$$K_1 = Q_0$$

$$J_0 = 1$$

$$K_0 = 1$$

Design with JK Flip-Flops by Partition

Shannon's expansion theorem

$$\begin{aligned} & Q_i^+(Q_{n-1}, Q_{n-2}, \dots, Q_i, \dots, Q_1, Q_0, X_{m-1}, X_{m-2}, \dots, X_1, X_0) \\ &= Q_i' \bullet Q_i^+(Q_{n-1}, Q_{n-2}, \dots, Q_i = 0, \dots, Q_1, Q_0, X_{m-1}, X_{m-2}, \dots, X_1, X_0) \\ &\quad + Q_i \bullet Q_i^+(Q_{n-1}, Q_{n-2}, \dots, Q_i = 1, \dots, Q_1, Q_0, X_{m-1}, X_{m-2}, \dots, X_1, X_0) \end{aligned}$$

$$Q_i^+ = J_i Q_i' + K_i' Q_i$$

$$J_i = Q_i^+(Q_{n-1}, Q_{n-2}, \dots, Q_i = 0, \dots, Q_1, Q_0, X_{m-1}, X_{m-2}, \dots, X_1, X_0) = (Q_i^+)_{Q_i = 0}$$

$$K_i' = Q_i^+(Q_{n-1}, Q_{n-2}, \dots, Q_i = 1, \dots, Q_1, Q_0, X_{m-1}, X_{m-2}, \dots, X_1, X_0) = (Q_i^+)_{Q_i = 1}$$

Binary Tree


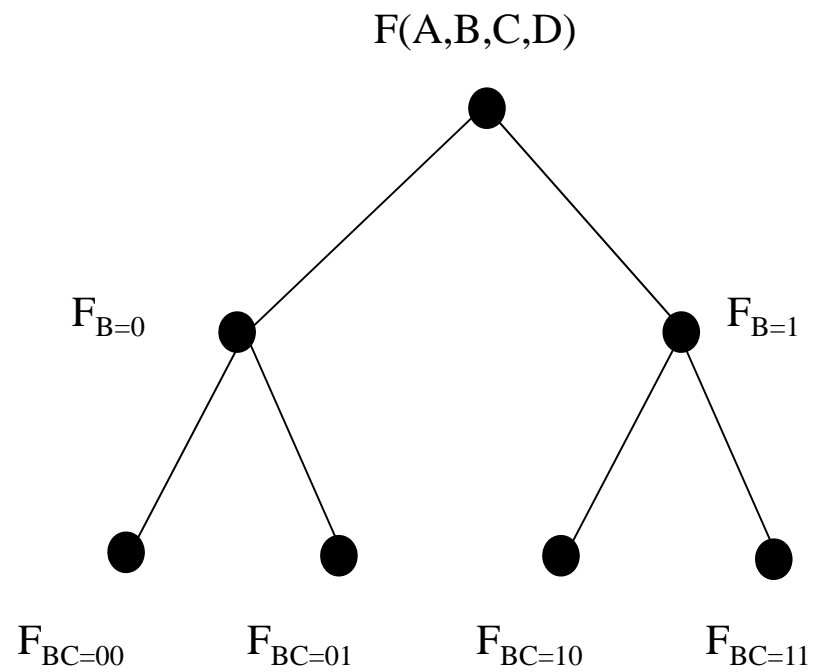


Figure 4.3 A binary tree for the expansion of a Boolean function.

Binary Tree

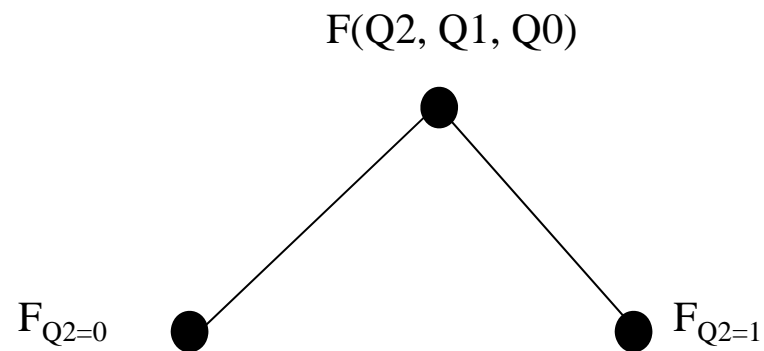

$$F = Q_2' F_{Q_2=0} + Q_2 F_{Q_2=1}$$

$$F = J_2 Q_2' + K_2' Q_2$$

$$J_2 = F_{Q_2=0} \quad K_2 = (F_{Q_2=1})'$$

Design with JK Flip-Flops by Partition

$$J_i = Q_i^+(Q_{n-1}, Q_{n-2}, \dots, Q_i = 0, \dots, Q_1, Q_0, x_{m-1}, x_{m-2}, \dots, x_1, x_0) = (Q_i^+)_{Q_i=0}$$

$$K_i' = Q_i^+(Q_{n-1}, Q_{n-2}, \dots, Q_i = 1, \dots, Q_1, Q_0, x_{m-1}, x_{m-2}, \dots, x_1, x_0) = (Q_i^+)_{Q_i=1}$$

From the next state equations of the modulo-8 counter, which are

$$Q_2^+ = (Q_1 Q_0) \oplus Q_2$$

$$Q_1^+ = Q_1 \oplus Q_0$$

$$Q_0^+ = Q_0'$$

the excitation functions can be obtained as follows:

$$J_2 = (Q_2^+)_{Q_2=0} = (Q_1 Q_0) \oplus 0 = Q_1 Q_0$$

$$K_2 = [(Q_2^+)_{Q_2=1}]' = [(Q_1 Q_0) \oplus 1]' = Q_1 Q_0$$

$$J_1 = (Q_1^+)_{Q_1=0} = 0 \oplus Q_0 = Q_0$$

$$K_1 = [(Q_1^+)_{Q_1=1}]' = (1 \oplus Q_0)' = Q_0$$

$$J_0 = (Q_0^+)_{Q_0=0} = 0' = 1$$

$$K_0 = [(Q_0^+)_{Q_0=1}]' = (1')' = 1$$




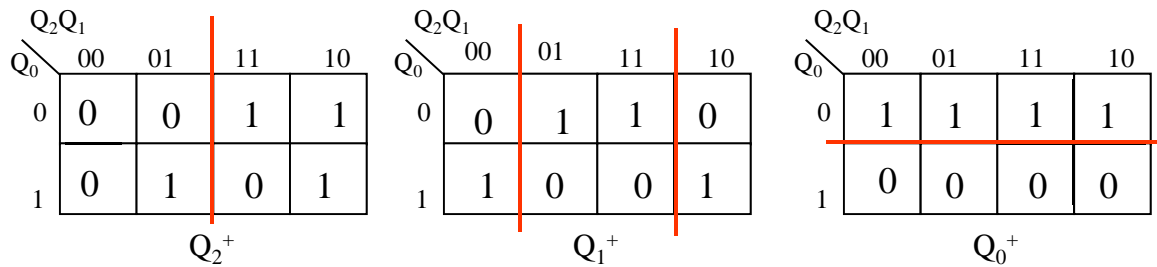
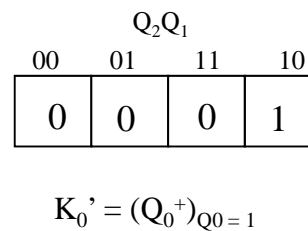
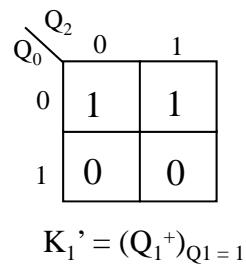
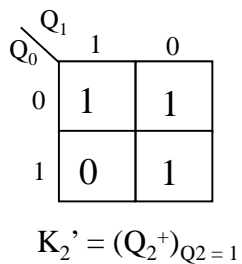
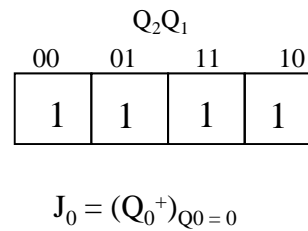
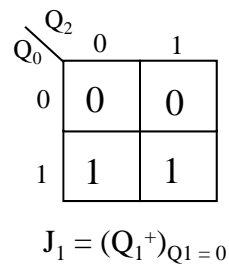
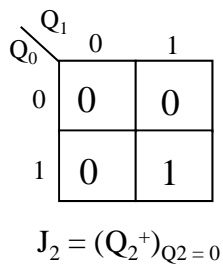


Figure 10.15 Next-state maps for a modulo-8 counter.

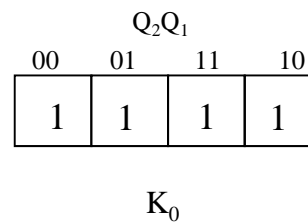
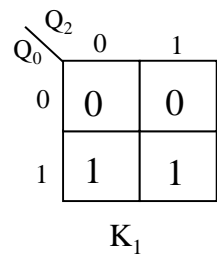
$$\begin{aligned} J_2 &= K_2 = Q_1 Q_0 \\ J_1 &= K_1 = Q_0 \\ J_0 &= K_0 = 1 \end{aligned}$$



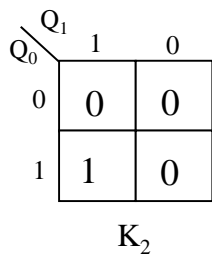

Design with T flip-flops

Table 10.12 Excitation table for T flip-flops.

Q	Q ⁺	T	Function
0	0	0	No change
0	1	1	Toggled
1	0	1	Toggled
1	1	0	No change

$$T = Q \oplus Q^+$$

$$T_2 = Q_2 \oplus Q_2^+ = Q_2 \oplus (Q_1 Q_0) \oplus Q_2 = Q_1 Q_0$$

$$T_1 = Q_1 \oplus Q_1^+ = Q_1 \oplus Q_1 \oplus Q_0 = Q_0$$

$$T_0 = Q_0 \oplus Q_0^+ = Q_0 \oplus Q_0' = 1$$

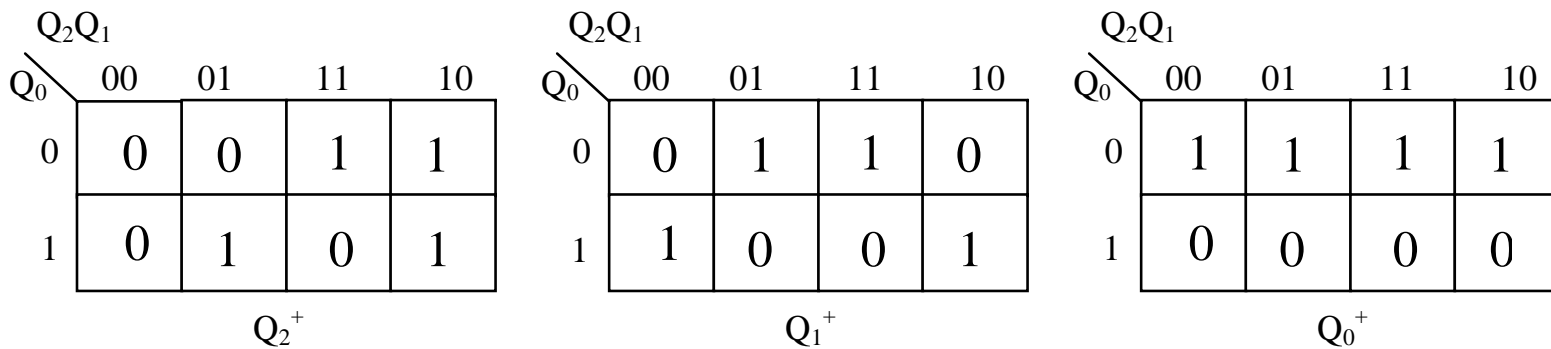


Figure 10.15 Next-state maps for a modulo-8 counter.

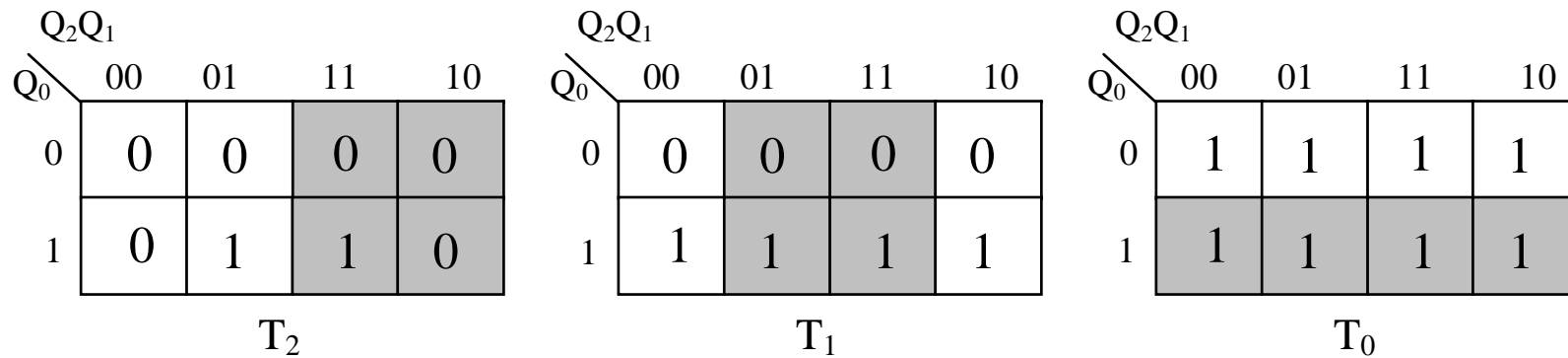


Figure 10.19 K-maps for the excitations of T flip-flops.

$$T_2 = Q_2 \oplus Q_2^+ = Q_2 \oplus (Q_1 Q_0) \oplus Q_2 = Q_1 Q_0$$

$$T_1 = Q_1 \oplus Q_1^+ = Q_1 \oplus Q_1 \oplus Q_0 = Q_0$$

$$T_0 = Q_0 \oplus Q_0^+ = Q_0 \oplus Q_0' = 1$$

10.4.2 Self-Correcting Counter

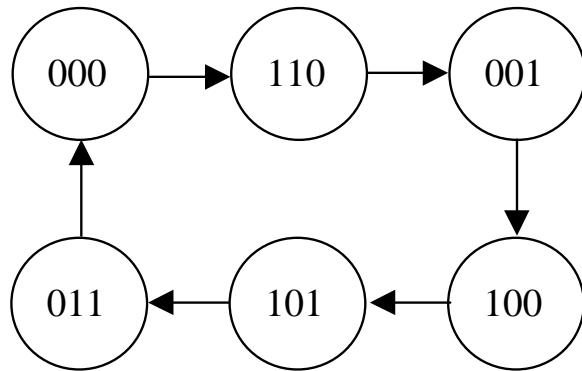


Figure 10.21 State diagram for a 6-state self-correcting counter.

Table 10.13 Transition table for a 6-state self-correcting counter.

Present state $Q_2Q_1Q_0$	Next state $Q_2^+Q_1^+Q_0^+$
0 0 0	1 1 0
0 0 1	1 0 0
0 1 0	d d d
0 1 1	0 0 0
1 0 0	1 0 1
1 0 1	0 1 1
1 1 0	0 0 1
1 1 1	d d d

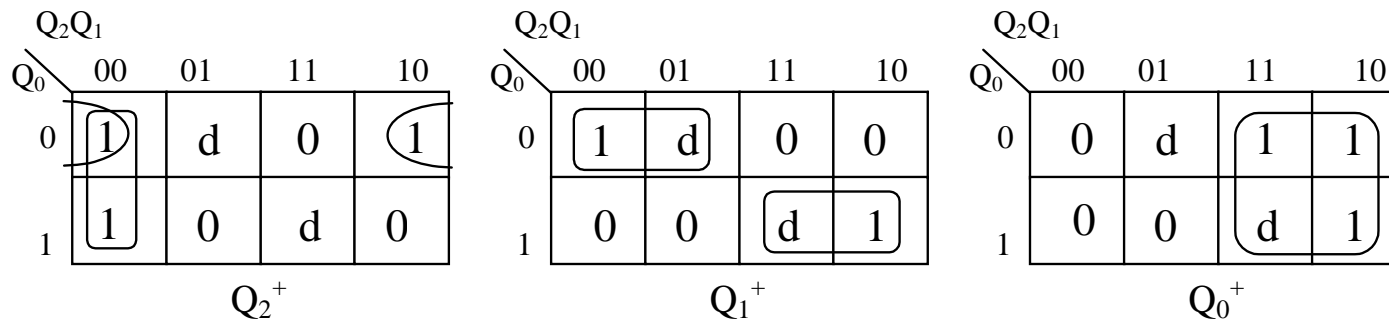


Figure 10.22 Next-state maps for the 6-state self-correcting counter.

$$\begin{aligned}
 D_2 = Q_2^+ &= Q_2'Q_1' + Q_1'Q_0' \\
 D_1 = Q_1^+ &= Q_2'Q_0' + Q_2Q_0 = (Q_2 \oplus Q_0)' \\
 D_0 = Q_0^+ &= Q_2
 \end{aligned}$$

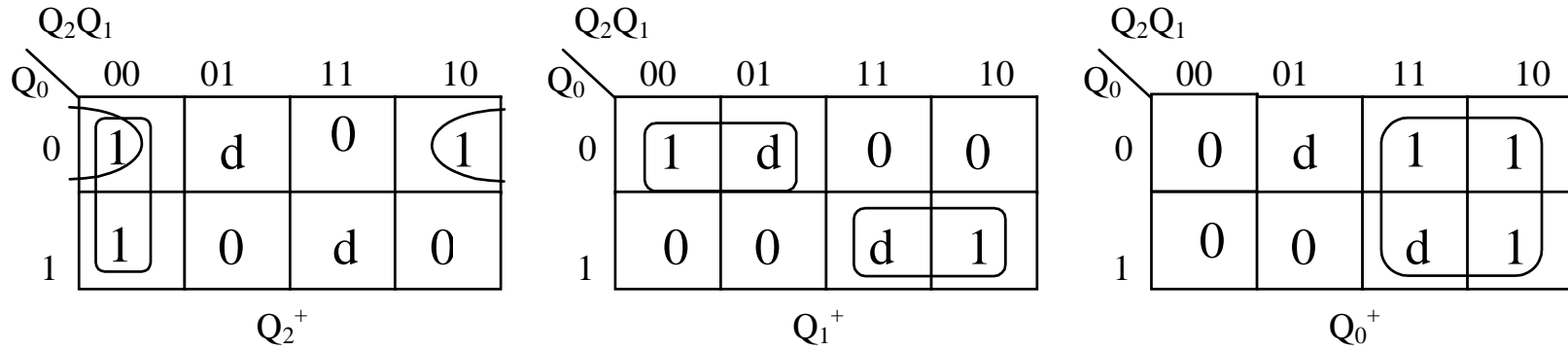


Figure 10.22 Next-state maps for the 6-state self-correcting counter.

$$\begin{aligned}
 D_2 = Q_2^+ &= Q_2'Q_1' + Q_1'Q_0' \\
 D_1 = Q_1^+ &= Q_2'Q_0' + Q_2Q_0 = (Q_2 \oplus Q_0)' \\
 D_0 = Q_0^+ &= Q_2
 \end{aligned}$$

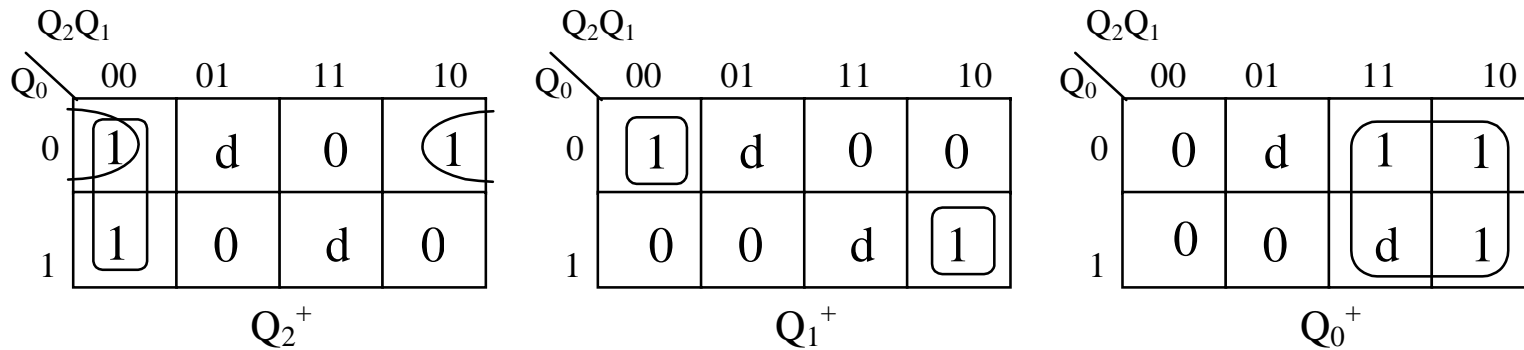


Figure 10.23 Re-design of the 6-state self-correcting counter.

$$D_1 = Q_1^+ = Q_2'Q_1'Q_0' + Q_2Q_1'Q_0 = Q_1'(Q_2 \oplus Q_0)'$$

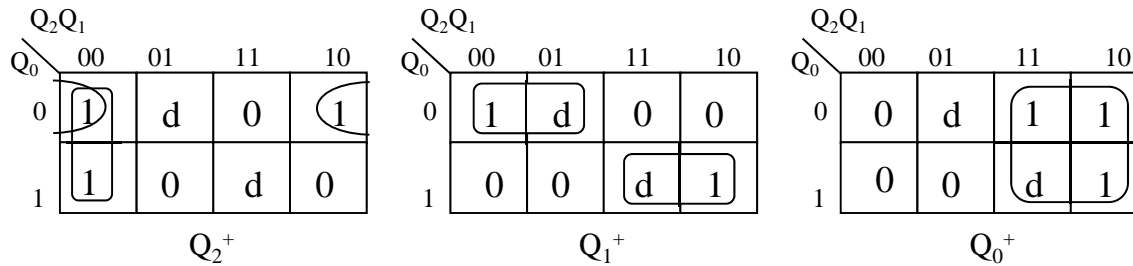


Figure 10.22 Next-state maps for the 6-state self-correcting counter.

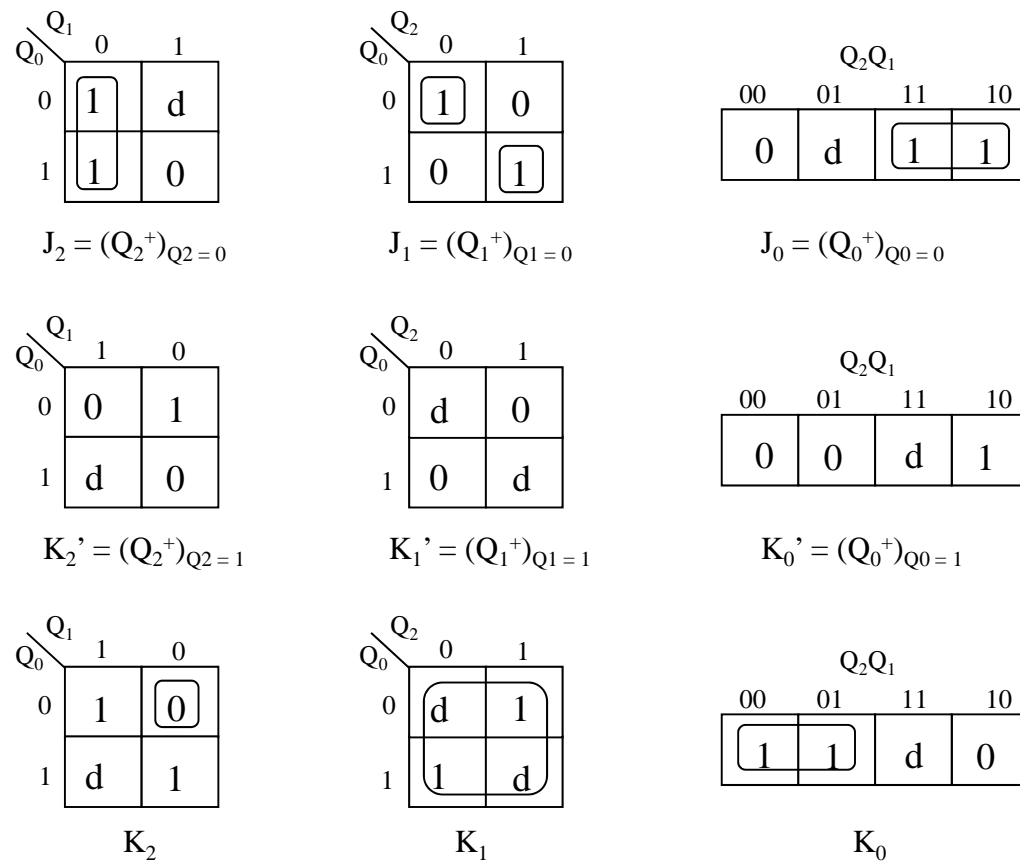


Figure 10.24 K-maps for JK excitations.

$Q_0 \backslash Q_1$	0	1
0	1	d
1	1	0

$$J_2 = (Q_2^+)_{Q_2=0}$$

$Q_0 \backslash Q_2$	0	1
0	1	0
1	0	1

$$J_1 = (Q_1^+)_{Q_1=0}$$

$Q_2 Q_1$			
00	01	11	10
0	d	1	1

$$J_0 = (Q_0^+)_{Q_0=0}$$

$Q_0 \backslash Q_1$	1	0
0	0	1
1	d	0

$$K_2' = (Q_2^+)_{Q_2=1}$$

$Q_0 \backslash Q_2$	0	1
0	d	0
1	0	d

$$K_1' = (Q_1^+)_{Q_1=1}$$

$Q_2 Q_1$			
00	01	11	10
0	0	d	1

$$K_0' = (Q_0^+)_{Q_0=1}$$

$Q_0 \backslash Q_1$	1	0
0	1	0
1	d	1

$$K_2$$

$Q_0 \backslash Q_2$	0	1
0	d	1
1	1	d

$$K_1$$

$Q_2 Q_1$			
00	01	11	10
1	1	d	0

$$K_0$$

Figure 10.24 K-maps for JK excitations.

$$Q_2^+ = J_2 Q_2' + K_2' Q_2 = Q_1' Q_2' + (Q_1 + Q_0)' Q_2 = Q_2' Q_1' + Q_2 Q_1' Q_0'$$

$$Q_1^+ = J_1 Q_1' + K_1' Q_1 = (Q_2 \oplus Q_0)' Q_1' + (1)' Q_1 = Q_2' Q_1' Q_0' + Q_2 Q_1' Q_0$$

$$Q_0^+ = J_0 Q_0' + K_0' Q_0 = Q_2 Q_0' + Q_2 Q_0 = Q_2$$

Up-Down Counter

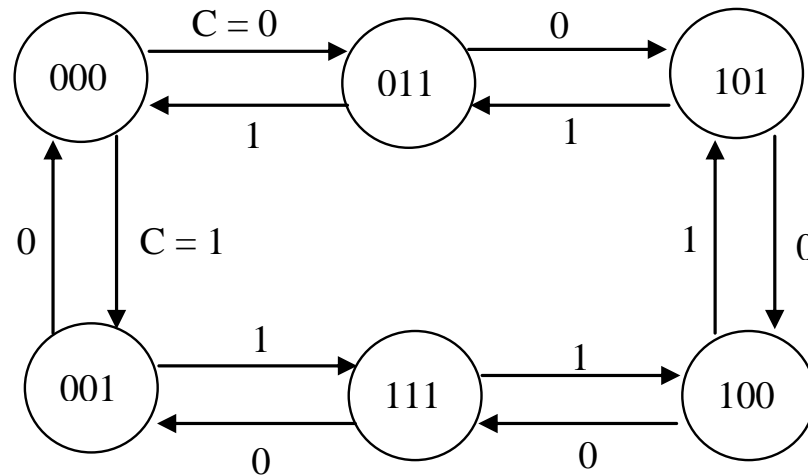


Figure 10.25 State diagram for a 6-state up-down counter.

Table 10.14 Transition table for a 6-state up-down counter.

Present state $Q_2Q_1Q_0$	Next state $Q_2^+Q_1^+Q_0^+$	
	$C = 0$	$C = 1$
0 0 0	0 1 1	0 0 1
0 0 1	0 0 0	1 1 1
0 1 0	d d d	d d d
0 1 1	1 0 1	0 0 0
1 0 0	1 1 1	1 0 1
1 0 1	1 0 0	0 1 1
1 1 0	d d d	d d d
1 1 1	0 0 1	1 0 0

Table 10.14 Transition table for a 6-state up-down counter.

Present state $Q_2Q_1Q_0$	Next state $Q_2^+Q_1^+Q_0^+$	
	$C = 0$	$C = 1$
0 0 0	0 1 1	0 0 1
0 0 1	0 0 0	1 1 1
0 1 0	d d d	d d d
0 1 1	1 0 1	0 0 0
1 0 0	1 1 1	1 0 1
1 0 1	1 0 0	0 1 1
1 1 0	d d d	d d d
1 1 1	0 0 1	1 0 0

Q_2Q_1 CQ_0					Q_2Q_1 CQ_0					Q_2Q_1 CQ_0				
	00	01	11	10		00	01	11	10		00	01	11	10
00	0	d	d	1	00	1	d	d	1	00	1	d	d	1
01	0	1	0	1	01	0	0	0	0	01	0	1	1	0
11	1	0	1	0	11	1	0	0	1	11	1	0	0	1
10	0	d	d	1	10	0	d	d	0	10	1	d	d	1
Q_2^+					Q_1^+					Q_0^+				

Figure 10.26 Next-state maps for a 6-state up-down counter.

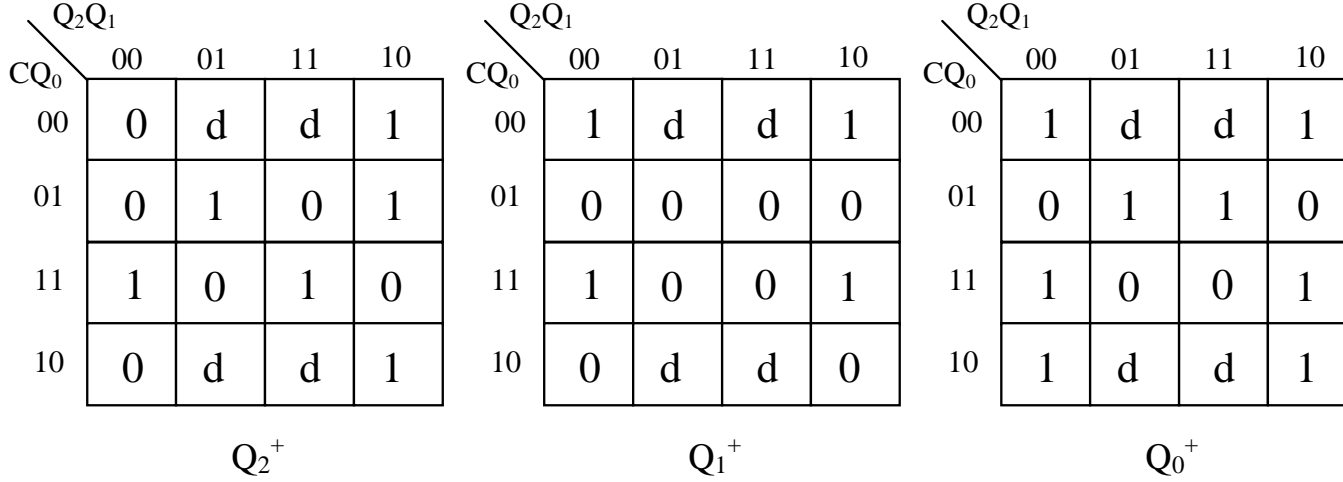


Figure 10.26 Next-state maps for a 6-state up-down counter.

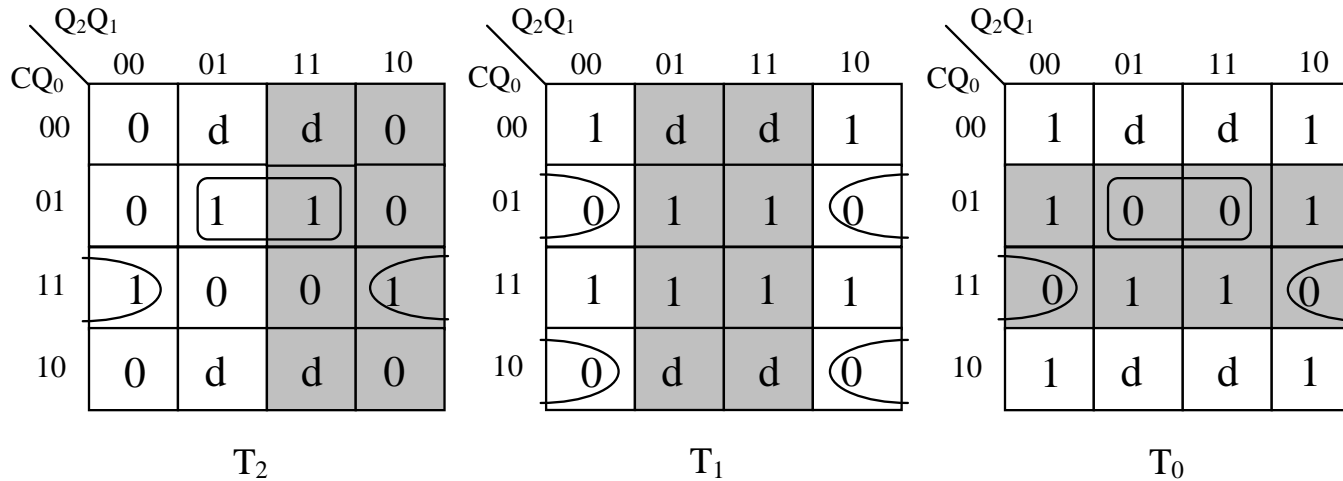


Figure 10.27 T excitations for the 6-state up-down counter in Figure 10.25.

$$T_2 = C'Q_1Q_0 + CQ_1'Q_0 = Q_0(C \oplus Q_1)$$

$$T_1 = (C + Q_1 + Q_0')(C' + Q_1 + Q_0) = Q_1 + (C \oplus Q_0)'$$

$$Q_2Q_1Q_0 = 010$$


$$Q_2^+Q_1^+Q_0^+ = 001$$


$$Q_2Q_1Q_0 = 110$$

$$Q_2^+Q_1^+Q_0^+ = 101$$



State
assignments

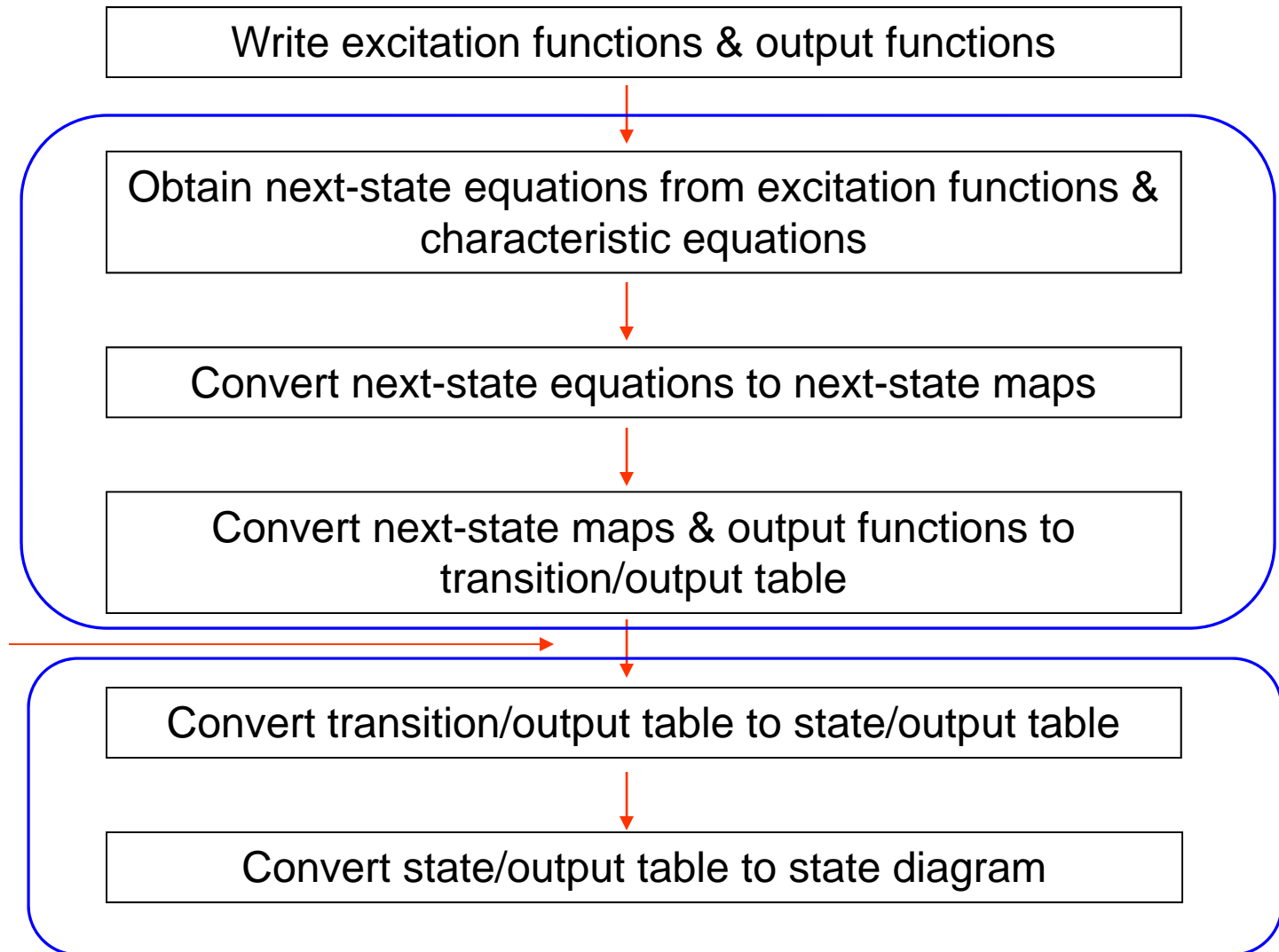

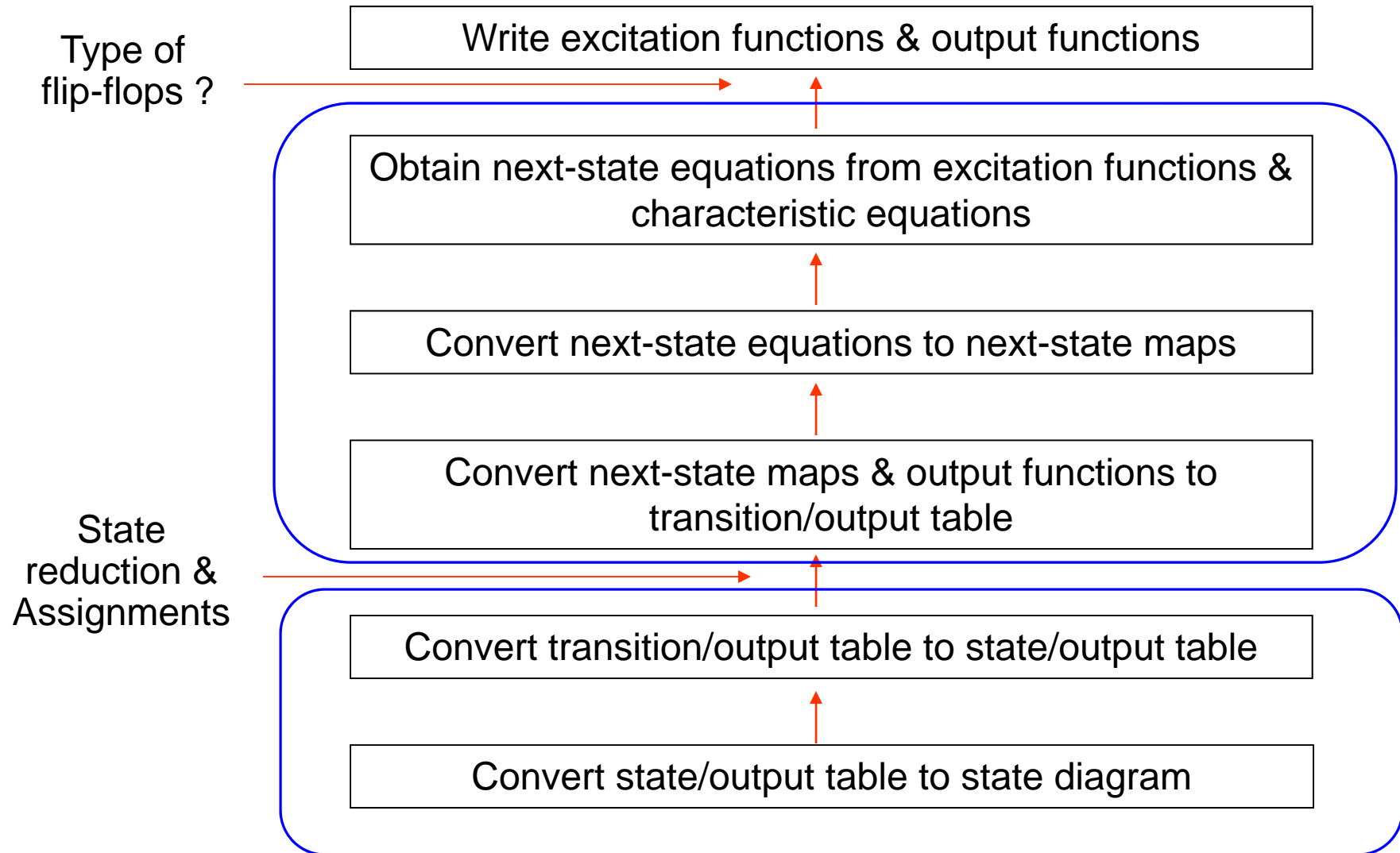




Bit sequence detector /recognizer to detect a 3-bit sequence 101.
Output Z = 1 when sequence is detected.

Moore model - Non-overlapping 001010100101

Mealy model - Non-overlapping

Moore model – Overlapping 001010100101

Mealy model - Overlapping

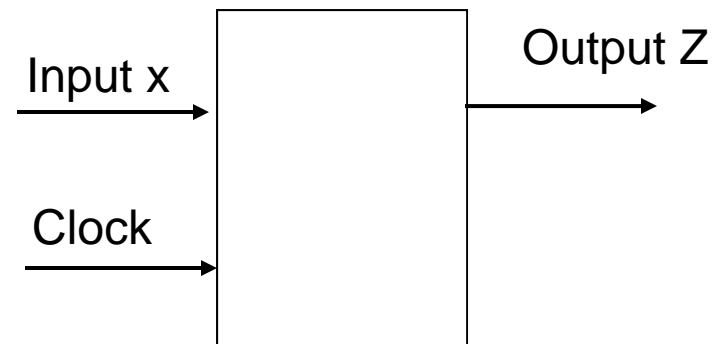



10.4.3 Design of Bit-Sequence Detector

Moore model

Table 10.15 Sample sequences of input and output for a Moore bit-sequence detector.

Clock cycle	1	2	3	4	5	6	7	8	9	10	11	12	13	14	15
Input x	1	1	0	0	1	0	1	0	1	0	1	1	0	1
Output Z	0	0	0	0	0	0	0	1	0	0	0	1	0	0	1

Condition A: Nothing has been detected, not even the first bit of the sequence.

Condition B: The first bit, 1, has been detected.

Condition C: The first two bits, 10, have been detected.

Condition D: All three bits, 101, have been detected.



Condition A: Nothing has been detected, not even the first bit of the sequence.
Condition B: The first bit, 1, has been detected.
Condition C: The first two bits, 10, have been detected.
Condition D: All three bits, 101, have been detected.

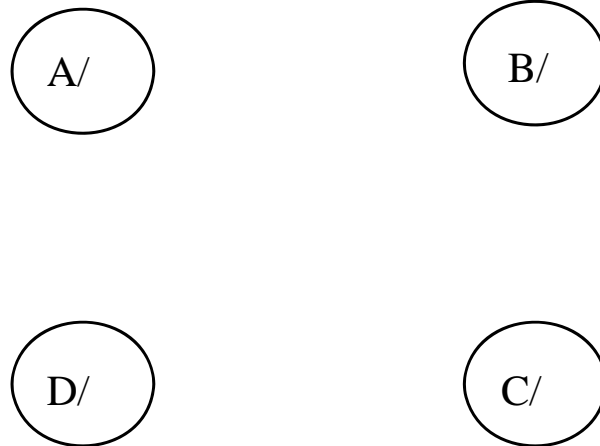


Figure 10.28 State diagram for a circuit of Moore model to detect 101.

- Condition A: Nothing has been detected, not even the first bit of the sequence.
Condition B: The first bit, 1, has been detected.
Condition C: The first two bits, 10, have been detected.
Condition D: All three bits, 101, have been detected.

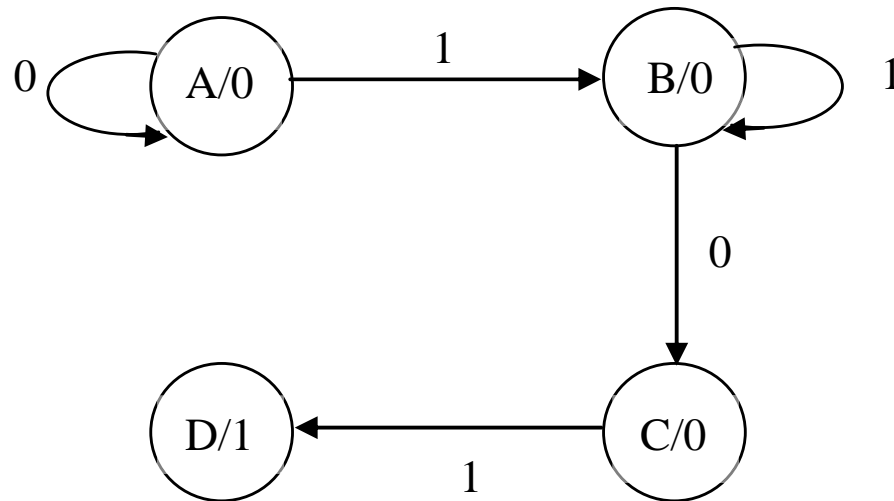


Figure 10.28 State diagram for a circuit of Moore model to detect 101.

- Condition A: Nothing has been detected, not even the first bit of the sequence.
Condition B: The first bit, 1, has been detected.
Condition C: The first two bits, 10, have been detected.
Condition D: All three bits, 101, have been detected.

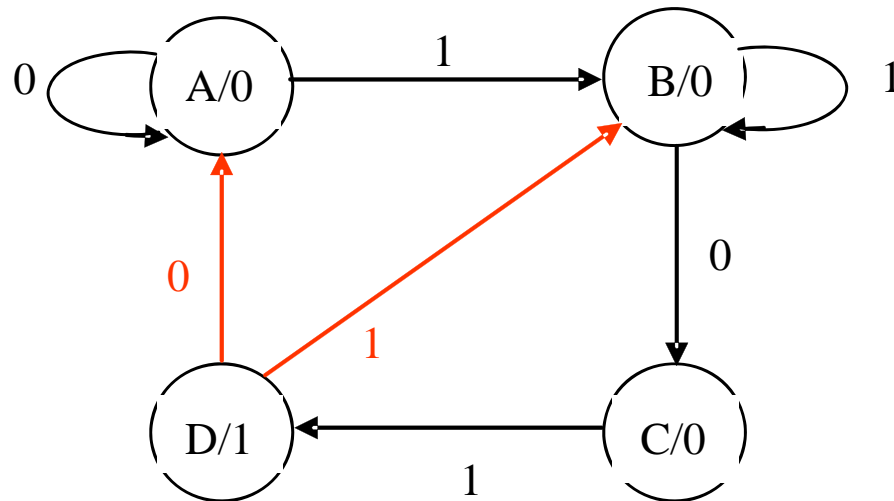


Figure 10.28 State diagram for a circuit of Moore model to detect 101.

- Condition A: Nothing has been detected, not even the first bit of the sequence.
Condition B: The first bit, 1, has been detected.
Condition C: The first two bits, 10, have been detected.
Condition D: All three bits, 101, have been detected.

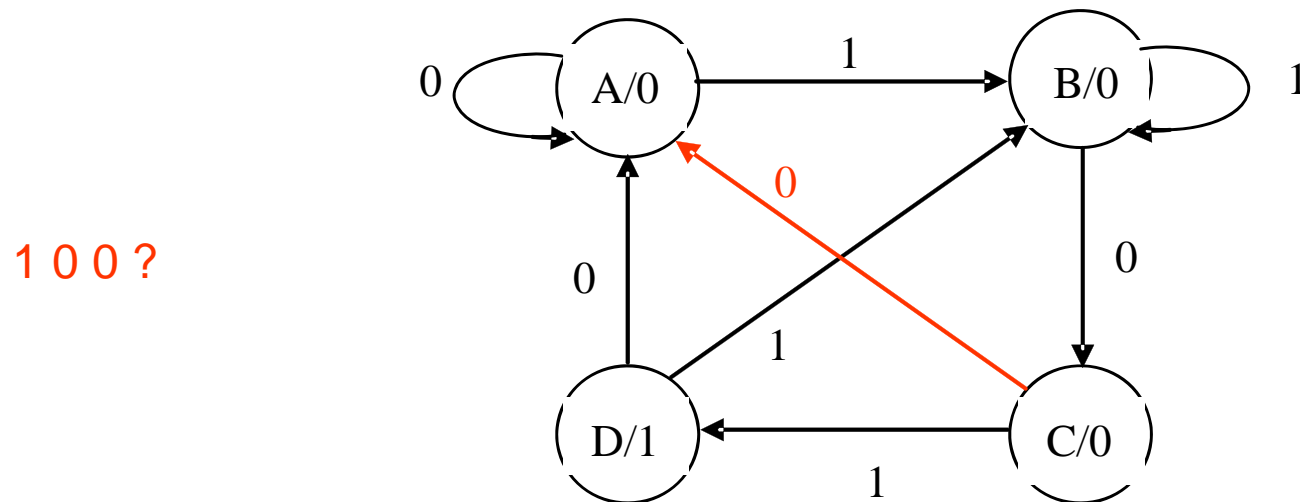


Figure 10.28 State diagram for a circuit of Moore model to detect 101.

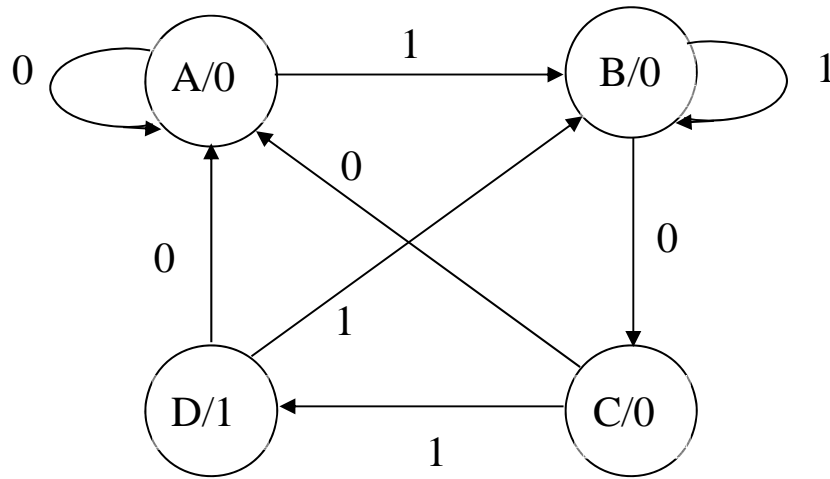


Table 10.16 State/output table for bit sequence detector.

Present state	Next state		Z
	x = 0	x = 1	
A	A	B	0
B	C	B	0
C	A	D	0
D	A	B	1

Table 10.16 State/output table for bit sequence detector.

Present state	Next state		Z	
	x = 0	x = 1		
A	A	B	0	A
B	C	B	0	B
C	A	D	0	C
D	A	B	1	D

Table 10.17 Transition/output table for bit sequence detector.

Q_2Q_1	$Q_2^+ Q_1^+$		Z
	x = 0	x = 1	
00	00	01	0
01	11	01	0
11	00	10	0
10	00	01	1

		Q_2Q_1			
		00	01	11	10
x	0	0	1	0	0
	1	0	0	1	0

Q_2^+

		Q_2Q_1			
		00	01	11	10
x	0	0	1	0	0
	1	1	1	0	1

Q_1^+

Figure 10.29 Next-state maps and the partition for excitations.

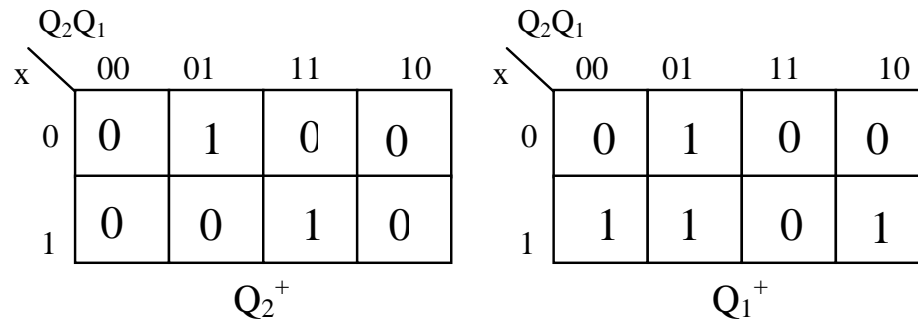


Figure 10.29 Next-state maps and the partition for excitations.

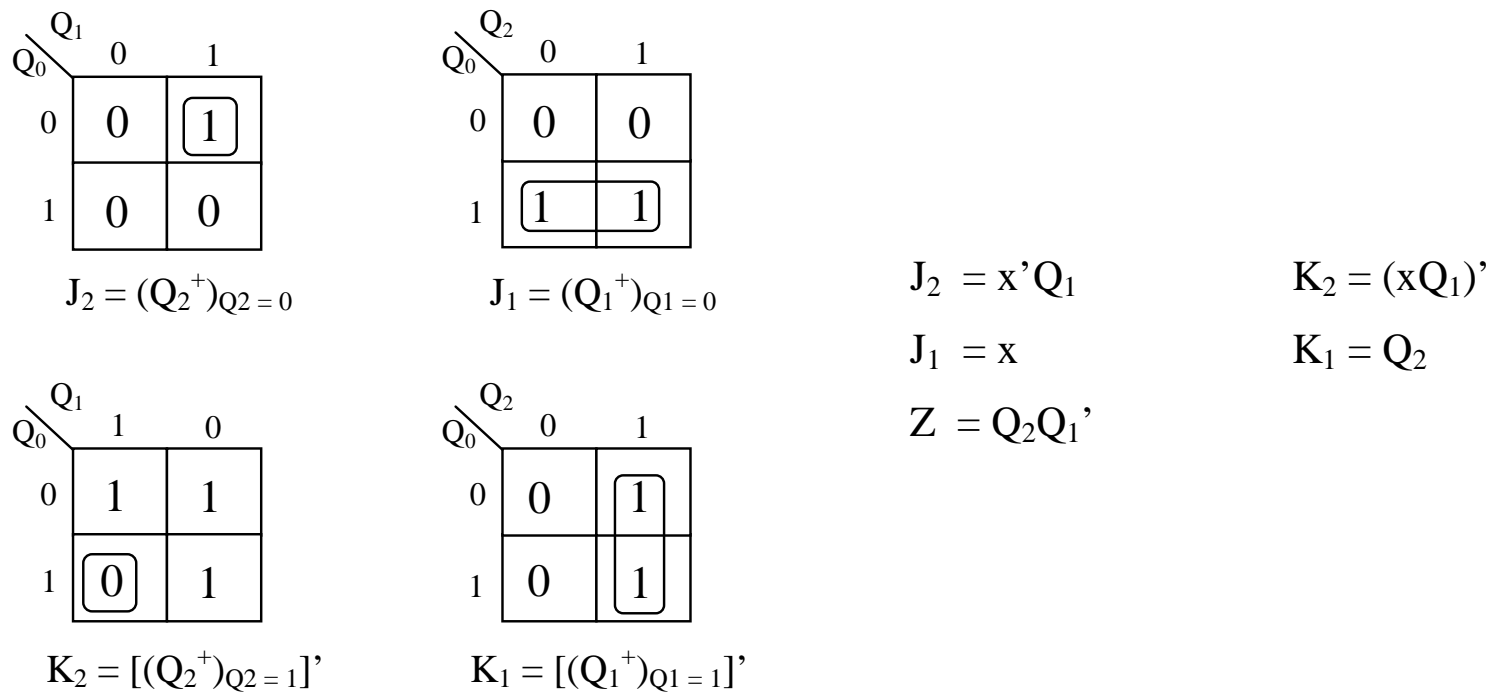


Figure 10.30 K-maps for the excitations of the bit sequence detector.

$$J_2 = x'Q_1 \quad K_2 = (xQ_1)' \quad J_1 = x \quad K_1 = Q_2 \quad Z = Q_2Q_1'$$

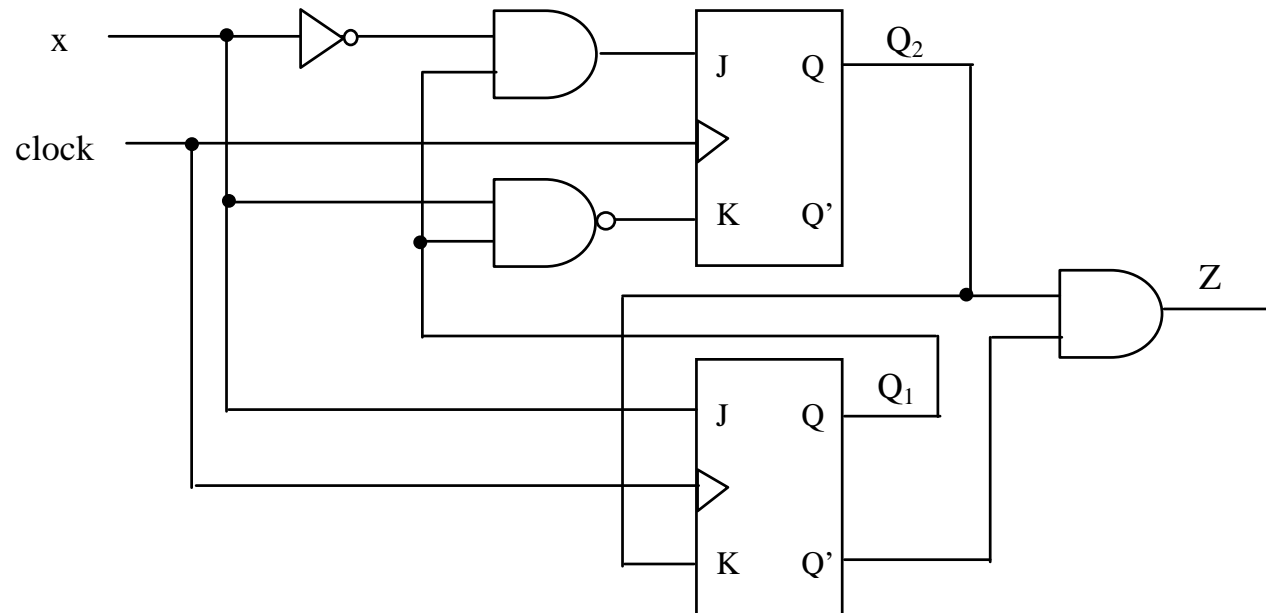


Figure 10.31 Sequential circuit of Moore model to detect a sequence of 101.

Mealy model

Table 10.18 Sample sequences of input and output for a Mealy bit-sequence detector.

Clock cycle	1	2	3	4	5	6	7	8	9	10	11	12	13	14	15
Input x	1	1	0	0	1	0	1	0	1	0	1	1	0	1
Output Z	0	0	0	0	0	0	1	0	0	0	1	0	0	1

Condition A: Nothing has been detected, not even the first bit of the sequence.

Condition B: The first bit, 1, has been detected.

Condition C: The first two bits, 10, have been detected. If present input $x = 0$, $Z = 0$. If $x = 1$, $Z = 1$.

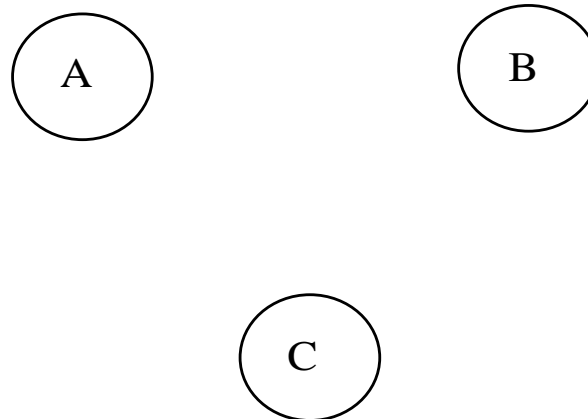


Figure 10.32 State diagram for a circuit of Mealy model to detect 101.

Mealy model

Table 10.18 Sample sequences of input and output for a Mealy bit-sequence detector.

Clock cycle	1	2	3	4	5	6	7	8	9	10	11	12	13	14	15
Input x	1	1	0	0	1	0	1	0	1	0	1	1	0	1
Output Z	0	0	0	0	0	0	1	0	0	0	1	0	0	1

Condition A: Nothing has been detected, not even the first bit of the sequence.

Condition B: The first bit, 1, has been detected.

Condition C: The first two bits, 10, have been detected. If present input $x = 0$, $Z = 0$. If $x = 1$, $Z = 1$.

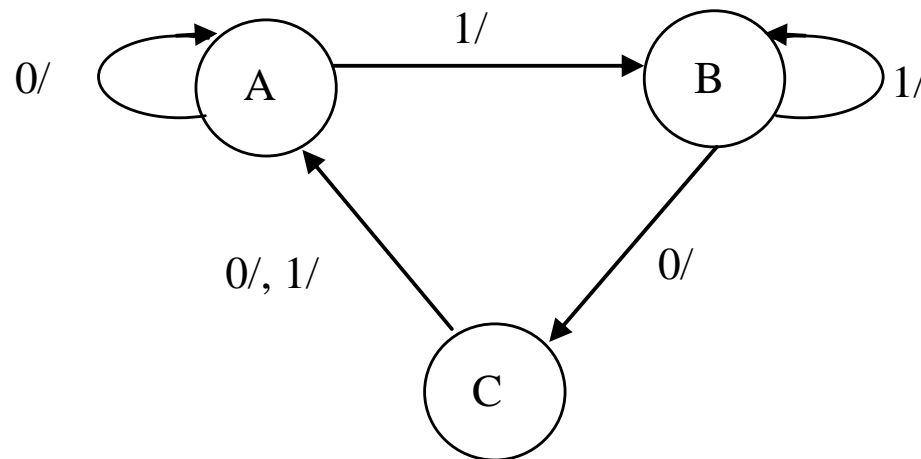


Figure 10.32 State diagram for a circuit of Mealy model to detect 101.

Mealy model

Table 10.18 Sample sequences of input and output for a Mealy bit-sequence detector.

Clock cycle	1	2	3	4	5	6	7	8	9	10	11	12	13	14	15
Input x	1	1	0	0	1	0	1	0	1	0	1	1	0	1	...
Output Z	0	0	0	0	0	0	1	0	0	0	1	0	0	1	...

Condition A: Nothing has been detected, not even the first bit of the sequence.

Condition B: The first bit, 1, has been detected.

Condition C: The first two bits, 10, have been detected. If present input $x = 0$, $Z = 0$. If $x = 1$, $Z = 1$.

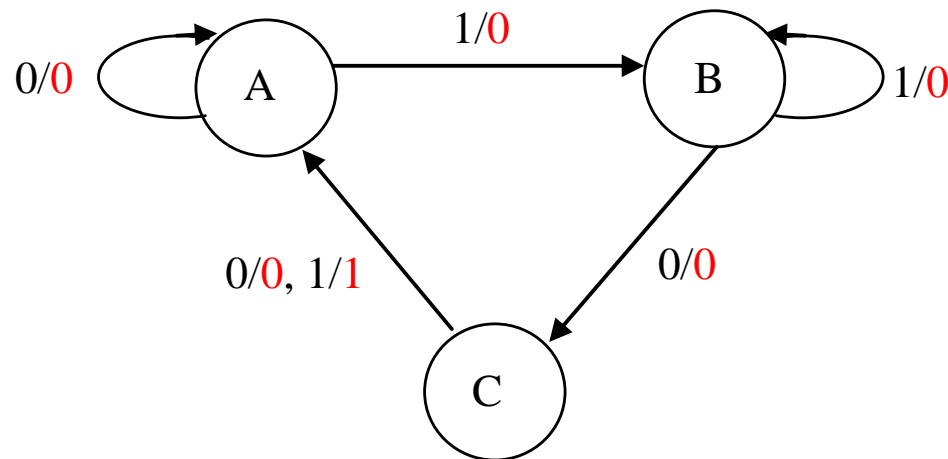


Figure 10.32 State diagram for a circuit of Mealy model to detect 101.

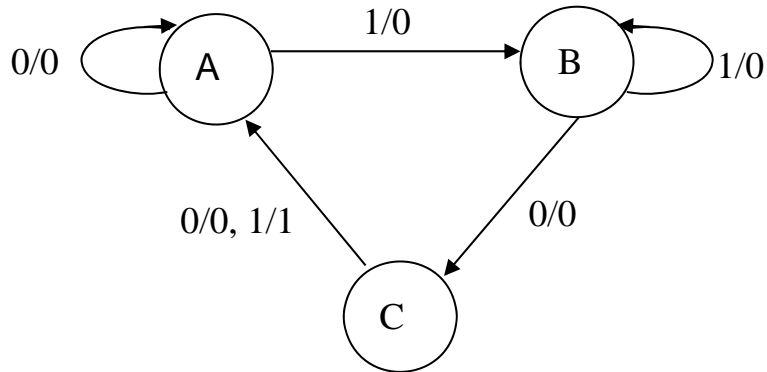


Table 10.19 State/output table for bit sequence detector.

Present state	Next state, Z	
	x = 0	x = 1
A	A, 0	B, 0
B	C, 0	B, 0
C	A, 0	A, 1

Table 10.20 Transition/output table for bit sequence detector.

Q_2Q_1	$Q_2^+ Q_1^+, Z$	
	x = 0	x = 1
A 00	00, 0	10, 0
B 10	11, 0	10, 0
C 11	00, 0	00, 1
01	d d, d	d d, d

Q_2Q_1		Q_2^+			
		00	01	11	10
x	0	0	d	0	1
	1	1	d	0	1

Q_2^+

Q_2Q_1		Q_1^+			
		00	01	11	10
x	0	0	d	0	1
	1	0	d	0	0

Q_1^+

Q_2Q_1		Z			
		00	01	11	10
x	0	0	d	0	0
	1	0	d	1	0

Z

Figure 10.33 Next-state maps and output K-map.

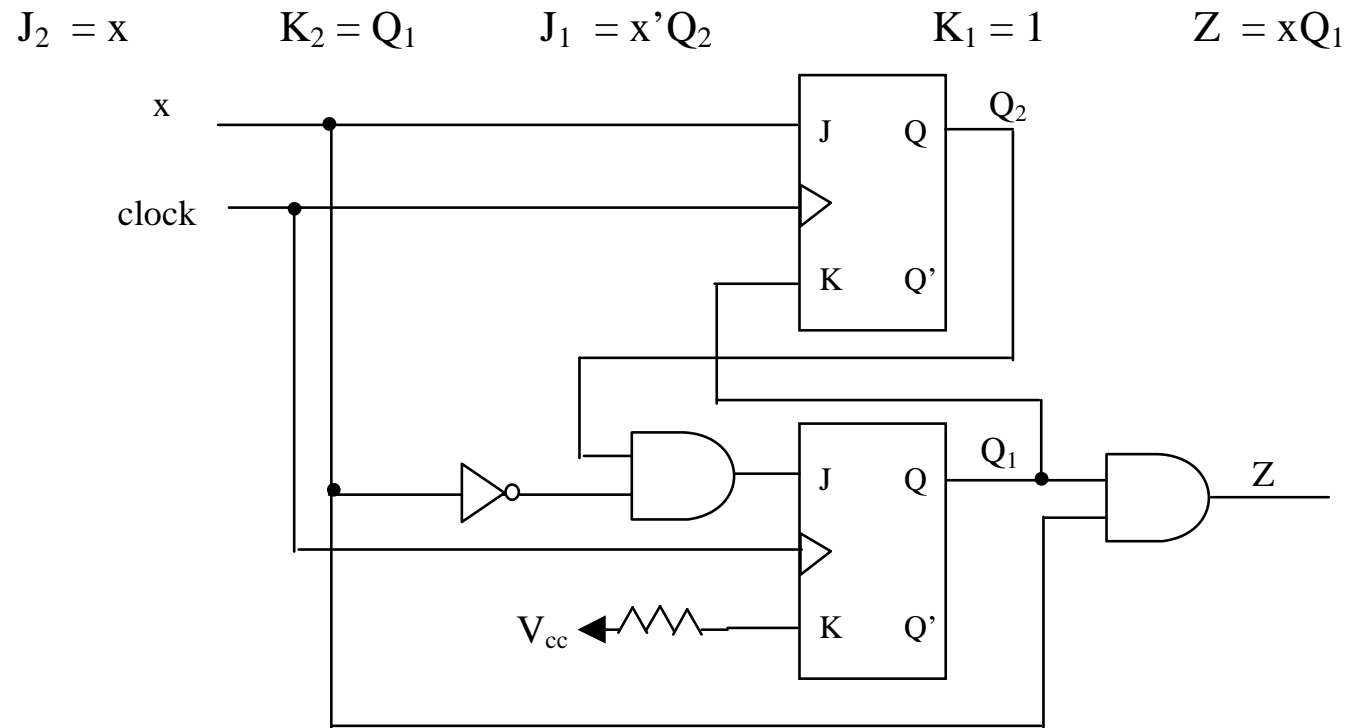


Figure 10.34 Sequential circuit of Mealy model to detect a sequence of 101.

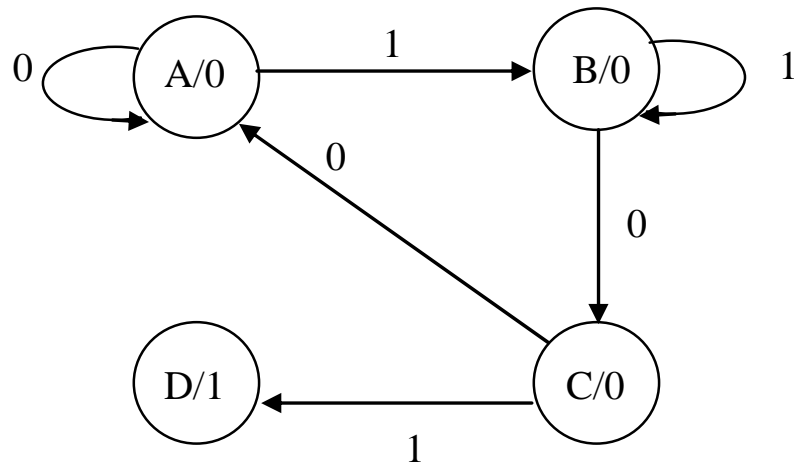


Figure 10.35 Moore model state diagram for overlapping sequences.

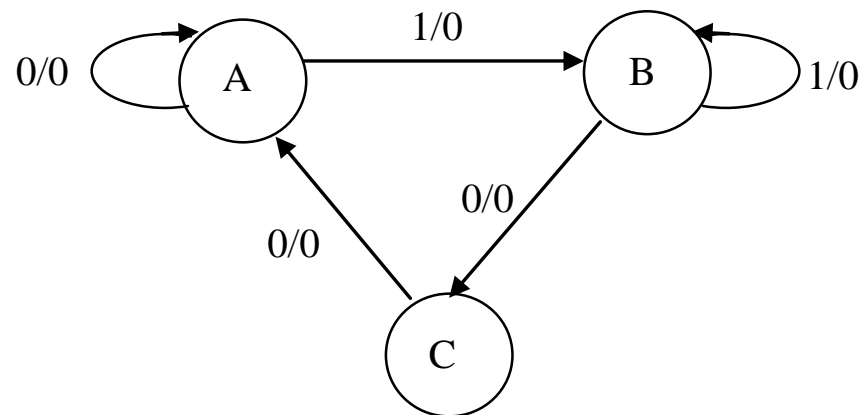


Figure 10.36 Mealy model state diagram for overlapping sequences.

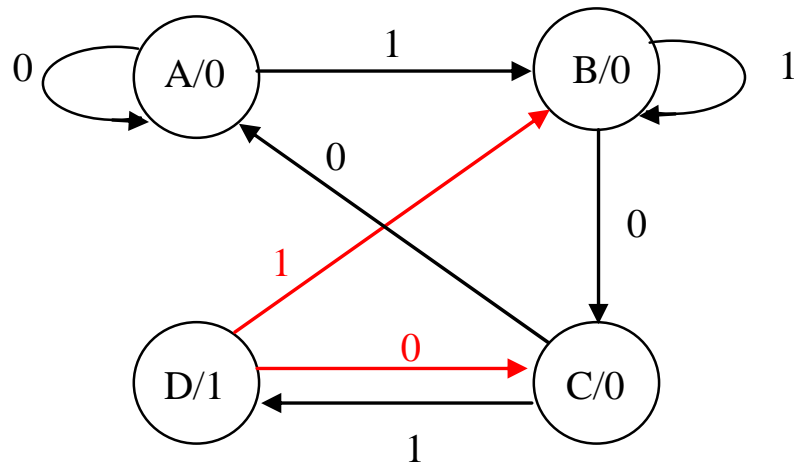


Figure 10.35 Moore model state diagram for overlapping sequences.

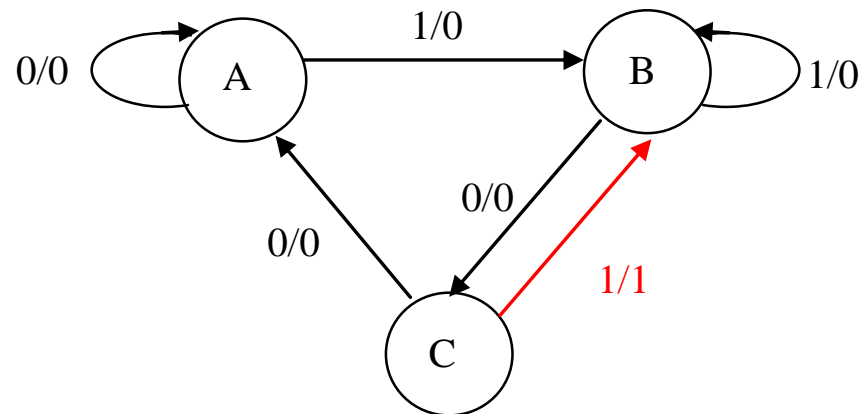


Figure 10.36 Mealy model state diagram for overlapping sequences.