

16.265	Logic Design
Student Logic Number	140
Name	Dangnhi Ngo
E-mail address (print)	Nhi_Ngo@student.uml.edu
Experiment Number	4
Date	11/27/2017


For grader use	
Schematic diagram submitted is different from the one in the report. (Need to re-submit the schematic diagram in the report or will be graded based on a maximum of 50 points.)	5 points deduction
Cannot open file	<u> </u>
File is not readable	<u> </u>
Date student is notified to re-submit a schematic file by e-mail	<u> </u>
Date schematic file received	<u> </u>

Report will be graded based on a maximum of 50 (out of 100 points) if a schematic diagram is not received within three calendar days of notification or the re-submitted schematic file still cannot be opened or is not readable.

Grade: 100

Experiment 4 Six-State Up-Down Counter

1. Sequence assignment

 

2. Next-state maps

Construction of transition table

Present state $Q_2 Q_1 Q_0$	Next state $Q_2^+ Q_1^+ Q_0^+$	
	$C = 0$	$C = 1$
0 0 0	0 0 1	1 1 0
0 0 1	0 1 1	0 0 0
0 1 0	d d d	d d d
0 1 1	1 0 0	0 0 1
1 0 0	1 1 1	0 1 1
1 0 1	d d d	d d d
1 1 0	0 0 0	1 1 1
1 1 1	1 1 0	1 0 0

Convert the transition table to next-state maps.

$Q_2 Q_1$ $C Q_0$	00	01	11	10
00	0	d	0	1
01	0	1	1	d
11	0	0	1	d
10	1	d	1	0

Q_2^+

$Q_2 Q_1$ $C Q_0$	00	01	11	10
00	0	d	0	1
01	1	0	1	d
11	0	0	0	d
10	1	d	1	1

Q_1^+

$Q_2 Q_1$ $C Q_0$	00	01	11	10
00	1	d	0	1
01	1	0	0	d
11	0	1	0	d
10	0	d	1	1

Q_0^+

3. Design using D flip-flops

Q_2Q_1	00	01	11	10	
CQ_0	00	0	d	0	1
01	0	1	1	d	
11	0	0	1	d	
10	1	d	1	0	

D_2

Q_2Q_1	00	01	11	10	
CQ_0	00	0	d	0	1
01	1	0	1	d	
11	0	0	0	d	
10	1	d	1	1	

D_1

Q_2Q_1	00	01	11	10	
CQ_0	00	1	d	0	1
01	1	0	0	d	
11	0	1	0	d	
10	0	d	1	1	

D_0

Determine the excitation functions from the next state maps.

$$D_2 = C'(Q_1Q_0 + Q_2Q_1') + C(Q_2Q_1 + Q_2'Q_0')$$


$$D_1 = CQ_0' + Q_2Q_1' + (Q_1' + Q_2)C'Q_0$$

$$D_0 = Q_1'Q_0' + (Q_2Q_0' + Q_2'Q_1)C$$

List of ICs and unused gates for design using D flip-flops









IC number	Type number	Function	Unused gates
1	7474	Dual D type flip-flops	None
2	7474	Dual D type flip-flops	1 D flip-flop
3	7400	2 Input NAND Gates	None
4	7400	2 Input NAND Gates	None
5	7400	2 Input NAND Gates	None
6	7400	2 Input NAND Gates	None
7	7410	3 Input NAND Gates	None
8			

 Simulation results for design using D flip-flops



Draw the schematic diagrams for the counter using D flip-flops.
Insert a complete schematic diagram including the title box.

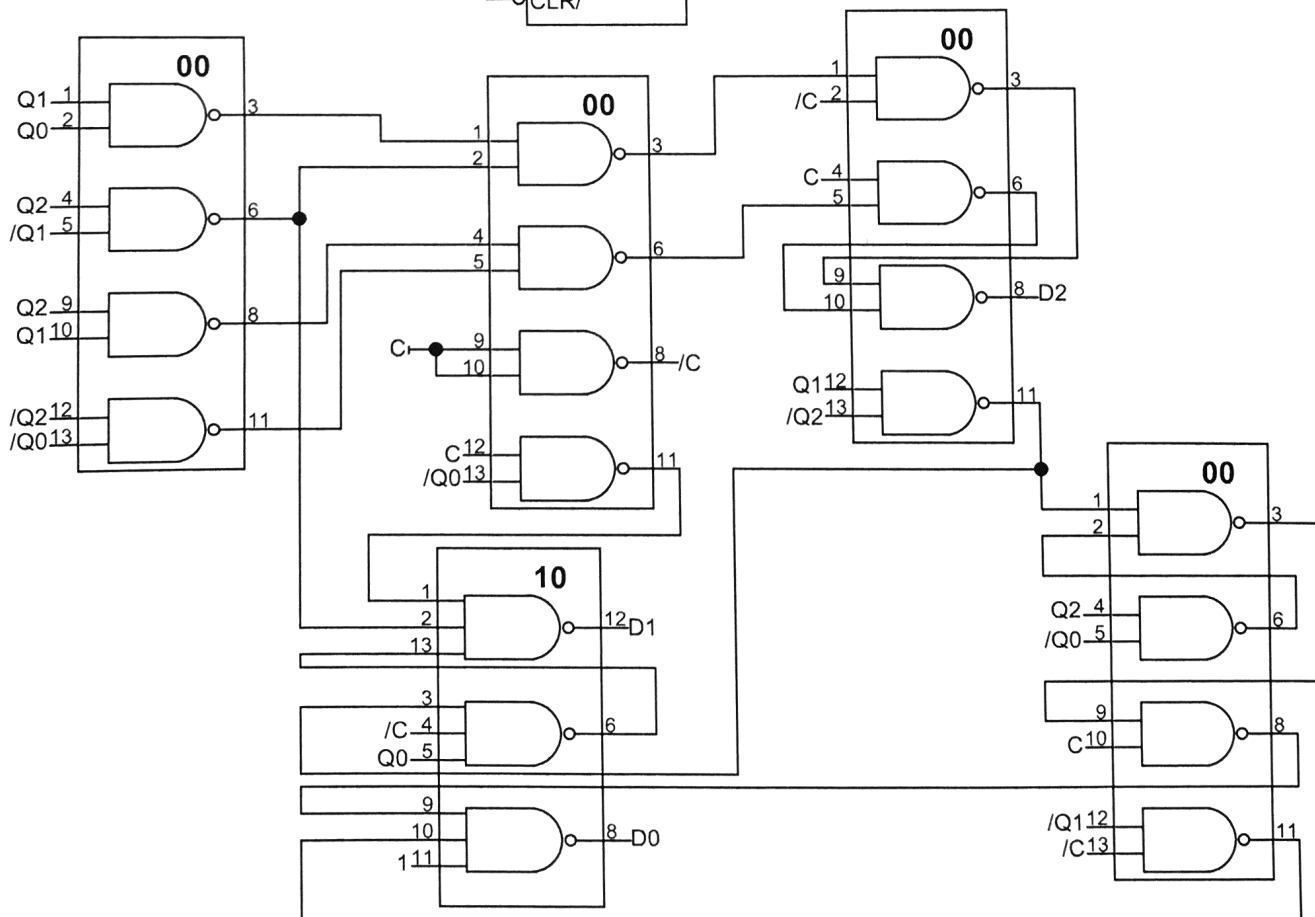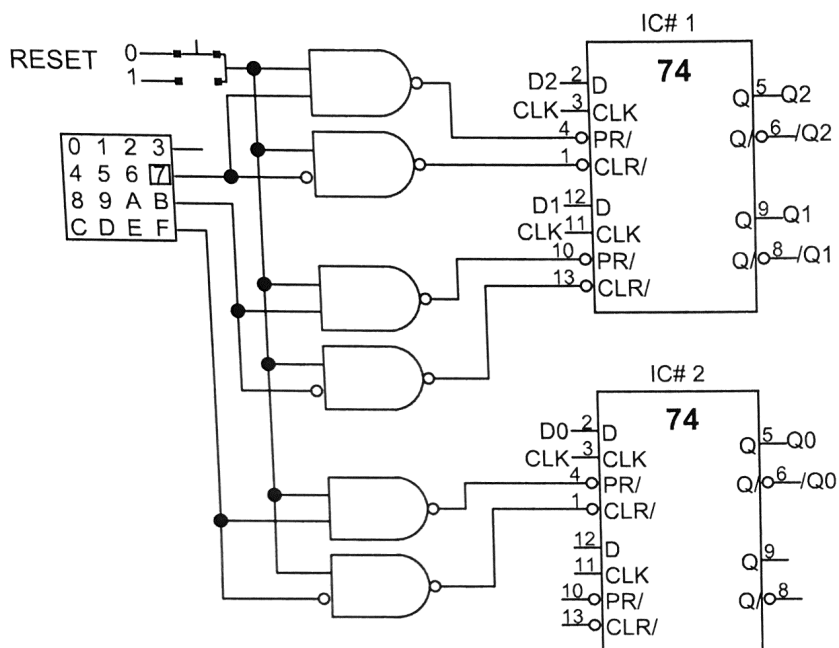      16.265 Logic Design
 Experiment 4: Counter -D flip-flops
 Name: Dangnhi Ngo
 Student Logic Number: 140
 Counter sequence: 134760



4. Design using JK flip-flops

Q_2Q_1	00	01	11	10
CQ_0				
00	0	d	0	1
01	0	1	1	d
11	0	0	1	d
10	1	d	1	0

Q_2^+

Q_2Q_1	00	01	11	10
CQ_0				
00	0	d	0	1
01	1	0	1	d
11	0	0	0	d
10	1	d	1	d

Q_1^+

Q_2Q_1	00	01	11	10
CQ_0				
00	1	d	0	1
01	1	0	0	d
11	0	1	0	d
10	0	d	1	1

Q_0^+

Partition the next state maps into K-maps for the excitation functions.
(Don't forget to label the variables at the upper left corner of each K-map.)

CQ_0	Q_1	00	01	11	10
0	0	0	0	0	1
1	d	1	0	d	d

J_2

CQ_0	Q_2	00	01	11	10
0	0	1	0	1	1
1	1	d	d	d	d

J_1

CQ_0	Q_2Q_1	00	01	11	10
0	1	d	0	1	1
1	0	d	1	1	1

J_0

CQ_0	Q_1	00	01	11	10
0	0	d	d	1	1
1	1	0	0	0	0

K_2

CQ_0	Q_2	00	01	11	10
0	d	1	1	d	d
1	1	0	1	0	0

K_1

CQ_0	Q_2Q_1	00	01	11	10
0	0	1	1	d	d
1	1	0	1	d	d

K_0

Determine the excitation functions from the six K-maps.



$$\begin{aligned} J_2 &= C'Q_1 + CQ_0' \\ J_1 &= Q_2 + (C \oplus Q_0) \\ J_0 &= Q_1'C' + Q_2C \end{aligned}$$

$$\begin{aligned} K_2 &= CQ_1' + C'Q_0'Q_1 \\ K_1 &= Q_2' + CQ_0 + C'Q_0' \\ K_0 &= Q_2 + (Q_1 \oplus C) \end{aligned}$$

List of ICs and unused gates for design using JK flip-flops

IC number	Type number	Function	Unused gates
1	7476	Dual JK type flip-flops	None
2	7476	Dual JK type flip-flops	1 JK flip-flop
3	7400	2 Input NAND Gates	None
4	7400	2 Input NAND Gates	None
5	7400	2 Input NAND Gates	None
6	7400	2 Input NAND Gates	1
7	7410	3 Input NAND Gates	1
8	7486	2 Input XOR Gates	2

  Simulation results for design using JK flip-flops



Draw the schematic diagrams for the counter using JK flip-flops.
Insert a complete schematic diagram including the title box.

16.265 Logic Design
 Experiment 4:: Counter - JK flip-flops
 Name: Dangnhi Ngo
 Student Logic Number: 140
 Counter sequence: 134760

