 




CHAPTER 7

MODULAR CIRCUITS



Decoder

Encoder

Multiplexer

Demultiplexer



7.1.1 Decoder Structure

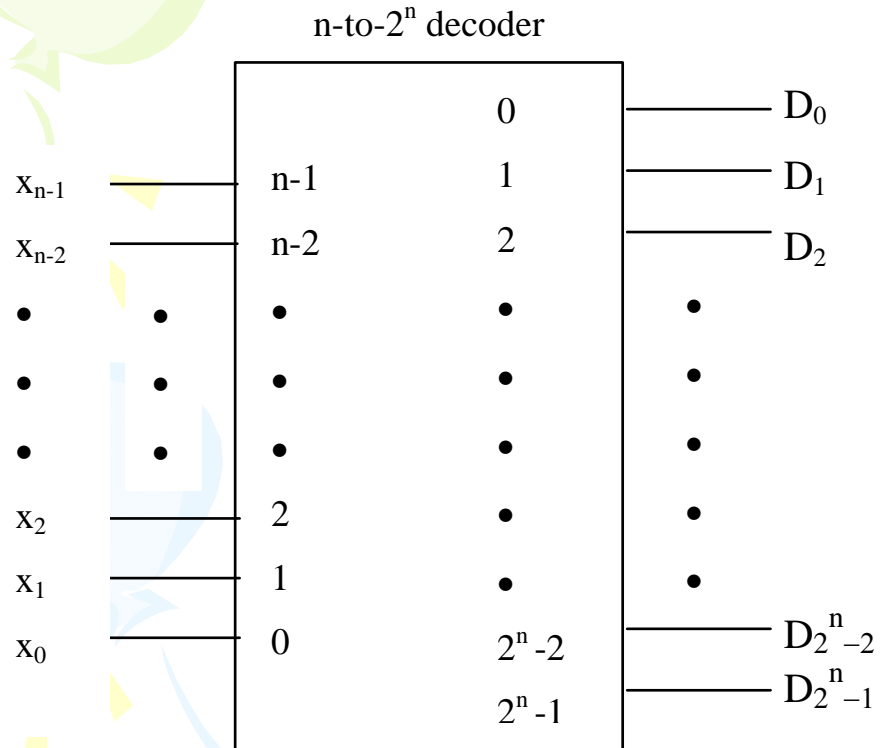


Figure 7.1 n-to- 2^n decoder.

Table 7.1 Truth table for a 3-to-8 decoder.

$x_2 x_1 x_0$	D_0	D_1	D_2	D_3	D_4	D_5	D_6	D_7
0 0 0	1	0	0	0	0	0	0	0
0 0 1	0	1	0	0	0	0	0	0
0 1 0	0	0	1	0	0	0	0	0
0 1 1	0	0	0	1	0	0	0	0
1 0 0	0	0	0	0	1	0	0	0
1 0 1	0	0	0	0	0	1	0	0
1 1 0	0	0	0	0	0	0	1	0
1 1 1	0	0	0	0	0	0	0	1

7.1.2 Decoders with Active-Low Outputs

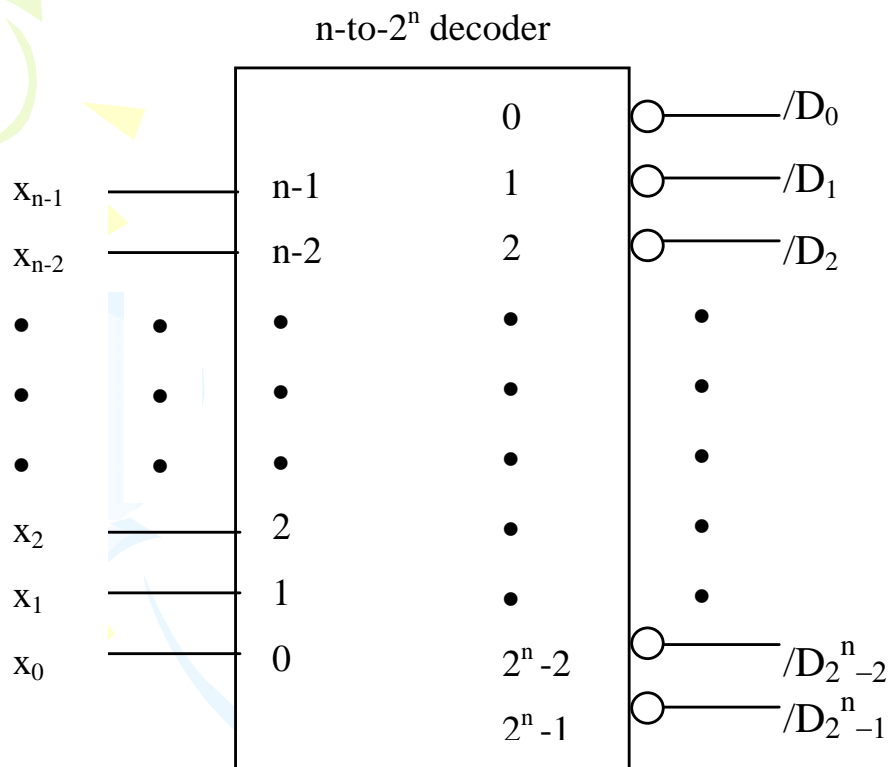


Figure 7.2 n-to- 2^n decoder with active-low outputs.

Table 7.2 Truth table for a 3-to-8 decoder with active-low output.

$x_2 \ x_1 \ x_0$	D_0	D_1	D_2	D_3	D_4	D_5	D_6	D_7
0 0 0	0	1	1	1	1	1	1	1
0 0 1	1	0	1	1	1	1	1	1
0 1 0	1	1	0	1	1	1	1	1
0 1 1	1	1	1	0	1	1	1	1
1 0 0	1	1	1	1	0	1	1	1
1 0 1	1	1	1	1	1	0	1	1
1 1 0	1	1	1	1	1	1	0	1
1 1 1	1	1	1	1	1	1	1	0

$$D_i = M_i$$

7.1.3 Decoders with Enable Control

$$D_0 = \text{EN} (x_1' x_0')$$

$$D_1 = \text{EN} (x_1' x_0)$$

$$D_2 = \text{EN} (x_1 x_0')$$

$$D_3 = \text{EN} (x_1 x_0)$$

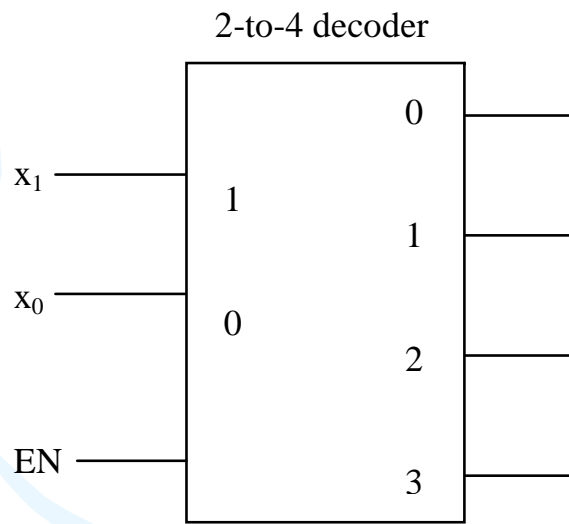


Figure 7.3 2-to-4 decoder with enable control.

Table 7.3 Truth table for Figure 7.7.

EN	x_1	x_0	D_0	D_1	D_2	D_3
0	d	d	0	0	0	0
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1

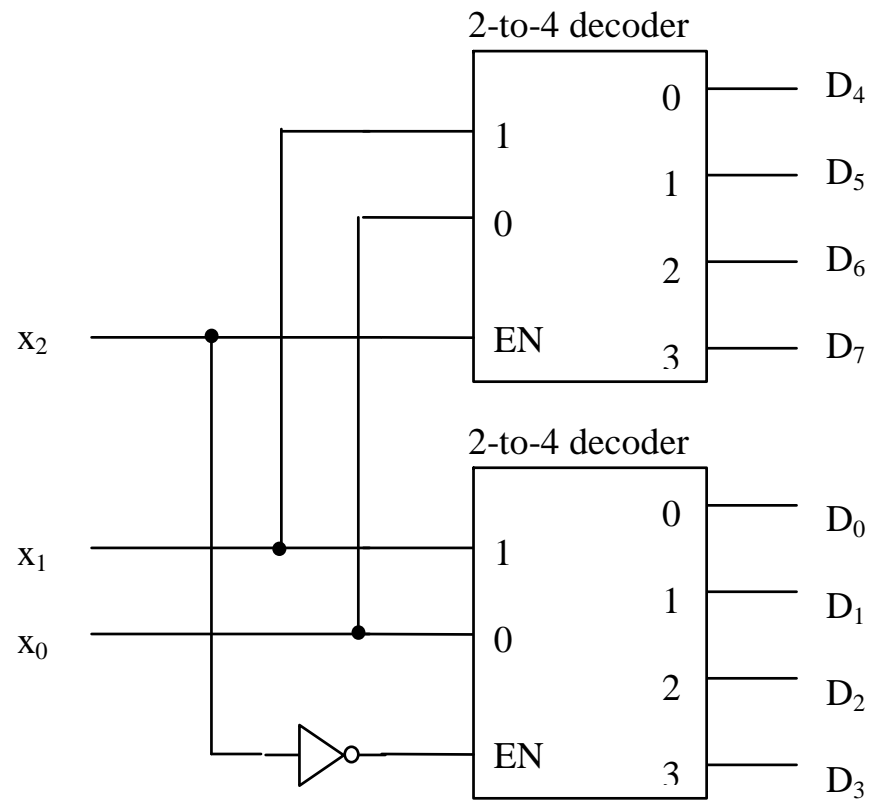


Figure 7.4 Realization of 3-to-8 decoder by 2-to-4 decoders.


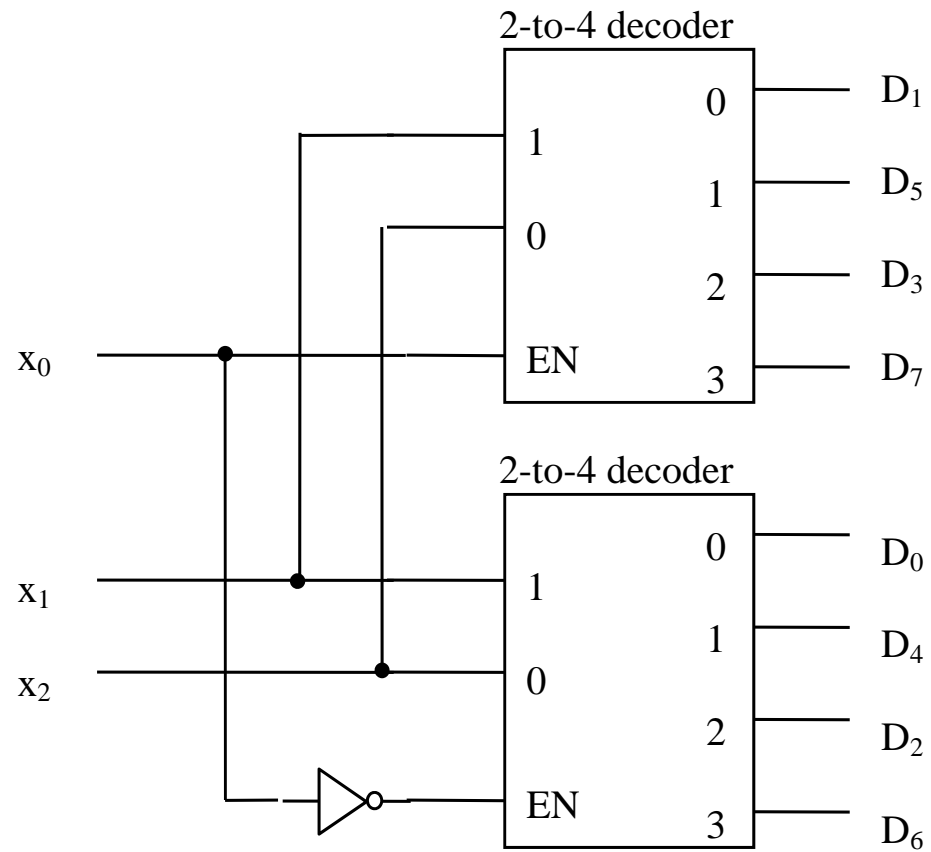


Figure 7.4 Realization of 3-to-8 decoder by 2-to-4 decoders.

Figure 7.5 Realization of 4-to-16 decoder by 2-to-4 decoders.

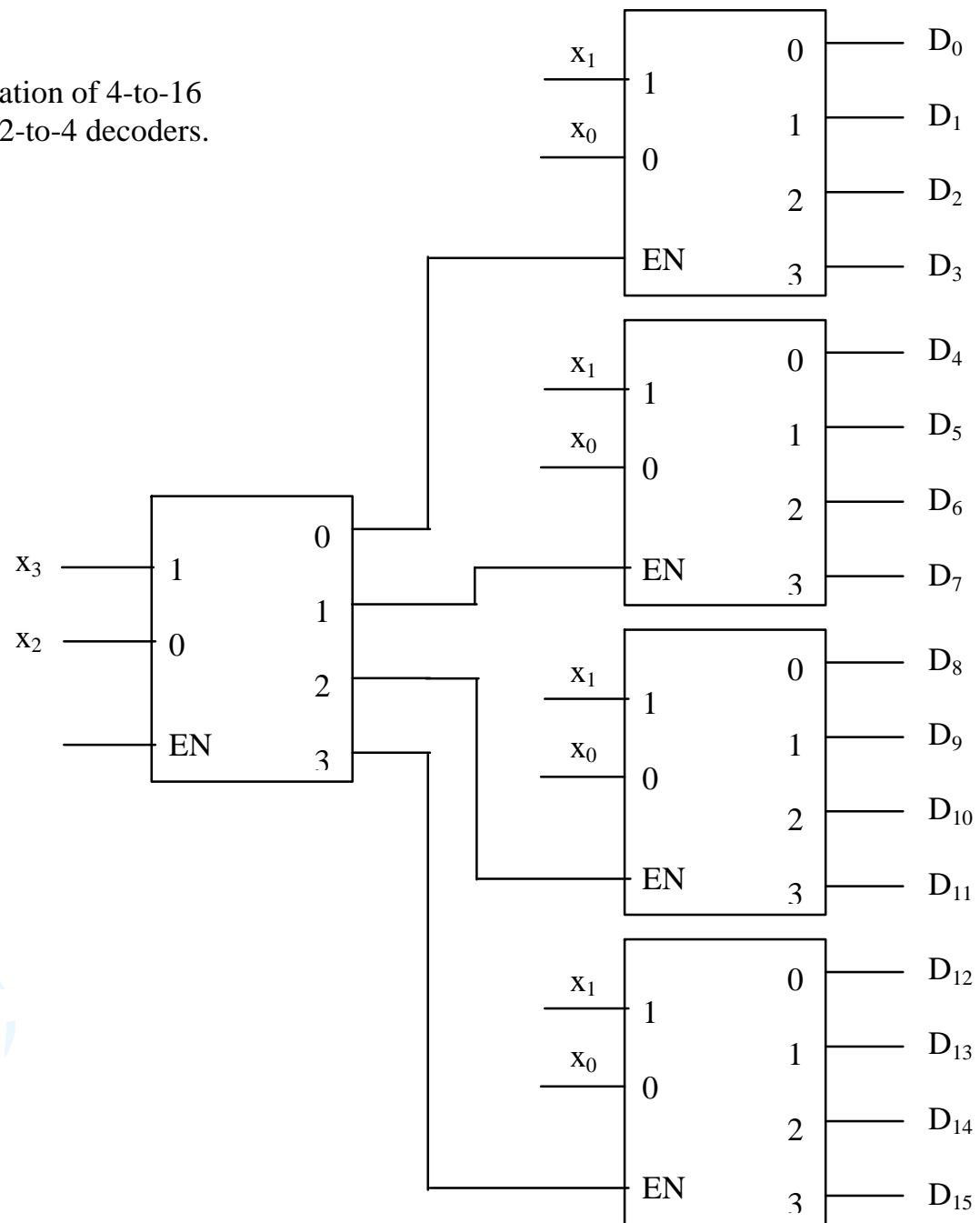

7.1.5 Implementation of Functions Using Decoders

$$F(A, B, C) = \Sigma m(0, 3, 5)$$

 
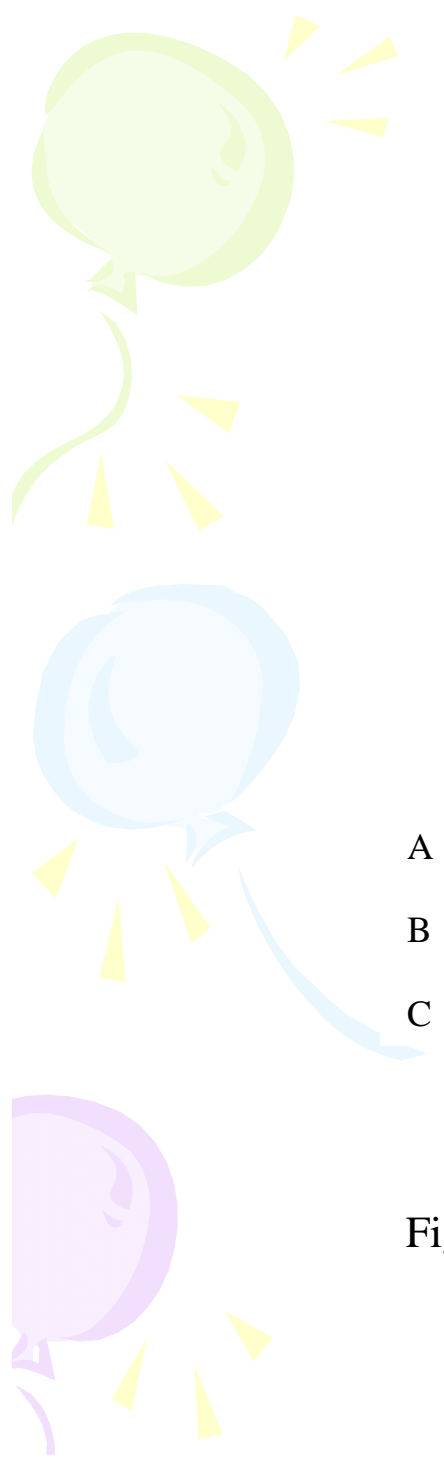


Figure 7.6 Function realization using decoder and OR gate.


$$F(A, B, C) = \Sigma m(0, 3, 5)$$

$$F'(A, B, C) = \pi M(0, 3, 5) = \Sigma m(1, 2, 4, 6, 7)$$

 


Figure 7.7 Function realization using decoder and OR gate.

$$F = \sum m(0, 3, 5) = \pi M(1, 2, 4, 6, 7)$$

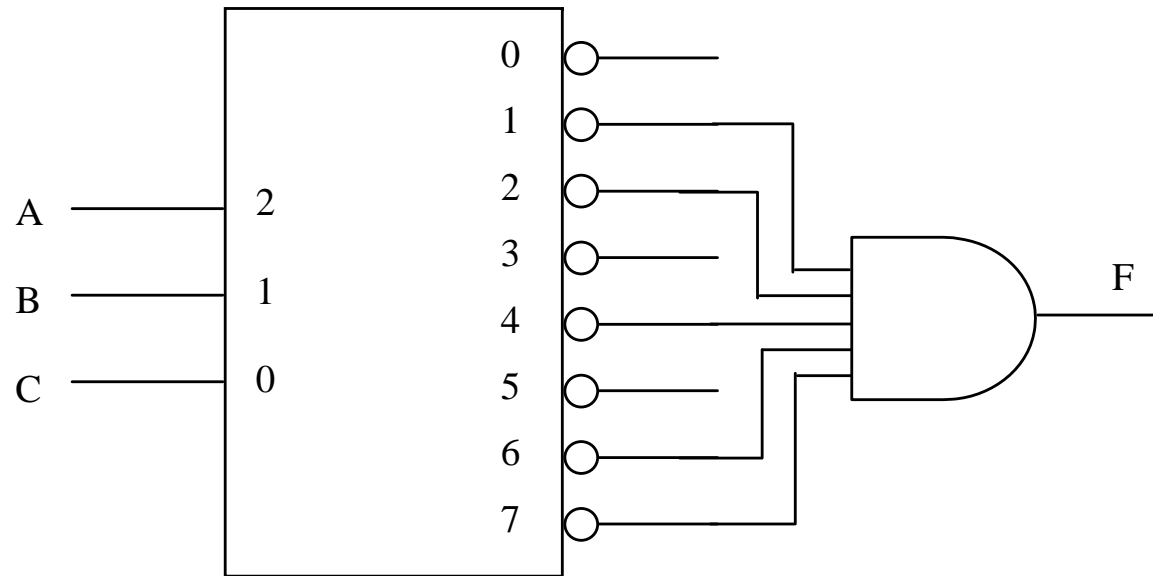
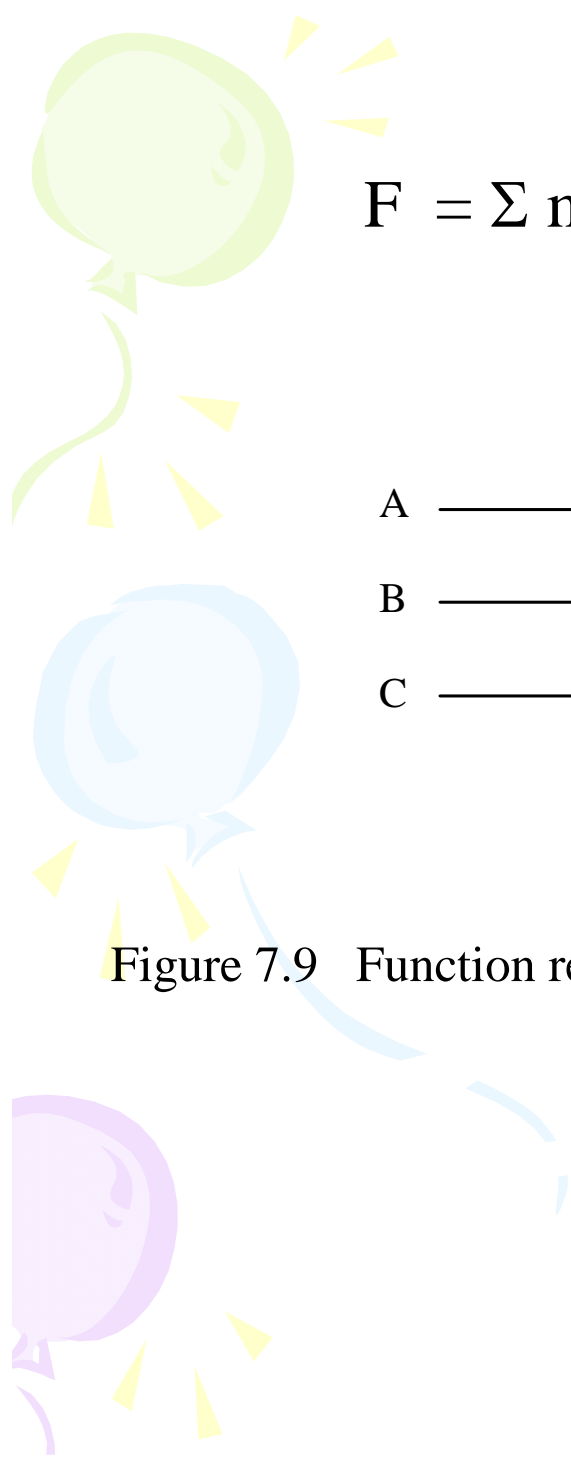


Figure 7.8 Function realization using decoder with inverted output and AND gate.


$$F = \Sigma m(0, 3, 5) = \pi M(1, 2, 4, 6, 7)$$

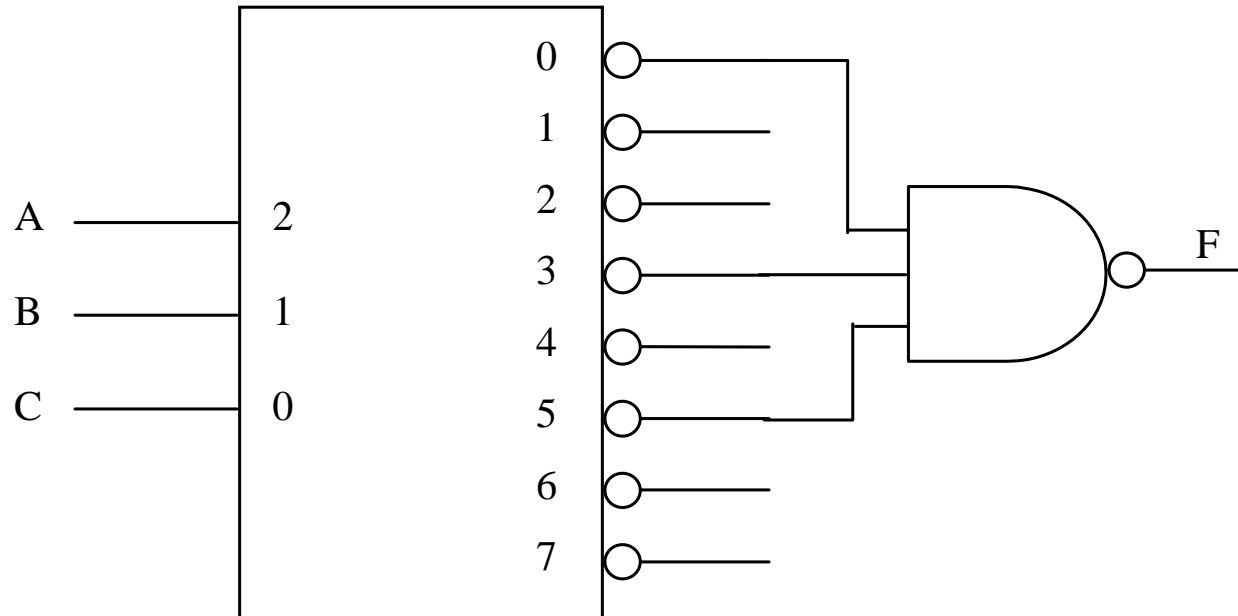


Figure 7.9 Function realization using decoder with inverted output and NAND gate.

7.2.1 Encoder Structure

 


Figure 7.10 4-to-2 encoder.

Table 7.4 Truth table for a 4-to-2 encoder.

D ₃	D ₂	D ₁	D ₀	x ₁	x ₀
1	0	0	0	1	1
0	1	0	0	1	0
0	0	1	0	0	1
0	0	0	1	0	0

$$x_1 = \Sigma m(4, 8) + d(0, 3, 5, 6, 7, 9, 10, 11, 12, 13, 14, 15) = D_3 + D_2$$

$$x_0 = \Sigma m(2, 8) + d(0, 3, 5, 6, 7, 9, 10, 11, 12, 13, 14, 15) = D_3 + D_1$$

 
 


Figure 7.11 4-to-3 encoder.


Table 7.5 Truth table for a 4-to-3 encoder.

D ₃ D ₂ D ₁ D ₀	x ₂ x ₁ x ₀
1 0 0 0	1 1 1
0 1 0 0	1 1 0
0 0 1 0	1 0 1
0 0 0 1	1 0 0
All other input states	0 0 0

$$\begin{aligned}x_2 &= \Sigma m(1, 2, 4, 8) \\&= D_3'D_2'D_1'D_0 + D_3'D_2'D_1D_0' + D_3'D_2D_1'D_0' + D_3D_2'D_1'D_0'\end{aligned}$$

$$x_1 = \Sigma m(4, 8) = D_3'D_2D_1'D_0' + D_3D_2'D_1'D_0'$$
 
$$x_0 = \Sigma m(2, 8) = D_3'D_2'D_1D_0' + D_3D_2'D_1'D_0'$$



7.2.2 Priority Encoders

 


Table 7.6 Truth table for a 4-to-2 priority encoder.

D_3	D_2	D_1	D_0	x_1	x_0	G
0	0	0	0	0	0	0
0	0	0	1	0	0	1
0	0	1	d	0	1	1
0	1	d	d	1	0	1
1	d	d	d	1	1	1

Figure 7.12 4-to-2 priority encoder.

$$x_1 = \Sigma m(4 - 7, 8 - 15) = D_3 + D_2'$$

$$x_0 = \Sigma m(2, 3, 8 - 15) = D_3 + D_2' D_1$$

$$G = \Sigma m(1-15) = M_0 = D_3 + D_2 + D_1 + D_0$$

7.3 Multiplexers

7.3.1 Multiplexer Structure

 


Figure 7.13 Logic diagram of a 2ⁿ-to-1 multiplexer.




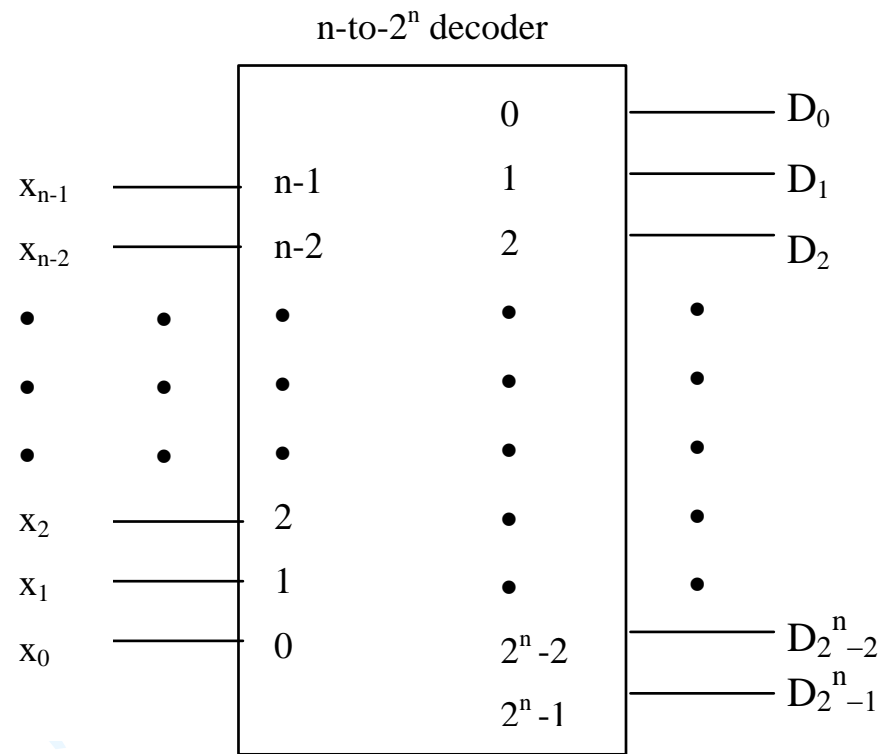
 
 
 


Figure 7.1 n-to- 2^n decoder.

 

 

$Y = 0$ if $C = 0$
 $Y = I$ if $C = 1$

 

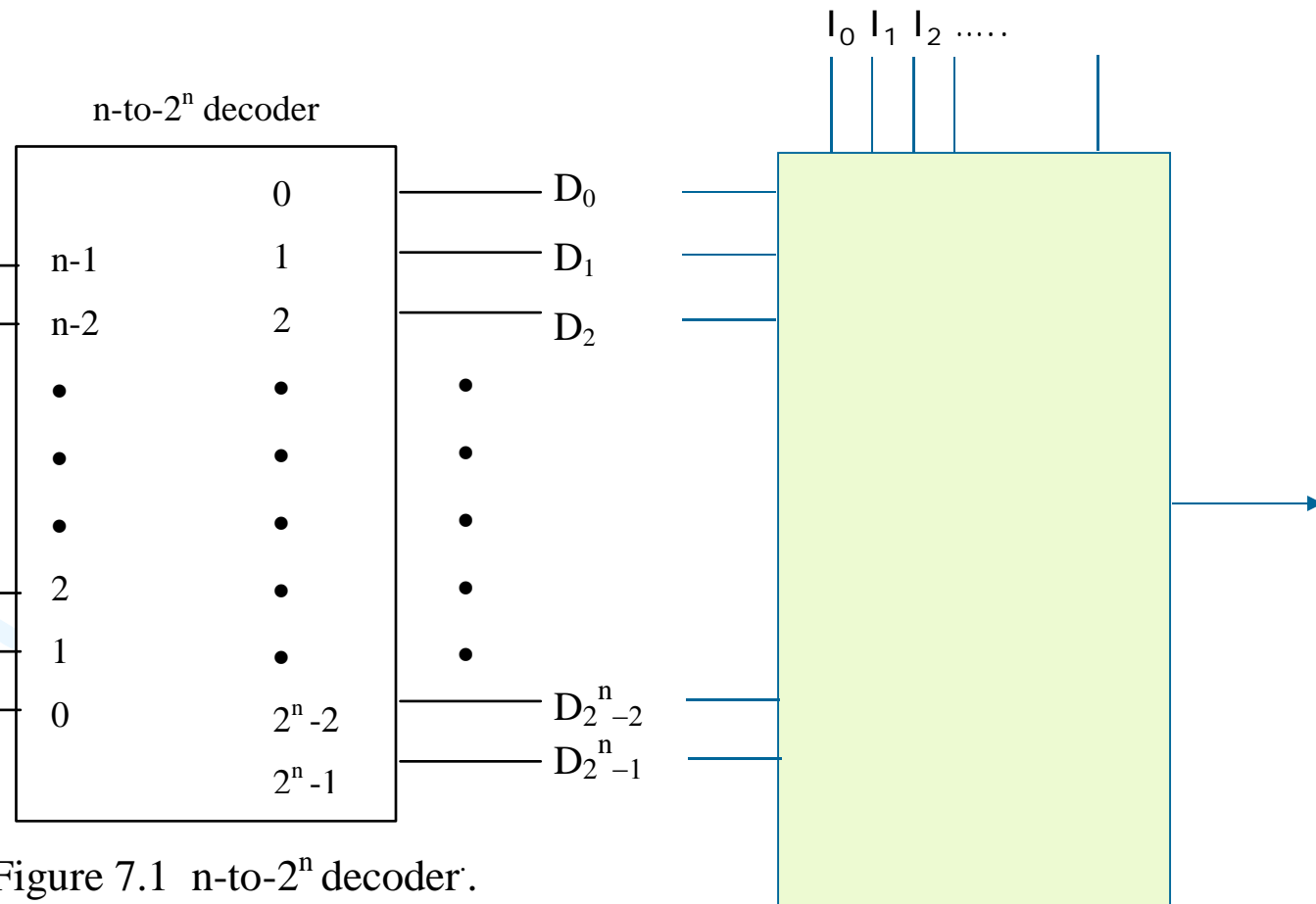
 


Table 7.7 Truth table for a 4-to-1 multiplexer.

A	B	Y
0	0	I ₀
0	1	I ₁
1	0	I ₂
1	1	I ₃

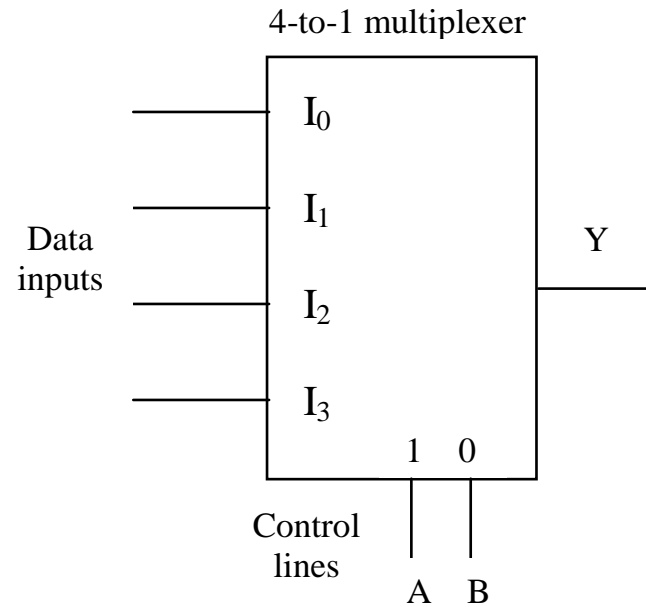


Figure 7.14 Logic diagram for a 4-to-1 multiplexer.

$$Y = A'B'I_0 + A'BI_1 + A'BI_2 + ABI_3$$

$$Y = m_0I_0 + m_1I_1 + m_2I_2 + m_3I_3 = \sum_{i=0}^3 m_i I_i$$

The above equation can be generalized to a 2^n -to-1 multiplexer.

$$Y = \sum_{i=0}^{2^n - 1} m_i I_i$$

Table 7.7 Truth table for a 4-to-1 multiplexer.

A	B	Y
0	0	I ₀
0	1	I ₁
1	0	I ₂
1	1	I ₃

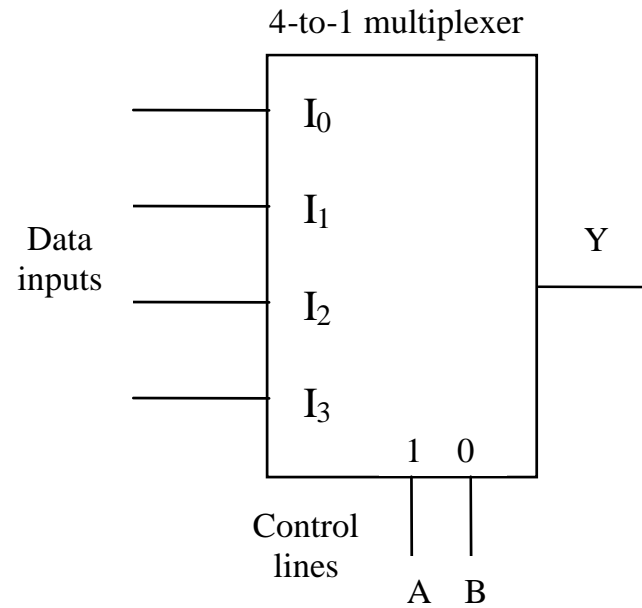


Figure 7.14 Logic diagram for a 4-to-1 multiplexer.

$$Y = A'B'I_0 + A'BI_1 + A'BI_2 + ABI_3$$

$$Y = m_0I_0 + m_1I_1 + m_2I_2 + m_3I_3 = \sum_{i=0}^3 m_i I_i$$

The above equation can be generalized to a 2^n -to-1 multiplexer.

$$Y = \sum_{i=0}^{2^n - 1} m_i I_i$$

7.3.2 Design of Multiplexers

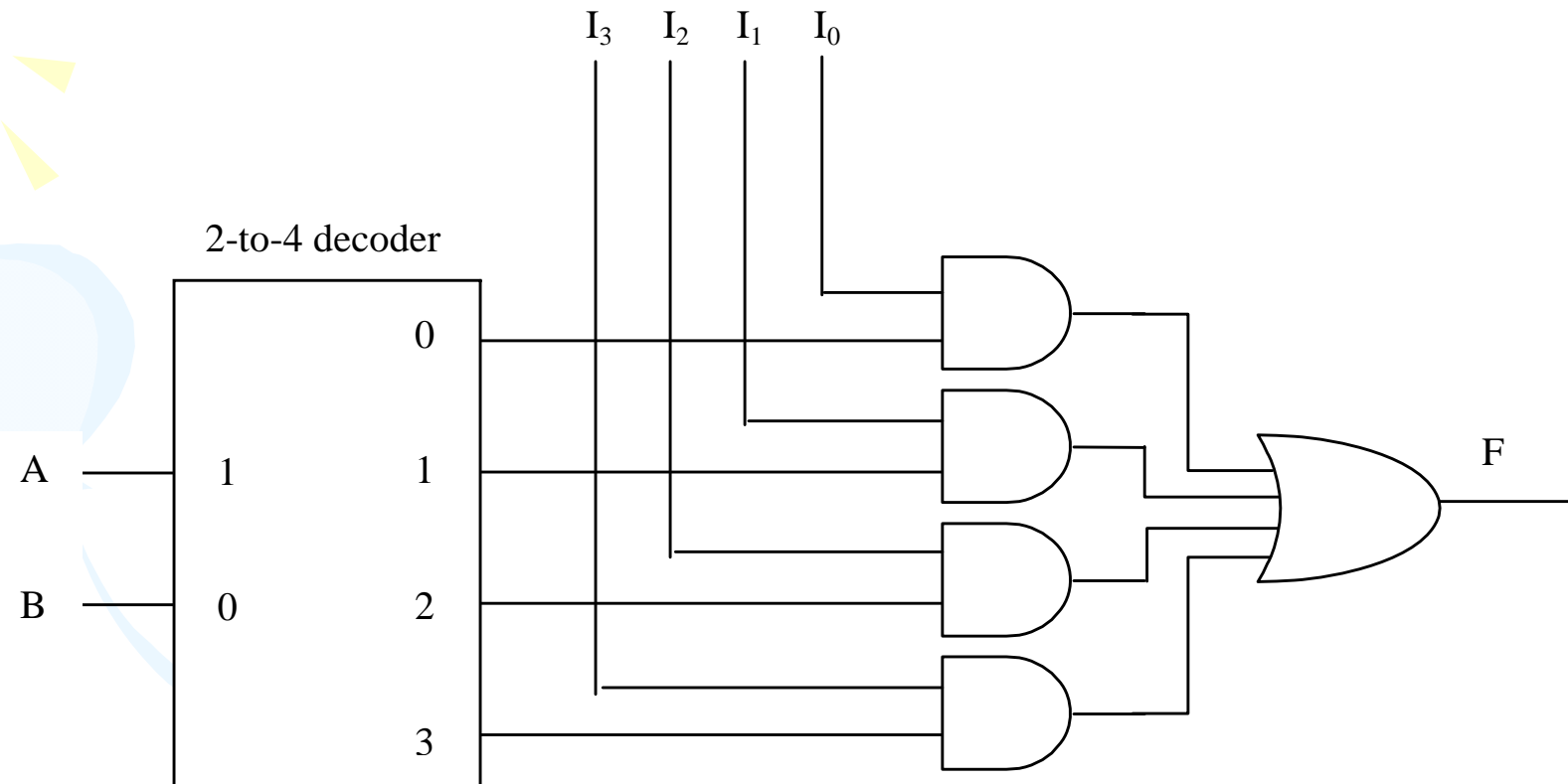


Figure 7.15 Design of a 4-to-1 multiplexer using a 2-to-4 decoder.

Figure 7.16 Logic diagram of a tri-state buffer.

$EN = 1$ $X = Y$
 $EN = 0$ High Z


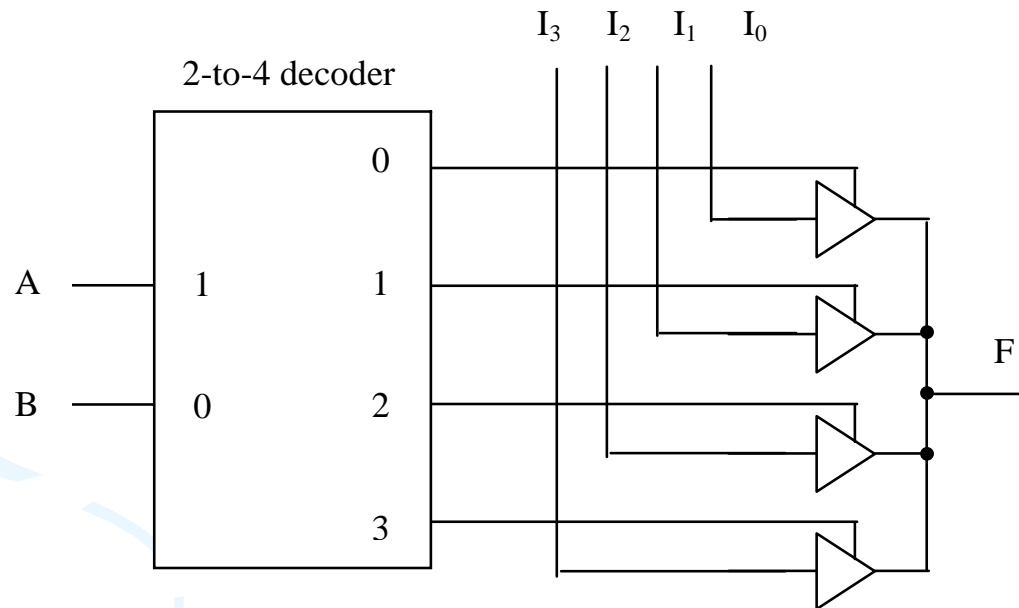


Figure 7.17 Design of a multiplexer using a decoder and four tri-state buffers.

 


7.3.3 Multiplexers with Enable Control


Similar to decoders, multiplexers may be enabled or disabled. When the enable signal is asserted, a multiplexer is activated. One of the data inputs is routed to the output. When the enable signal is de-asserted, a multiplexer is disabled. The output is de-asserted and has a value of 0 for active-high output, or a value of 1 for active-low output. The standard expression for a 2^n -to-1 multiplexers can be modified as follows. EN is the enable input.

$$Y = EN \left(\sum_{i=0}^{2^n - 1} m_i I_i \right)$$

For an active-low enable input $/EN$,

$$Y = (/EN)' \left(\sum_{i=0}^{2^n - 1} m_i I_i \right)$$


7.3.4 Expansion of Multiplexers

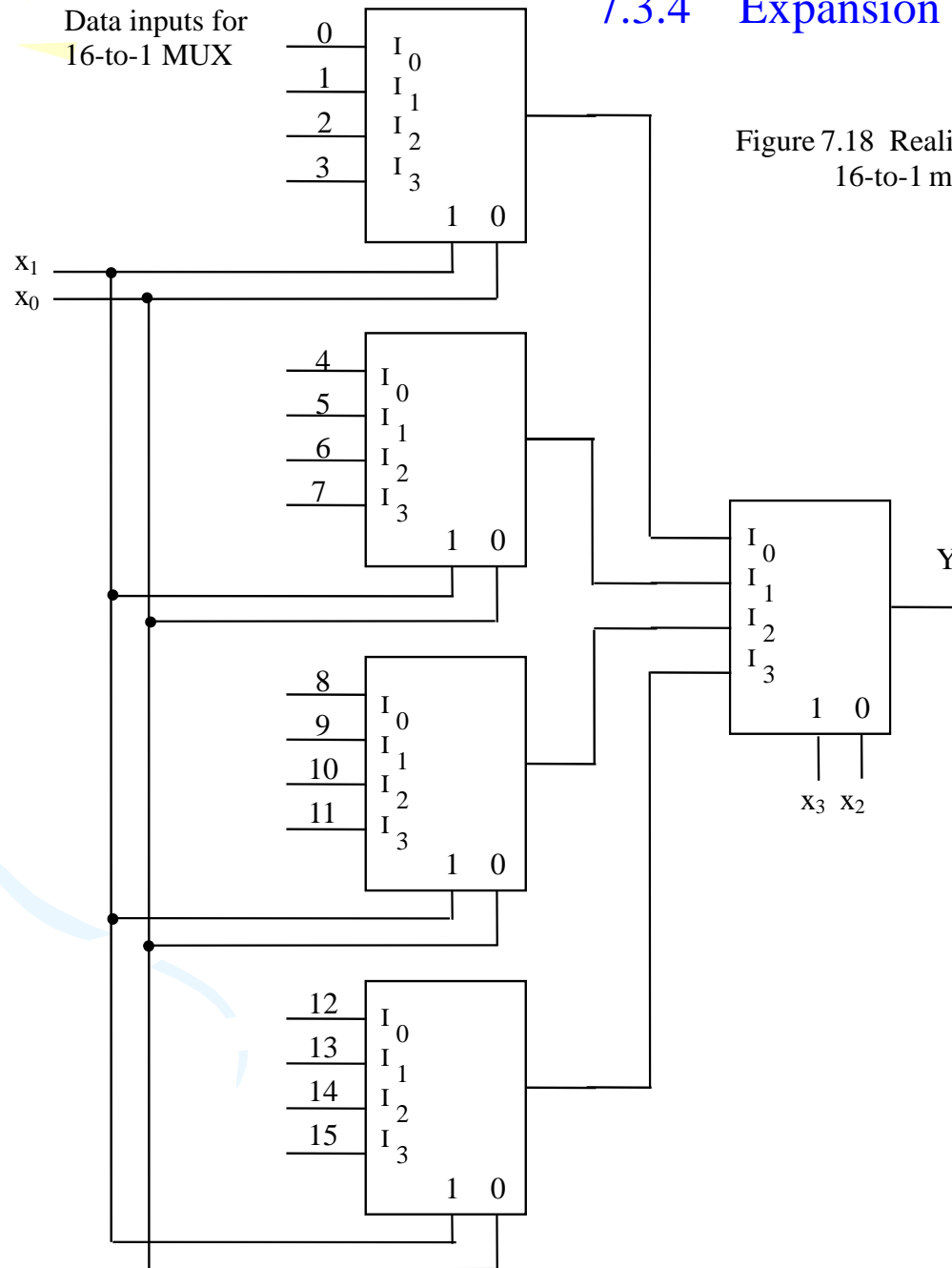

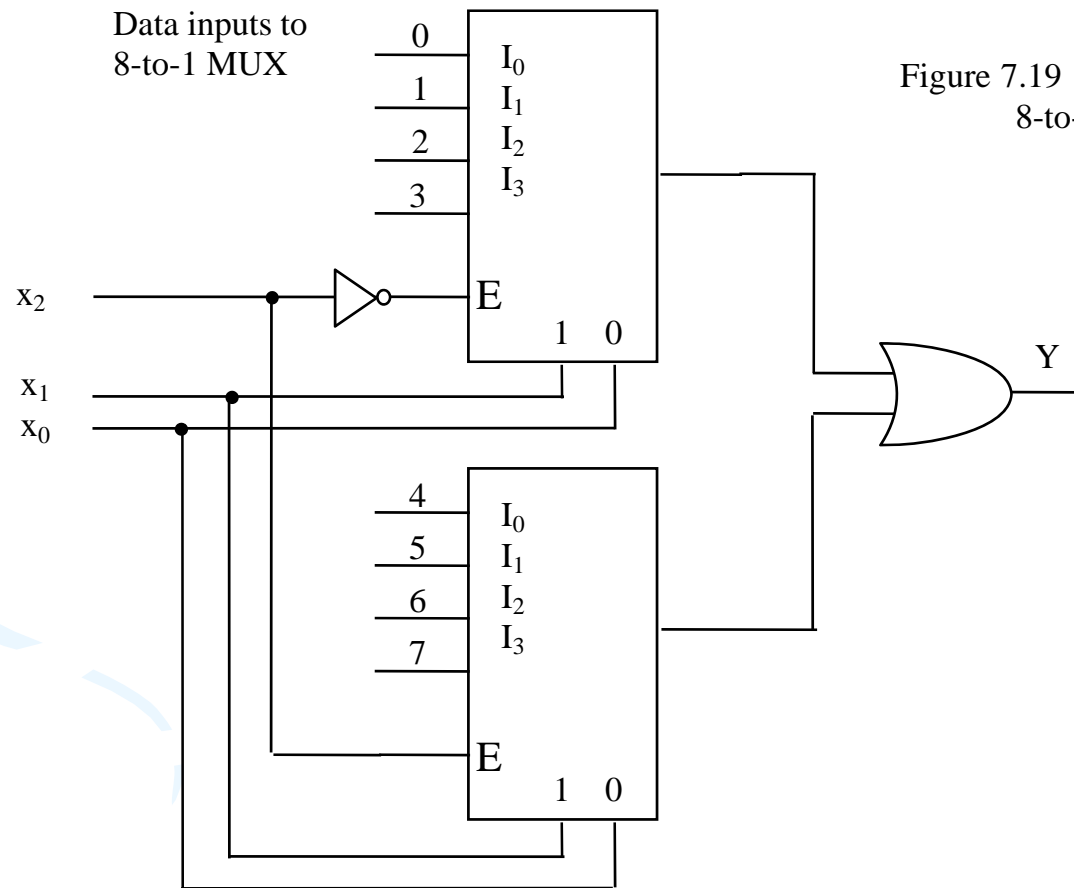
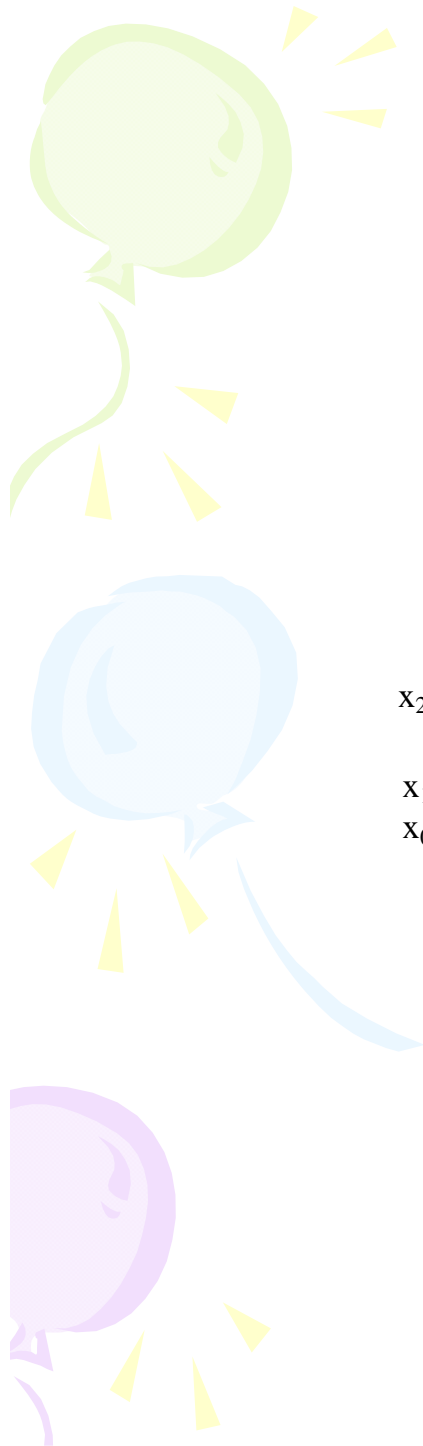


Figure 7.19 Realization of 8-to-1 multiplexer.

7.3.5 Implementation of Functions Using Multiplexers

Table 7.8 Combined table for $F(A,B,C)$ and an 8-to-1 multiplexer.

A	B	C	Y	$F(A,B,C)$
0	0	0	I_0	0
0	0	1	I_1	0
0	1	0	I_2	1
0	1	1	I_3	1
1	0	0	I_4	1
1	0	1	I_5	0
1	1	0	I_6	0
1	1	1	I_7	1

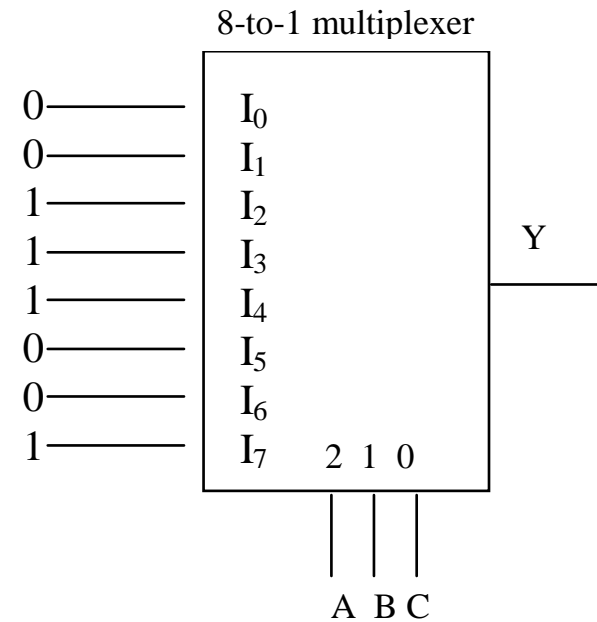



Figure 7.20 Implementation of a 3-variable function by an 8-to-1 multiplexer.



Implementation of $F(A,B,C)$ by a 4-to-1 multiplexer

3-variable function $F(A,B,C)$ is expanded with A and B
 
$$F = A'B'F_{AB=00} + A'B F_{AB=01} + AB' F_{AB=10} + AB F_{AB=11} \quad (7.2)$$





Implementation of $F(A,B,C)$ by a 4-to-1 multiplexer


4-to-1 multiplexer output $Y = A'B'(I_0) + A'B(I_1) + AB'(I_2) + AB(I_3) \quad (7.1)$

3-variable function $F(A,B,C)$ is expanded with A and B

$$F = A'B'F_{AB=00} + A'B F_{AB=01} + AB' F_{AB=10} + AB F_{AB=11} \quad (7.2)$$

Compare Equations (7.1) and (7.2)

$$F = Y \quad \text{if} \quad \begin{array}{ll} I_0 = F_{AB=00}, I_1 = F_{AB=01}, \\ I_2 = F_{AB=10}, \quad I_3 = F_{AB=11} \end{array}$$

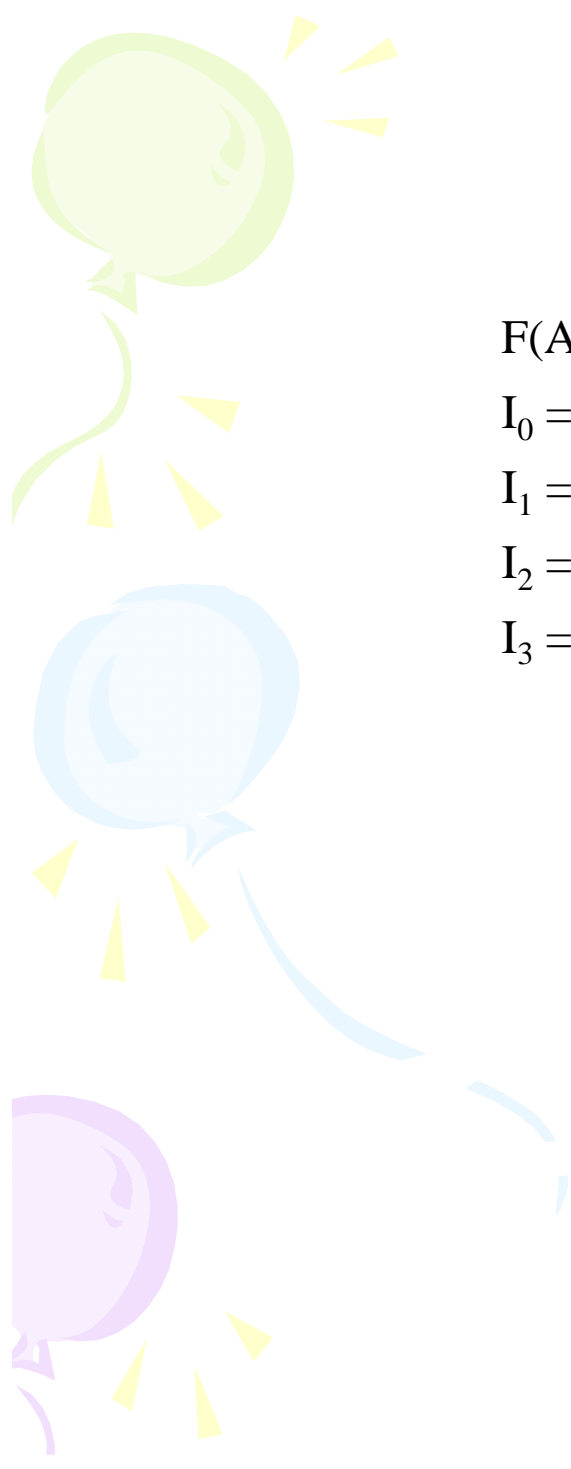
$$F(A,B,C) = \Sigma m(2, 3, 4, 7) = A'B + BC + AB'C'$$

$$I_0 = F_{AB=00} = 0$$

$$I_1 = F_{AB=01} = 1$$

$$I_2 = F_{AB=10} = C'$$

$$I_3 = F_{AB=11} = C$$

 


Figure 7.21 Realization of a 3-variable function by a 4-to-1 multiplexer.

❖ Example 7.1

A 4 variable function is implemented by an 8-to-1 multiplexer in this example. The minterm list form of the function is

$$F(A,B,C,D) = \sum m(0, 2, 3, 5, 7, 10, 14, 15)$$

$$\begin{array}{llll} I_0 = B' & I_1 = B & I_2 = B' & I_3 = 1 \\ I_4 = 0 & I_5 = 0 & I_6 = 1 & I_7 = B \end{array}$$

	I_0	I_1	I_2	I_3	I_4	I_5	I_6	I_7
	$F_{ACD} = 000$	$F_{ACD} = 001$	$F_{ACD} = 010$	$F_{ACD} = 011$	$F_{ACD} = 100$	$F_{ACD} = 101$	$F_{ACD} = 110$	$F_{ACD} = 111$
B								
0	1 ₀	0 ₁	1 ₂	1 ₃	0 ₈	0 ₉	1 ₁₀	0 ₁₁
1	0 ₄	1 ₅	0 ₆	1 ₇	0 ₁₂	0 ₁₃	1 ₁₄	1 ₁₅

Figure 7.22 Sub-function K-maps as data inputs in the implementation of a 4-variable function by an 8-to-1 multiplexer.



Example 7.2



Implementation of a 4-variable function F using a 4-to-1 multiplexer.


$$F(A, B, C, D) = \sum m(0, 1, 3, 5, 8, 11, 14, 15) + d(9, 10, 13)$$



Control inputs A, B

$$I_0 = C' + D$$

$$I_1 = C'D$$

$$I_2 = 1$$

$$I_3 = C$$


Control inputs C, D

$$I_0 = B'$$

$$I_1 = 1$$

$$I_2 = A$$

$$I_3 = A + B'$$

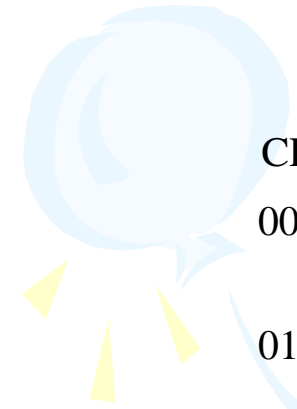

	I_0 $F_{AB=00}$	I_1 $F_{AB=01}$	I_3 $F_{AB=11}$	I_2 $F_{AB=10}$
CD				
00	1 ₀	0 ₄	0 ₁₂	1 ₈
01	1 ₁	1 ₅	d ₁₃	d ₉
11	1 ₃	0 ₇	1 ₁₅	1 ₁₁
10	0 ₂	0 ₆	1 ₁₄	d ₁₀

	AB			
	00	01	11	10
I_0 $F_{CD=00}$	1 ₀	0 ₄	0 ₁₂	1 ₈
I_1 $F_{CD=01}$	1 ₁	1 ₅	d ₁₃	d ₉
I_3 $F_{CD=11}$	1 ₃	0 ₇	1 ₁₅	1 ₁₁
I_2 $F_{CD=10}$	0 ₂	0 ₆	1 ₁₄	d ₁₀




Figure 7.23 Sub-function K-maps as data inputs in the implementation of a 4-variable function by a 4-to-1 multiplexer.

Control inputs B, C

$$I_0 = 1$$

$$I_1 = D$$

$$I_2 = D$$

$$I_3 = A$$

Control inputs A, D

$$I_0 = B'C'$$

$$I_1 = B' + C'$$

$$I_2 = B' + C$$

$$I_3 = 1$$

	I_0	I_1	I_3	I_2
	$F_{BC=00}$	$F_{BC=01}$	$F_{BC=11}$	$F_{BC=10}$
AD				
00	1 ₀	0 ₂	0 ₆	0 ₄
01	1 ₁	1 ₃	0 ₇	1 ₅
11	d ₉	1 ₁₁	1 ₁₅	d ₁₃
10	1 ₈	d ₁₀	1 ₁₄	0 ₁₂

		00	01	11	10
I_0	$F_{AD=00}$	1 ₀	0 ₂	0 ₆	0 ₄
I_1	$F_{AD=01}$	1 ₁	1 ₃	0 ₇	1 ₅
I_3	$F_{AD=11}$	d ₉	1 ₁₁	1 ₁₅	d ₁₃
I_2	$F_{AD=10}$	1 ₈	d ₁₀	1 ₁₄	0 ₁₂

Figure 7.23 Sub-function K-maps as data inputs in the implementation of a 4-variable function by a 4-to-1 multiplexer.

Control inputs A, C

$$I_0 = B' + D$$

$$I_1 = B'D$$

$$I_2 = B'$$

$$I_3 = 1$$

Control inputs B, D

$$I_0 = C'$$

$$I_1 = 1$$


$$I_2 = AC$$

$$I_3 = A + C'$$

	I_0	I_1	I_3	I_2
	$F_{AC=00}$	$F_{AC=01}$	$F_{AC=11}$	$F_{AC=10}$
BD				
00	1 ₀	0 ₂	d ₁₀	1 ₈
01	1 ₁	1 ₃	1 ₁₁	d ₉
11	1 ₅	0 ₇	1 ₁₅	d ₁₃
10	0 ₄	0 ₆	1 ₁₄	0 ₁₂

		AC			
		00	01	11	10
I_0	$F_{BD=00}$	1 ₀	0 ₂	d ₁₀	1 ₈
I_1	$F_{BD=01}$	1 ₁	1 ₃	1 ₁₁	d ₉
I_3	$F_{BD=11}$	1 ₅	0 ₇	1 ₁₅	d ₁₃
I_2	$F_{BD=10}$	0 ₄	0 ₆	1 ₁₄	0 ₁₂

Figure 7.23 Sub-function K-maps as data inputs in the implementation of a 4-variable function by a 4-to-1 multiplexer.

 

Control inputs A, B

$$I_0 = C' + D$$

$$I_1 = C'D$$

$$I_2 = 1$$

$$I_3 = C$$

Control inputs C, D

$$I_0 = B'$$

$$I_1 = 1$$

$$I_2 = A$$

$$I_3 = A + B'$$

Control inputs B, C

$$I_0 = 1$$

$$I_1 = D$$

$$I_2 = D$$

$$I_3 = A$$



Control inputs A, D

$$I_0 = B'C'$$

$$I_1 = B' + C'$$

$$I_2 = B' + C$$

$$I_3 = 1$$

Control inputs A, C

$$I_0 = B' + D$$

$$I_1 = B'D$$

$$I_2 = B'$$

$$I_3 = 1$$



Control inputs B, D

$$I_0 = C'$$

$$I_1 = 1$$

$$I_2 = AC$$

$$I_3 = A + C'$$

7.4 Demultiplexer

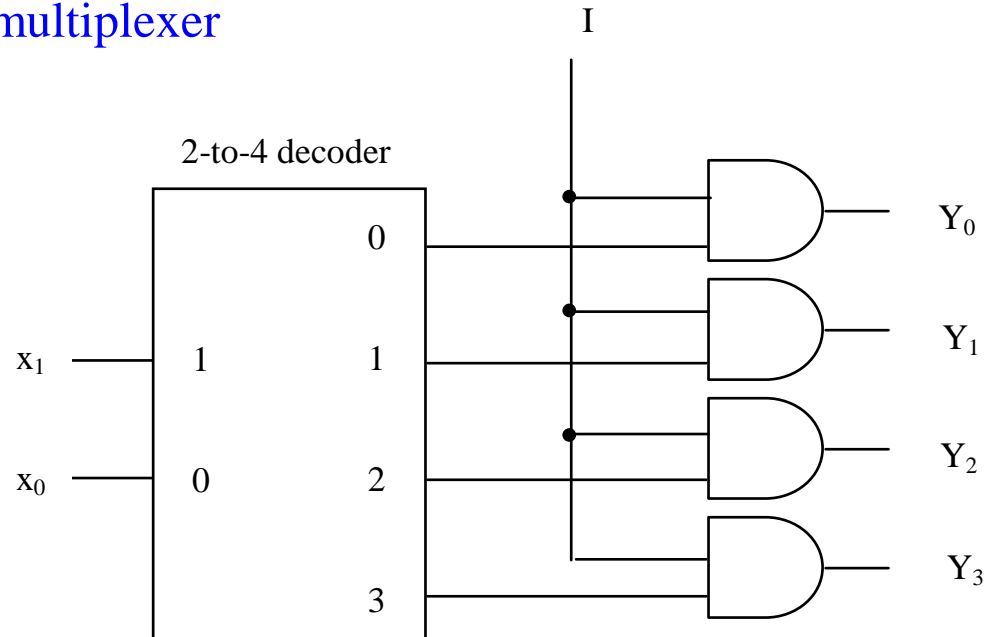


Figure 7.24 Example of a de-multiplexer.

2-to-4 decoder with enable EN
(Section 7.1.4)

$$D_0 = EN (x_1' x_0')$$

$$D_1 = EN (x_1' x_0)$$

$$D_2 = EN (x_1 x_0')$$

$$D_3 = EN (x_1 x_0)$$

Demultiplexer

$$Y_0 = I (x_1' x_0')$$

$$Y_1 = I (x_1' x_0)$$

$$Y_2 = I (x_1 x_0')$$

$$Y_3 = I (x_1 x_0)$$

EN input of decoder as data input for demultiplexer

Demultiplexer with Enable

$$Y_0 = I \cdot EN \cdot (x_1' x_0')$$

$$Y_1 = I \cdot EN \cdot (x_1' x_0)$$

$$Y_2 = I \cdot EN \cdot (x_1 x_0')$$

$$Y_3 = I \cdot EN \cdot (x_1 x_0)$$

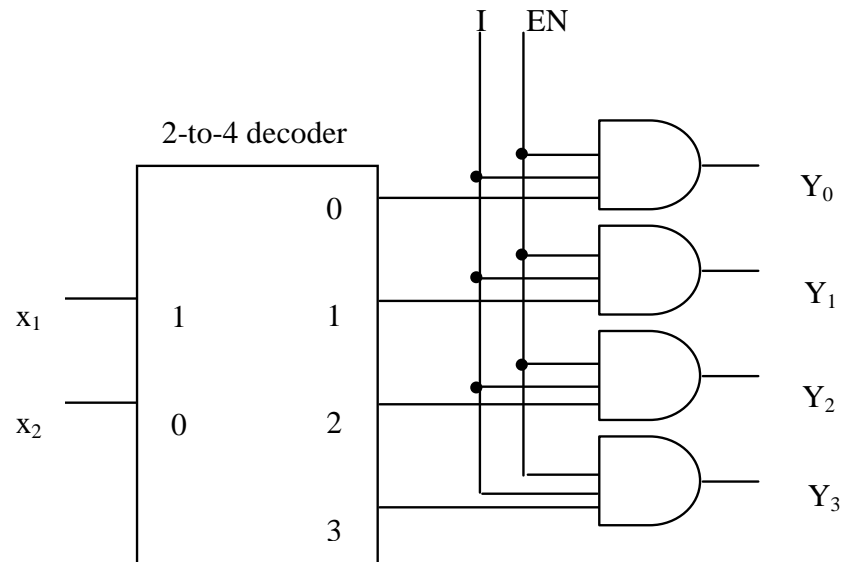


Figure 7.25 A de-multiplexer with enable input.

Demultiplexer with Enable

Data input: I

Control signals: x_1, x_2

Enable (Strobe): EN



Outputs: Y_0, Y_1, Y_2, Y_3

Decoder with Enable

Inputs: x_1, x_2

Enable (strobe): EN, I

Outputs: Y_0, Y_1, Y_2, Y_3

 
 


74155 Dual 2-to-4 Decoders/Demultiplexers

EN (active-high) \rightarrow G (active-low)
 I (active-high) \rightarrow C (active-low in 1), C (active-high in 2)
 x_1, x_2 \rightarrow B, A respectively
 Active-high outputs \rightarrow Active-low outputs


Conversion of 74155 to 3-to-8 Decoder

3-to-8 decoder

  

74153 Dual 4-to-1 Multiplexer

Active-low strobe G. Active-high output.

 

Conversion of 74153 to 8-to-1 Multiplexer

