



CHAPTER 3

BOOLEAN ALGEBRA

Basic Logical Operations

NOT

$$F = x' = \overline{x}$$

Table 3.1 Truth table for NOT.

x	F
0	1
1	0

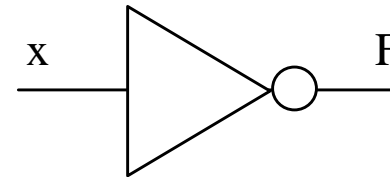


Figure 3.1 Logic symbol for inverter.

$$F(x) = x'$$

$$(x')' = x$$

F : logic function, Boolean function, switching function, or in short a function of x.

x : Boolean variable, switching variable, or in short, a variable.


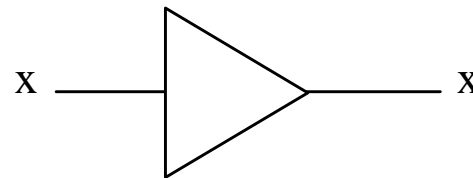


Figure 3.2 Logic symbol for buffer.

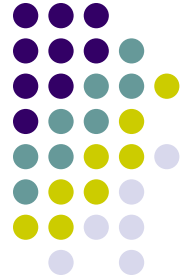

AND

$$F(x,y) = x \bullet y = xy$$

Table 3.2 Truth table for AND.

x	y	F(x,y)
0	0	0
0	1	0
1	0	0
1	1	1

$$A \bullet A = A$$

$$A \bullet 1 = A$$

$$A \bullet 0 = 0$$

$$A \bullet A' = 0$$

$$A \bullet B = B \bullet A$$


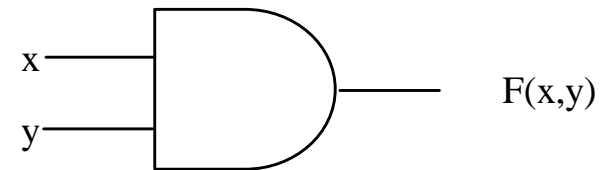


Figure 3.3 Logic symbol for AND gate.

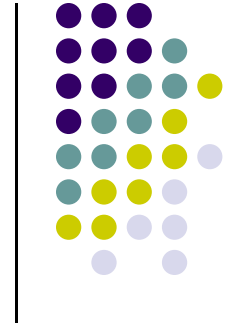

OR

$$F(x,y) = x + y$$

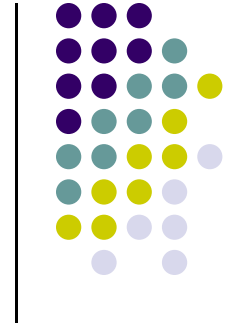


Table 3.3 Truth table for OR.

X	Y	F(x,y)
0	0	0
0	1	1
1	0	1
1	1	1

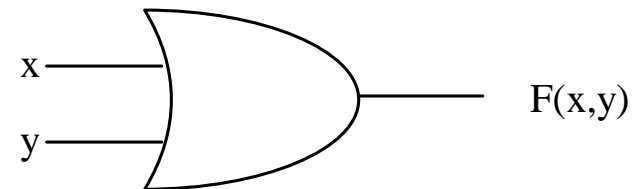


Figure 3.4 Logic symbol for OR.


$$A + A = A$$

$$A + 0 = A$$

$$A + 1 = 1$$

$$A + A' = 1$$

$$A + B = B + A$$

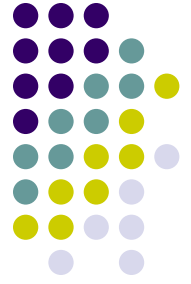

$$\begin{array}{ccccccc} (A \bullet C) & + & (D \bullet (& (& A + B') & ' & + C) &) \\ 1 & & 1 & & 4 & 3 & 2 & & 2 & & 3 & 4 \end{array}$$


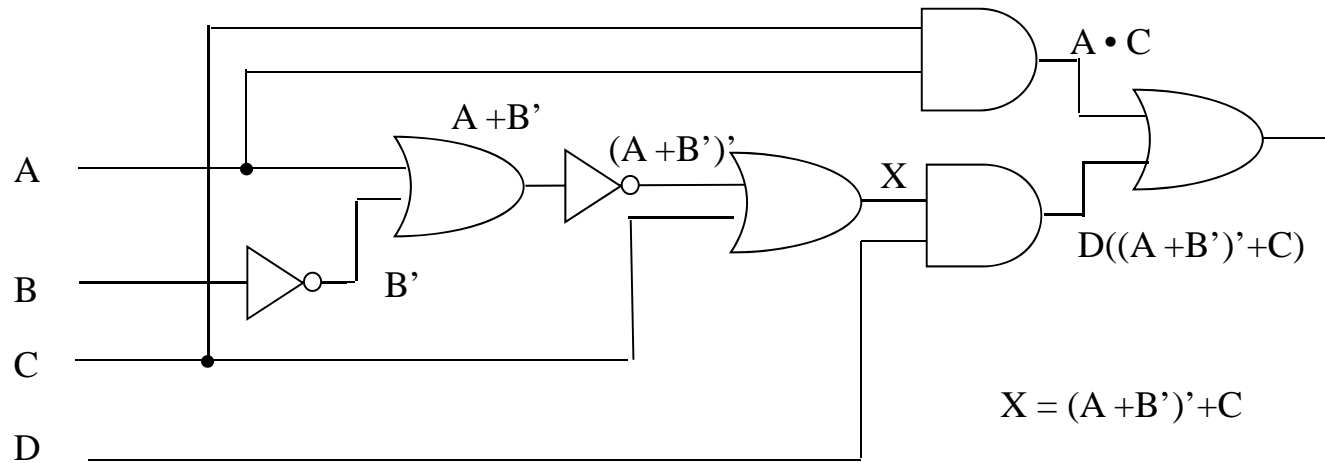


Figure 3.5 Logic circuit.

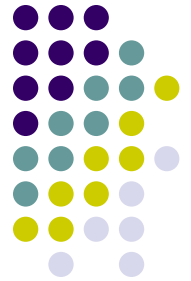

Basic Laws

(1) Involution law

$$(A')' = A$$

(2) Idempotency law

(a) $A \cdot A = A$

(b) $A + A = A$

(3) Laws of 0 and 1

(a) $A \cdot 1 = A$

(b) $A + 0 = A$

(a') $A \cdot 0 = 0$

(b') $A + 1 = 1$

(4) Complementary law


(a) $A \cdot A' = 0$

(b) $A + A' = 1$

(5) Commutative law

(a) $A \cdot B = B \cdot A$

(b) $A + B = B + A$

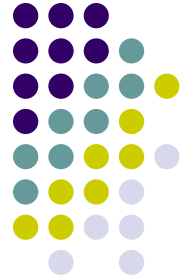


(6) Associative law

$$(a) \quad (A \cdot B) \cdot C = A \cdot (B \cdot C)$$


$$(b) \quad (A + B) + C = A + (B + C)$$

Table 3.4 Proof of associative law (6a)


A B C	A B	Left-hand-side of (6a) (A B) C	B C	Right-hand- side of (6a) A (B C)
0 0 0	0	0	0	0
0 0 1	0	0	0	0
0 1 0	0	0	0	0
0 1 1	0	0	1	0
1 0 0	0	0	0	0
1 0 1	0	0	0	0
1 1 0	1	0	0	0
1 1 1	1	1	1	1

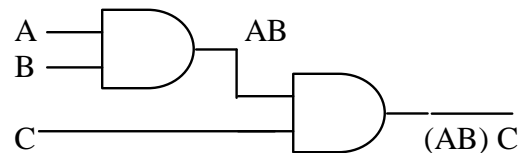

(a)

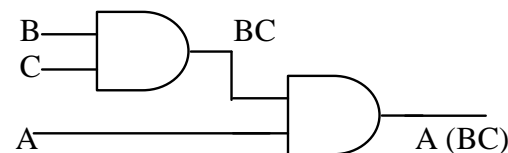


(b)

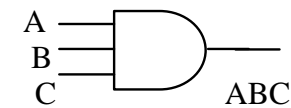

(c)

Figure 3.6 (a) Logic circuit for $(AB)C$. (b) Logic circuit for $A(BC)$. (c) 3-input AND gate.

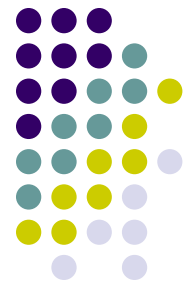


(6) Associative law

$$(a) \quad (A \cdot B) \cdot C = A \cdot (B \cdot C)$$

$$(b) \quad (A + B) + C = A + (B + C)$$

Table 3.4 Proof of associative law (6a)

A B C	A B	Left-hand-side of (6a) (A B) C	B C	Right-hand- side of (6a) A (B C)
0 0 0		0		0
0 0 1		$AB = 0$		0
0 1 0		0		0
0 1 1		$AB = 0$		0
1 0 0		0		$BC = 0$
1 0 1		$AB = 0$		$BC = 0$
1 1 0		0		$BC = 0$
1 1 1		$AB = 1$		$BC = 1$

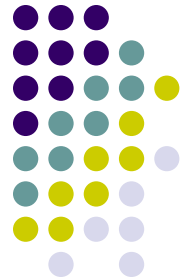

(7) Distributive law

(a) $A(B + C) = AB + AC$

(b) $A + BC = (A + B)(A + C)$

Table 3.5 Proof of distributive law (7a).

A B C	B + C	Left-hand-side of (7a) A (B + C)	A B	A C	Right-hand-side of (7a) AB + AC
0 0 0	0	0	0	0	0
0 0 1	1	0	0	0	0
0 1 0	1	0	0	0	0
0 1 1	1	0	0	0	0
1 0 0	0	0	0	0	0
1 0 1	1	1	0	1	1
1 1 0	1	1	1	0	1
1 1 1	1	1	1	1	1



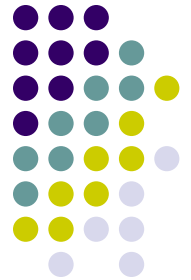


Table 3.6 Proof of distributive law (7b).


A	Left-hand-side of (7b) $A + B C$	Right-hand-side of (7b) $(A + B)(A + C)$
0	$0 + B C = B C$	$(0 + B)(0 + C) = B C$
1	$1 + B C = 1$	$(1 + B)(1 + C) = 1 \bullet 1 = 1$

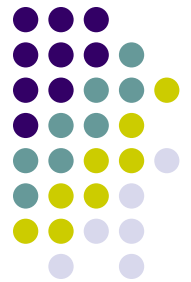


Distributive law (7a)

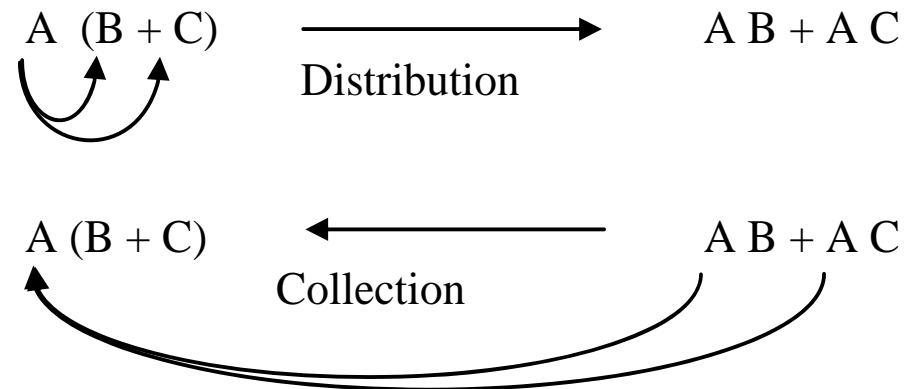

Distributive law (7b)

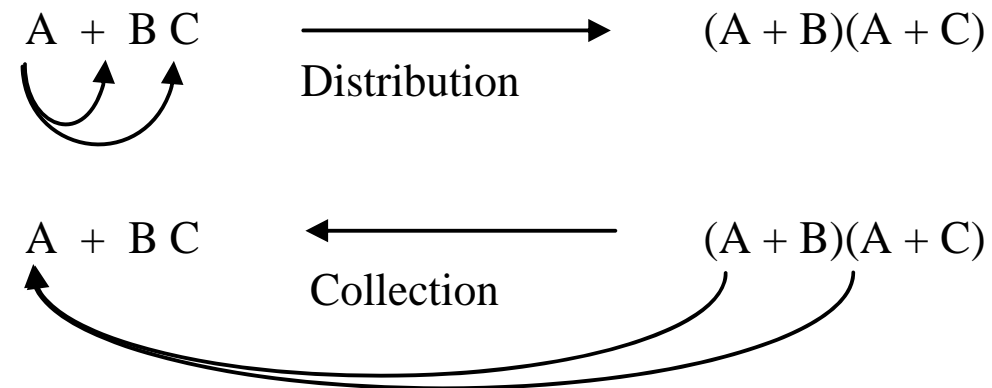

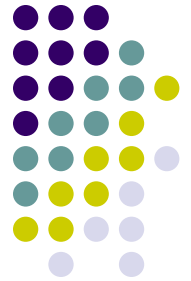

3.3 Sum-of-Products and Product-of-sums Expressions

Literal : a variable appears unprimed or primed in a switching expression.

Sum-of-product (SOP)

$$AB' + BC + A'BD'$$

$$B' + CD + A'C'D' + AE'$$

Product-of-sums (POS)

$$(A' + C')(A + C + D')(B + D')$$

$$C' (B' + D') (A + B + D)$$



(7) Distributive law

$$(a) \quad A (B + C) = A B + A C$$

POS

SOP

$$(b) \quad A + B C = (A + B) (A + C)$$


SOP

POS



Simplest (Minimal) Sum-of-Products and Product-of-Sums Expressions

When a literal or a product is deleted from a sum-of-products expression for a switching function, the expression with deleted literal/product is no longer correct for the function. Then the sum-of-products expression is said to be simplest or minimal. In other words, a sum-of-products expression is simplest if and only if no literal or product can be deleted from the expression. Thus a simplest sum-of-products expression for a function consists of a minimum number of product terms and the total number of literals in all the product terms is also a minimum.

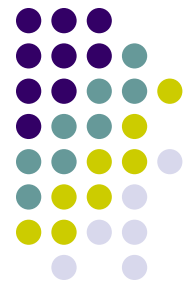

❖ Example 3.1

Show that the sum-of-product expression $(AB' + BCD + A'B'D')$ is not minimal and can be simplified by removing the literal A' from the third product. In other words, show that the following equation is valid.

$$AB' + BCD + A'B'D' = AB' + BCD + B'D' \quad (3.1)$$

Table 3.7 Proof of Equation (3.1).

A B	Left-hand-side of Equation (3.1) $AB' + BCD + A'B'D'$	Right-hand-side of Equation (3.1) $AB' + BCD + B'D'$
0 0	$0 \cdot 0' + 0 \cdot C \cdot D + 0' \cdot 0' \cdot D' = D'$	$0 \cdot 0' + 0 \cdot C \cdot D + 0' \cdot D' = D'$
0 1	$0 \cdot 1' + 1 \cdot C \cdot D + 0' \cdot 1' \cdot D' = CD$	$0 \cdot 1' + 1 \cdot C \cdot D + 1' \cdot D' = CD$
1 0	$1 \cdot 0' + 0 \cdot C \cdot D + 1' \cdot 0' \cdot D' = 1$	$1 \cdot 0' + 0 \cdot C \cdot D + 0' \cdot D' = 1 + D' = 1$
1 1	$1 \cdot 1' + 1 \cdot C \cdot D + 1' \cdot 1' \cdot D' = CD$	$1 \cdot 1' + 1 \cdot C \cdot D + 1' \cdot D' = CD$



❖ Example 3.2

Show that the sum-of-products expression $(AB' + BCD + B'D')$ on the right-hand-side of Equation (3.1) is minimal.

Table 3.8 Proof for simplest sum-of-products expression.

A B C D	Right-hand-side of Equation (3.1)	Expression after removing either a literal or a product from right-hand-side of Equation (3.1)	Literal or product removed from right-hand-side of Equation (3.1)
0 0 0 1 0 0 1 1	$AB' + BCD + B'D' = 0$	$B' + BCD + B'D' = 1$	A in 1 st product
1 1 0 0 1 1 0 1 1 1 1 0	$AB' + BCD + B'D' = 0$	$A + BCD + B'D' = 1$	B' in 1 st product
0 0 1 1	$AB' + BCD + B'D' = 0$	$AB' + CD + B'D' = 1$	B in 2 nd product
0 1 0 1 1 1 0 1	$AB' + BCD + B'D' = 0$	$AB' + BD + B'D' = 1$	C in 2 nd product
0 1 1 0 1 1 1 0	$AB' + BCD + B'D' = 0$	$AB' + BC + B'D' = 1$	D in 2 nd product
0 1 0 0 0 1 1 0 1 1 0 0 1 1 1 0	$AB' + BCD + B'D' = 0$	$AB' + BCD + D' = 1$	B' in 3 rd product
0 0 0 1 0 0 1 1	$AB' + BCD + B'D' = 0$	$AB' + BCD + B' = 1$	D' in 3 rd product
1 0 0 1 1 0 1 1	$AB' + BCD + B'D' = 1$	$BCD + B'D' = 0$	Product AB'
0 1 1 1 1 1 1 1	$AB' + BCD + B'D' = 1$	$AB' + B'D' = 0$	Product BCD
0 0 0 0 0 0 1 0	$AB' + BCD + B'D' = 1$	$AB' + BCD = 0$	Product $B'D'$



3.4 Theorems


(1) Combination theorem

$$(a) \quad A B + A B' = A$$

$$(b) \quad (A + B) (A + B') = A$$

$$\begin{aligned} \text{Proof: (a) LHS} &= A B + A B' \\ &= A (B + B') \\ &= A \bullet 1 \\ &= A = \text{RHS} \end{aligned}$$
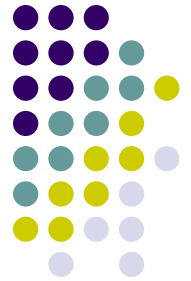
$$\begin{aligned} (b) \text{ LHS} &= (A + B) (A + B') \\ &= A + B B' \\ &= A + 0 \\ &= A = \text{RHS} \end{aligned}$$



(2) Absorption theorem

$$(a) \quad A + A B = A$$

$$(b) \quad A (A + B) = A$$


$$\begin{aligned} \text{Proof: (a) LHS} &= A + A B \\ &= A \cdot 1 + A B \\ &= A (1 + B) \\ &= A \cdot 1 \\ &= A = \text{RHS} \end{aligned}$$

$$\begin{aligned} (b) \text{ LHS} &= A (A + B) \\ &= A A + A B \\ &= A + A B \\ &= A = \text{RHS} \end{aligned}$$

❖ Example 3.3

$$(a) \quad AC + AB'CDE = (AC) + (AC) (B'DE) = AC$$
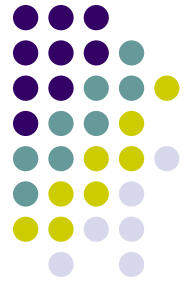
$$(b) \quad B' (A + B') (B' + CD') = B' (B' + CD') = B'$$



(3) Elimination theorem

$$(a) \quad A + A' B = A + B$$

$$(b) \quad A (A' + B) = A B$$


$$\begin{aligned} \text{Proof: (a) LHS} &= A + A' B \\ &= (A + A') (A + B) \\ &= 1 \cdot (A + B) \\ &= A + B = \text{RHS} \end{aligned}$$

$$\begin{aligned} (b) \text{ LHS} &= A (A' + B) \\ &= A A' + A B \\ &= 0 + A B \\ &= A B = \text{RHS} \end{aligned}$$

❖ Example 3.4

$$\begin{aligned} (a) \quad AC' + AB'CDE' &= A (C' + B'CDE') = A [C' + C(B'DE')] \\ &= A (C' + B'DE') = AC' + AB'DE' \end{aligned}$$
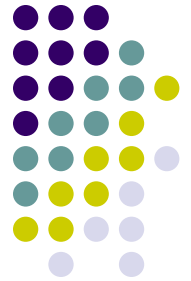
$$\begin{aligned} (b) \quad (B + C') (A + B + C' + D + E) \\ &= (B + C') [(B + C') + (A + D + E)] \\ &= B + C' \end{aligned}$$




❖ Example 3.5

Simplify the sum-of-products expression $(AB' + BCD + A'B'D')$.

This example is the revisit of Example 3.1. By applying the elimination theorem
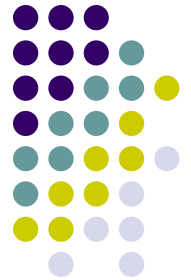
$$\begin{aligned} & AB' + BCD + A'B'D' \\ &= BCD + B'(A + A'D') \\ &= BCD + B'(A + D') \\ &= AB' + BCD + B'D' \end{aligned}$$



(4) Consensus theorem


$$(a) \quad A B + A' C + B C = A B + A' C$$

$$(b) \quad (A + B) (A' + C) (B + C) = (A + B) (A' + C)$$

$$\begin{aligned} \text{Proof: (a) LHS} &= A B + A' C + B C \\ &= A B + A' C + 1 \cdot B \cdot C \\ &= A B + A' C + (A + A') B C \\ &= A B + A' C + A B C + A' B C \\ &= (A B) + (A B) C + (A' C) + (A' C) B \\ &= A B + A' C = \text{RHS} \end{aligned}$$

❖ Example 3.6
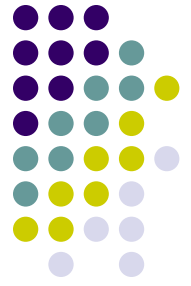
$$\begin{aligned} &\begin{array}{cc} \text{Variable in true form} & \text{Variable in complemented form} \end{array} \\ &\quad \swarrow \quad \searrow \\ &A B D' + A B C' + C D' \\ &= A B D' + C' (A B) + C (D') \\ &\quad \swarrow \quad \searrow \\ &\quad (A B) (D') = A B D' \quad \leftarrow \text{Consensus term} \\ &= A B C' + C D' \end{aligned}$$



❖ Example 3.7

$$B D' + A B' C' + A' C' D'$$

$$\text{Consensus term from } A \text{ and } A' \longrightarrow (B' C') (C' D') = B' C' D'$$

$$B D' + A B' C' + A' C' D'$$


\uparrow \nwarrow
 \swarrow \downarrow

$$\text{Consensus term from } B \text{ and } B' \longrightarrow D' (A C') = A C' D'$$

$$B D' + A B' C' + A' C' D' = B D' + A B' C' + A' C' D' + A C' D'$$

$$A' C' D' + A C' D' = (A' + A) C' D' = C' D'$$

$$B D' + A B' C' + C' D'$$

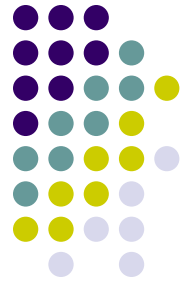

❖ Example 3.8

$$A'C + BCD + AC'D + AB'C'$$

$$A'C + \underline{BCD} + \underline{AC'D} + AB'C' = A'C + \underline{BCD} + \underline{AC'D} + AB'C' + \underline{ABD}$$

$$\underline{A'C} + \underline{BCD} + AC'D + AB'C' + \underline{ABD} = A'C + AC'D + AB'C' + ABD$$

$$A'C + \underline{AC'D} + \underline{AB'C'} + \underline{ABD} = A'C + AB'C' + ABD$$



(5) Interchange Theorem

$$A B + A' C = (A + C) (A' + B)$$

Proof: $\text{RHS} = (A + C) (A' + B)$

$$= A A' + A B + A' C + B C$$

$$= 0 + A B + A' C + B C$$

$$= A B + A' C + B C$$

$$= A B + A' C = \text{LHS}$$



POS to SOP

$$(A + B + C)(A + B + D)$$

$$= AA + AB + AD + AB + BB + BD + AC + BC + CD$$

$$= A + AB + AD + B + BD + AC + BC + CD$$

$$= A + B + BD + BC + CD = A + B + CD$$




POS to SOP

$$\begin{aligned} & (A + B + C)(A + B + D) \\ &= AA + AB + AD + AB + BB + BD + AC + BC + CD \end{aligned}$$

$$\begin{aligned} & AA + AB + AD + AB + BB + BD + AC + BC + CD \\ &= A + AB + AD + B + BD + AC + BC + CD \\ &= A + B + BD + BC + CD = A + B + CD \end{aligned}$$
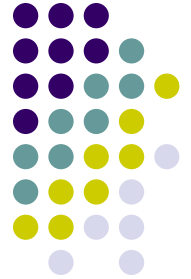
$$\begin{aligned} & (A + B + C)(A + B + D) \\ &= [\underline{(A + B) + C}] [\underline{(A + B) + D}] \\ & \quad \swarrow \quad \searrow \\ &= \underline{(A + B) + CD} \end{aligned}$$




Sandwich Algorithm

Distributive law (collections)


Interchange Theorem

Distributive law (distribution)

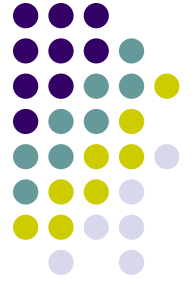

❖ Example 3.9
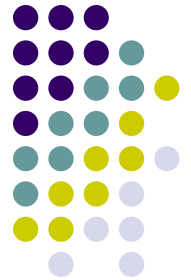
$$\begin{aligned} & (\underline{A + B + C})(\underline{A + B + D})(\underline{A + B + E})(B' + D') \\ & \quad \downarrow \quad \swarrow \quad \searrow \\ & = (\underline{A + B + CDE}) (B' + D') \\ & = [\textcolor{green}{B} + (\textcolor{violet}{A} + \textcolor{violet}{CDE})] (\textcolor{violet}{B'} + \textcolor{green}{D'}) \\ & = BD' + B' (A + CDE) \\ & = BD' + AB' + B' CDE \end{aligned}$$



❖ Example 3.10


Convert $(BCD' + B'D + AB)$ to a product-of-sums expression.

$$BCD' + B'D + AB = B(A + CD') + B'D$$

$$(B + D)(B' + A + CD')$$

$$A + B' + CD' = (A + B' + C)(A + B' + D')$$
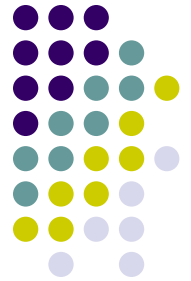
$$BCD' + B'D + A'B = (B + D)(A + B' + C)(A + B' + D')$$




❖ Example 3.11 POS to SOP

$$(A + B) (A' + C) (C' + D)$$

$$= (AC + A'B) (C' + D)$$

$$= ACC' + ACD + A'BC' + A'BD$$

$$= ACD + A'BC' + A'BD$$

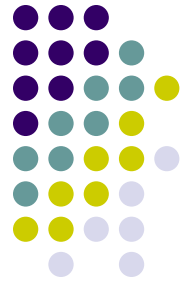

❖ Example 3.12


Convert the SOP expression $(A'B + CD)$ to a POS.

$$A'B + CD = (A'B + C)(A'B + D)$$

$$C + A'B = (C + A')(C + B)$$

$$D + A'B = (D + A')(D + B)$$
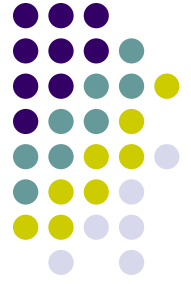
$$A'B + CD = (A' + C)(B + C)(A' + D)(B + D)$$



(6) DeMorgan's theorem

$$(a) \quad (A \bullet B)' = A' + B'$$

$$(b) \quad (A + B)' = A' \bullet B'$$

Distribute the prime, Change the sign

Collect the primes, change the sign



(6) DeMorgan's theorem

(a) $(A \cdot B)' = A' + B'$

(b) $(A + B)' = A' \cdot B'$

Table 3.9 Proof of DeMorgan's theorem (6a).


A	B	A B	Left-hand-side of (6a) $(A B)'$	A'	B'	Right-hand-side of (6a) $A' + B'$	$A' \cdot B'$
0	0	0	1	1	1	1	1
0	1	0	1	1	0	1	0
1	0	0	1	0	1	1	0
1	1	1	0	0	0	0	0

$(A B)' \neq A' B'$

$(A + B)' \neq A' + B'$

$$(a) (x_1 \bullet x_2 \bullet x_3 \bullet \dots \bullet x_{n-1} \bullet x_n)' = x_1' + x_2' + x_3' + \dots + x_{n-1}' + x_n'$$
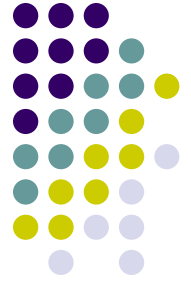
$$(b) (x_1 + x_2 + x_3 + \dots + x_{n-1} + x_n)' = x_1' \bullet x_2' \bullet x_3' + \dots \bullet x_{n-1}' \bullet x_n'$$



$$(x_1 \bullet x_2 \bullet x_3)' = ((x_1 \bullet x_2) \bullet x_3)' = (x_1 \bullet x_2)' + x_3'$$

$$= (x_1' + x_2') + x_3' = x_1' + x_2' + x_3'$$

$$(x_1 \bullet x_2 \bullet x_3 \bullet \dots \bullet x_{n-1})' = x_1' + x_2' + x_3' + \dots + x_{n-1}'$$

$$(x_1 \bullet x_2 \bullet x_3 \bullet \dots \bullet x_{n-1} \bullet x_n)'$$

$$= ((x_1 \bullet x_2 \bullet x_3 \bullet \dots \bullet x_{n-1}) \bullet x_n)'$$

$$= (x_1 \bullet x_2 \bullet x_3 \bullet \dots \bullet x_{n-1})' + x_n'$$

$$= (x_1' + x_2' + x_3' + \dots + x_{n-1}') + x_n'$$


$$= x_1' + x_2' + x_3' + \dots + x_{n-1}' + x_n'$$



$$(a) (x_1 \bullet x_2 \bullet x_3 \bullet \dots \bullet x_{n-1} \bullet x_n)' = x_1' + x_2' + x_3' + \dots + x_{n-1}' + x_n'$$


$$(b) (x_1 + x_2 + x_3 + \dots + x_{n-1} + x_n)' = x_1' \bullet x_2' \bullet x_3' + \dots \bullet x_{n-1}' \bullet x_n'$$

Distribute the prime, Change the sign
Collect the primes, change the sign

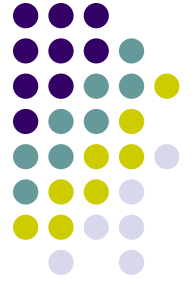

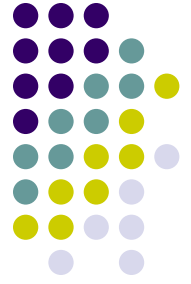Example 3.13



$$\begin{aligned} & [A' + B(C + D') + E]' \\ &= A \bullet [B (C + D')] ' \bullet E' \\ &= A \bullet [B' + (C + D')'] \bullet E' \\ &= A \bullet (B' + C' D) \bullet E' \\ &= AB'E' + AC'DE' \end{aligned}$$





Eliminating of internal inversions by gate equivalencies

$$(a) (x_1 \bullet x_2 \bullet x_3 \bullet \dots \bullet x_{n-1} \bullet x_n)' = x_1' + x_2' + x_3' + \dots + x_{n-1}' + x_n'$$

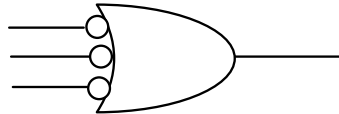
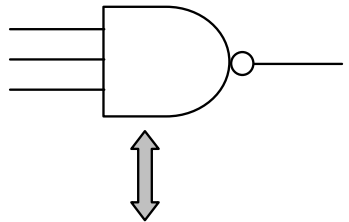
$$(b) (x_1 + x_2 + x_3 + \dots + x_{n-1} + x_n)' = x_1' \bullet x_2' \bullet x_3' + \dots \bullet x_{n-1}' \bullet x_n'$$





(a)

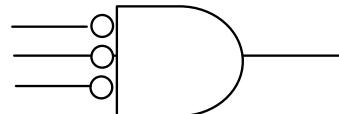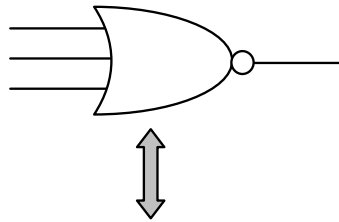

(b)

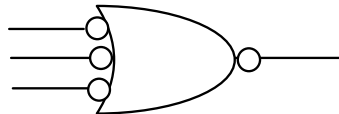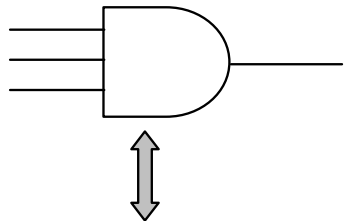

(c)

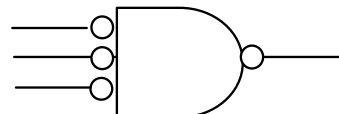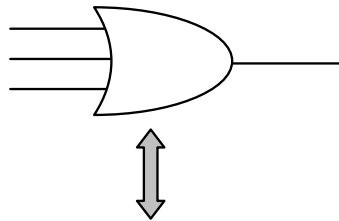


(d)

Move bubble(s),
change symbol.

Add bubble(s),
change symbol.

Figure 4.13 Gate equivalencies using DeMorgan's theorem.

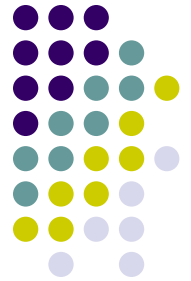

Minimization of Literals


❖ Example 3.14

$$F(A,B,C,D) = BD + CD + A'BC + ABC'$$

$$D(B + C) + B(A'C + AC')$$

$$CD + B(D + A'C + AC')$$

$$B(D + AC') + C(D + A'B)$$

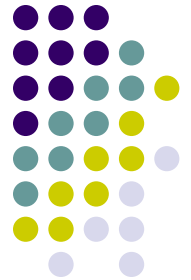

❖ Example 3.15

$$F(A,B,C,D) = (A + C') (B + D) (A' + C + D)$$

$$\begin{aligned} F(A,B,C,D) &= (A + C') (B + D) (A' + C + D) \\ &= (A + C') [D + B(A' + C)] \end{aligned}$$

.

$$\begin{aligned} F(A,B,C,D) &= (A + C') (B + D) (A' + C + D) \\ &= (B + D) (A + C') [A' + (C + D)] \\ &= (B + D) [A'C' + A(C + D)] \end{aligned}$$

Duality



AND	→	OR
OR	→	AND
0	→	1
1	→	0

$$F^D(x_{n-1}, x_{n-2}, \dots, x_2, x_1, x_0, 0, 1, \bullet, +)$$

$$= F(x_{n-1}, x_{n-2}, \dots, x_2, x_1, x_0, 1, 0, +, \bullet)$$

Laws of 0 and 1: (L3a')

$$A \bullet 0 = 0$$



Laws of 0 and 1: (L3b')

$$A + 1 = 1$$

Distributive law: (7a)

$$A \bullet (B + C) = (A \bullet B) + (A \bullet C)$$



Distributive law: (7b)

$$A + (B \bullet C) = (A + B) \bullet (A + C)$$



❖ Example 3.11

$$F = [A' + B (C + D') + E \bullet 0]' \bullet B'$$

F fully parenthesized:

$$F = \{ A' + [B \bullet (C + D')] + (E \bullet 0) \}' \bullet B'$$

$\downarrow \quad \downarrow \quad \downarrow \quad \downarrow \quad \downarrow \downarrow \quad \downarrow$

Transformation:

$$F^D = \{ A' \bullet [B + (C \bullet D')] \bullet (E + 1) \}' + B'$$

$$= [A' (B + C D') (E + 1)]' + B'$$

Positive Logic and Negative Logic

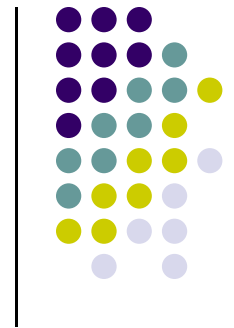
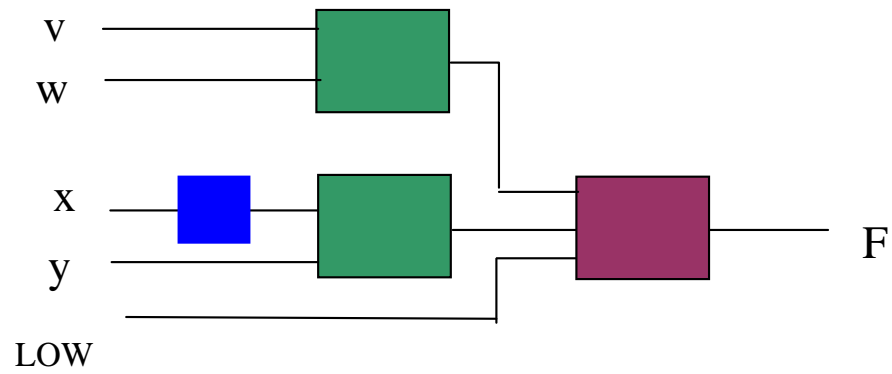


Table 3.10 Truth tables for three types of gates

(a)

Input	Output
L	H
H	L



(b)

Inputs	Output
L L	L
L H	L
H L	L
H H	H


(c)

Inputs	Output
L L L	L
L L H	H
L H L	H
L H H	H
H L L	H
H L H	H
H H L	H
H H H	H

Positive Logic and Negative Logic

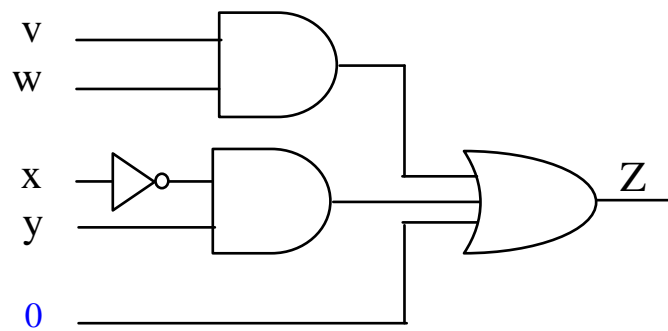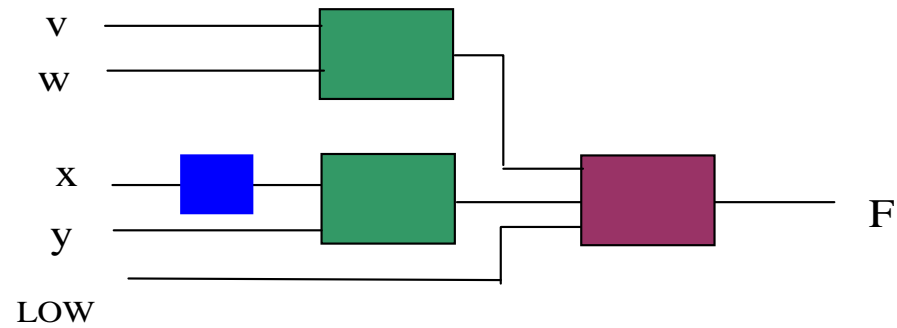

(a)

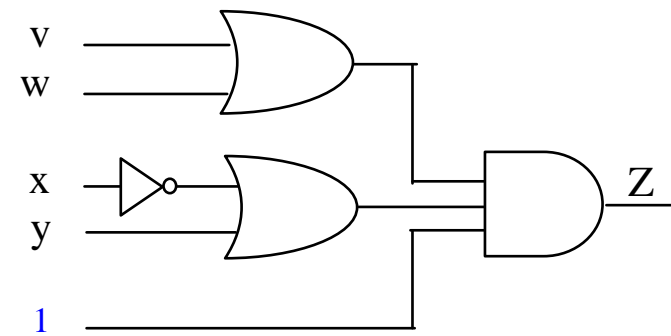

(b)

Figure 3.7 A digital circuit with different logic. (a) Positive logic. (b) Negative logic.

Positive Logic

$$Z = vw + x'y + 0$$

Negative Logic

$$Z = (v + w) \bullet (x' + y) \bullet 1$$

